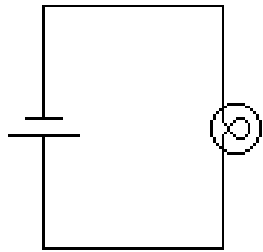



PHYSICS 2401
Lab Homework– Circuits I

This homework will be due when you come to lab the week of February 24.


Rank the current through all the bulbs for each of the following circuits. Explain your reasoning. For circuit 4, draw an ammeter that will measure the current through the bulb at the bottom left. Explain your reasoning.




1

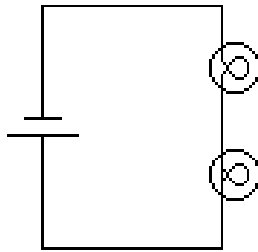


2

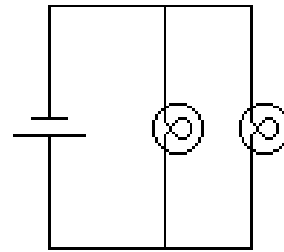

3

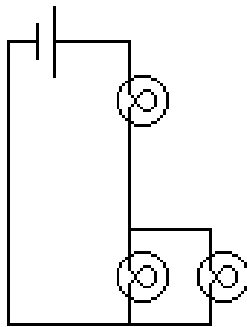

4

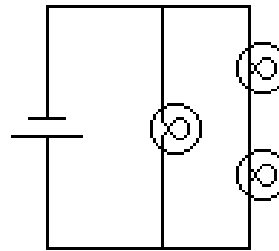

5