

## Homework 5

Due Date:4/22/2019

Show your full work for full credit. Upload your work in Blackboard. Don't submit hard copies or email. You can scan/take pictures, convert into one pdf file to submit.


Total Marks 30+30+20+20= 100

1. A sequential circuit with two D flipflops A and B , two inputs X and Y , and one output Z is specified by the following input equations:

$$D_A = XA + \bar{X}\bar{Y} \quad D_B = A\bar{X} + XB, \quad Z = \bar{X}B$$


- a) Draw the logic diagram
- b) Derive the state table
- c) Derive the state diagram

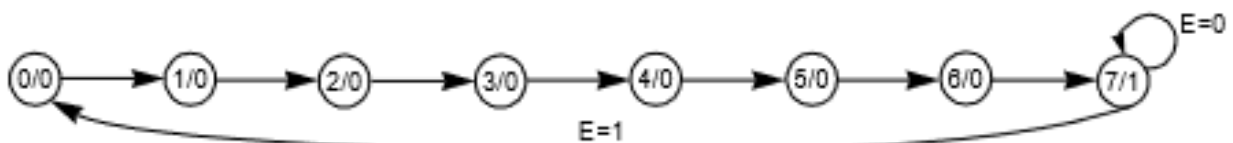2. The state diagram for a sequential circuit is given below:



- a) Find the state table for the circuit, make a state assignment for the circuit using 3 bit codes.
- b) Find an optimized circuit implementation using D flip flop and other necessary gates.
- c) Draw the logic diagram of the circuit.

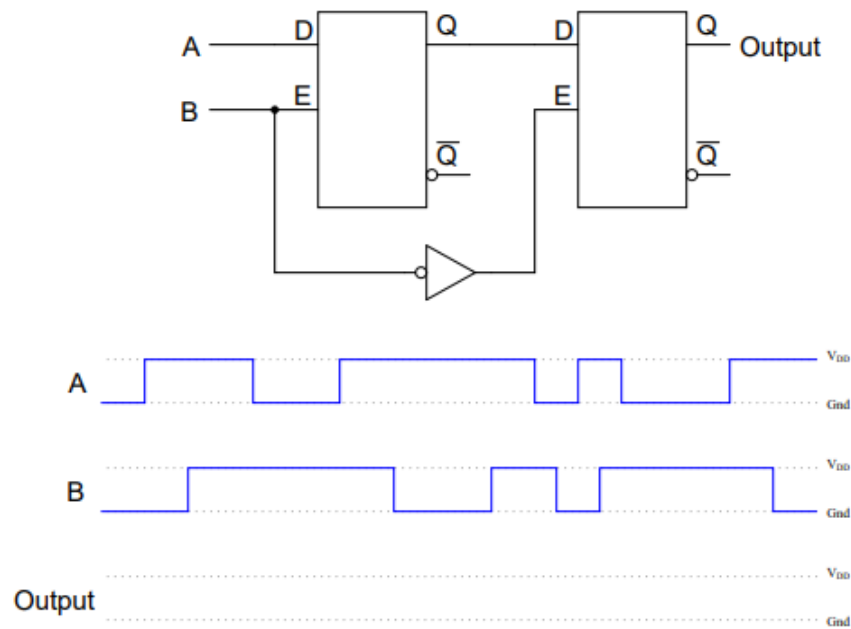3. Determine the final output states over time for the following circuit.



4. Determine the output state for this J-K flip-flop, given the pulse inputs shown:

