




Modern Digital System Design

ECE 2372 / Fall 2018 / Lecture 11

Texas Tech University
Dr. Tooraj Nikoubin

Sequential Circuit Elements

 


Outline




- Combinational Vs Sequential Logic Design
- Design a new building block, a **flip-flop**, that stores one bit
- Combine that block to build multi-bit storage – a **register**
- Describe the sequential behavior using a **finite state machine (FSM)**
- Convert a finite state machine to a **controller** – a sequential circuit having a register and combinational logic

 
- Design a new building block, a **flip-flop**, that stores one bit
- Latch Vs Flip Flop
- Master Slave Flip-Flop
- D Flip-Flop, J-K Flip-Flop and T Flip-Flop
- Combine that block to build multi-bit storage – a **register**



Combinational Vs Sequential Logic

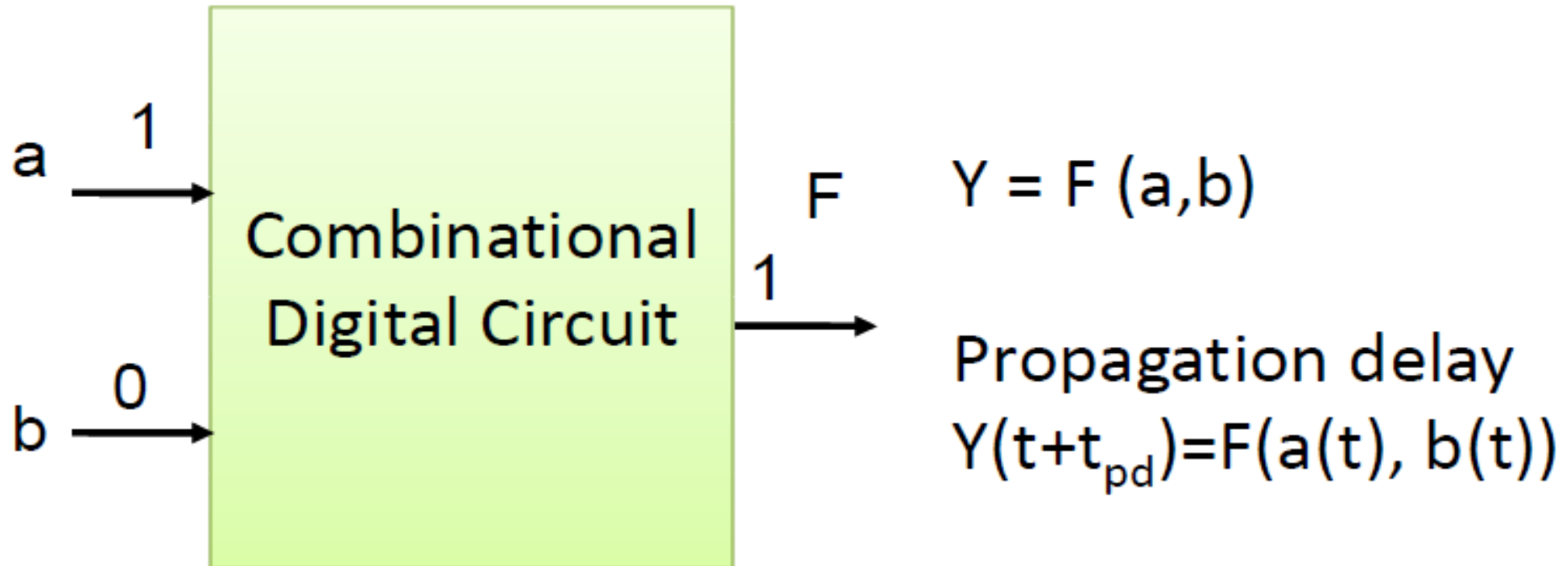
- Combinational circuit
 - Output depends on present input
 - Examples: F (A,B,C), FA, HA, Multiplier, Decoder, Multiplexor, Adder, Priority Encoder




 


Combinational Vs Sequential Logic

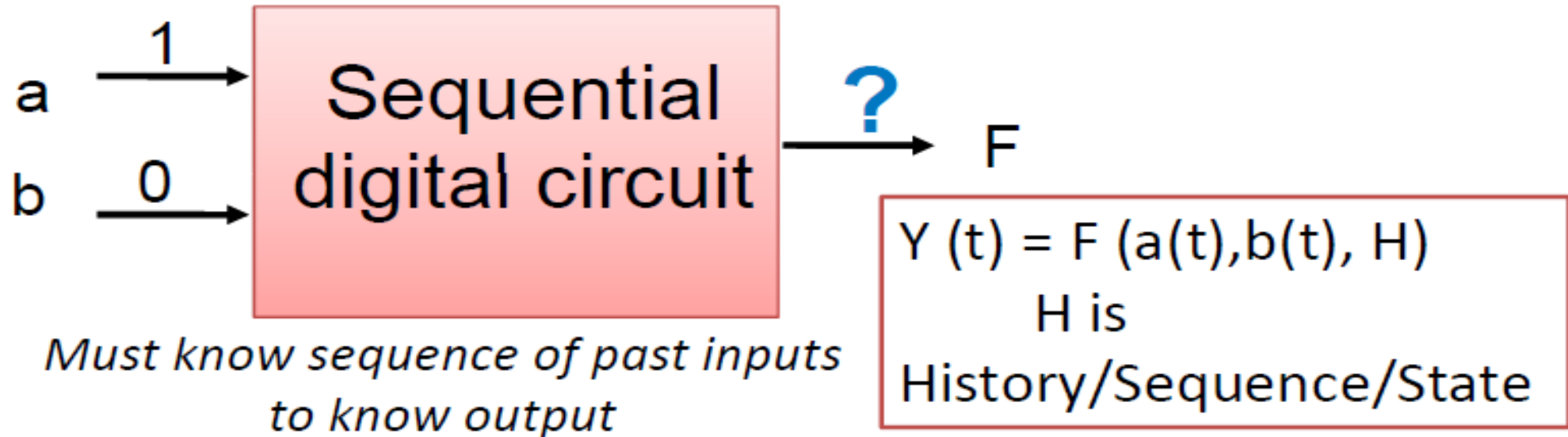- Sequential circuit
 - Output depends not just on present inputs
 - But also on past sequence of inputs (State)
 - Stores bits, also known as having “state”
- Simple example: a circuit that counts up in binary



 

Sequential Circuit

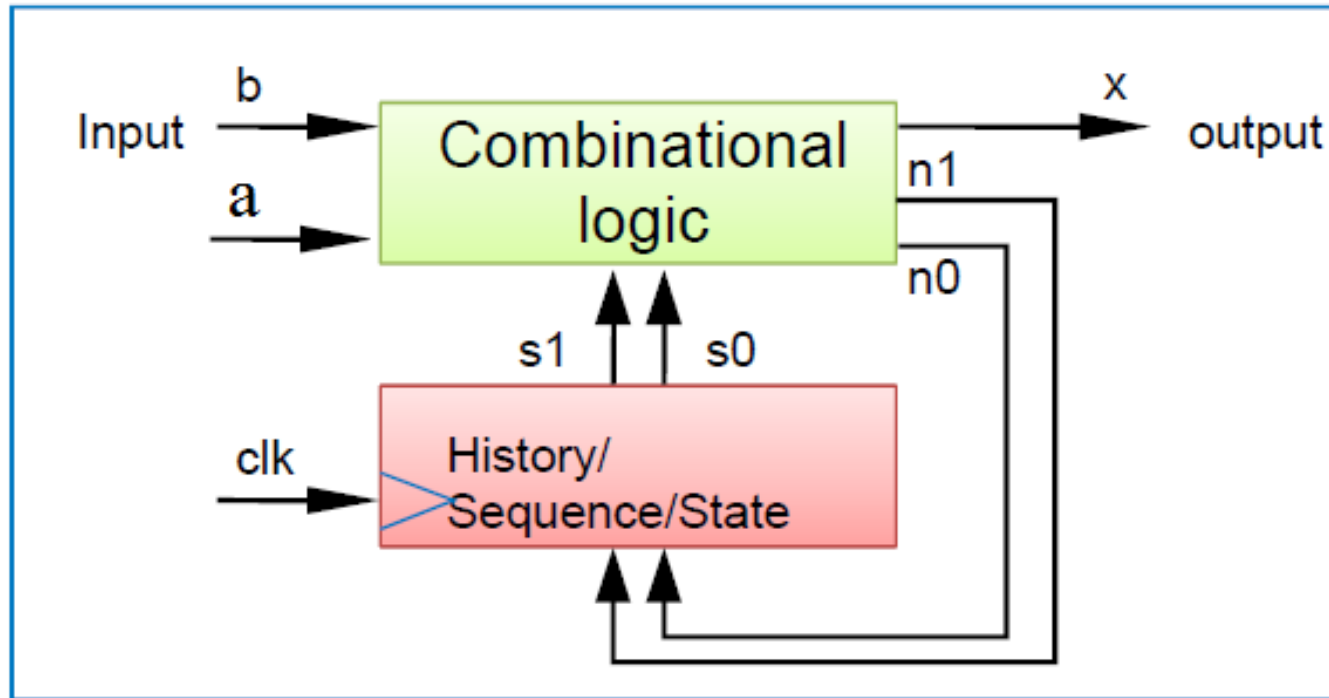


$$Y(t) = F(a(t), b(t), H)$$

H is History/Sequence/State


Where to
Store this
History

(Memory
Element)

 


 Example Needing Bit Storage


- Flight attendant call button
 - Press call: light turns on
 - **Stays on** after button released
 - Press cancel: light turns off
 - Logic gate circuit to implement this?



 
Doesn't work. $Q=1$ when $\text{Call}=1$, but doesn't stay 1 when Call returns to 0



1. Call button pressed – light turns on

 


 2. Call button released – light **stays on**



 
3. Cancel button pressed – light turns off


Need some form of “feedback” in the circuit



First attempt at Bit Storage






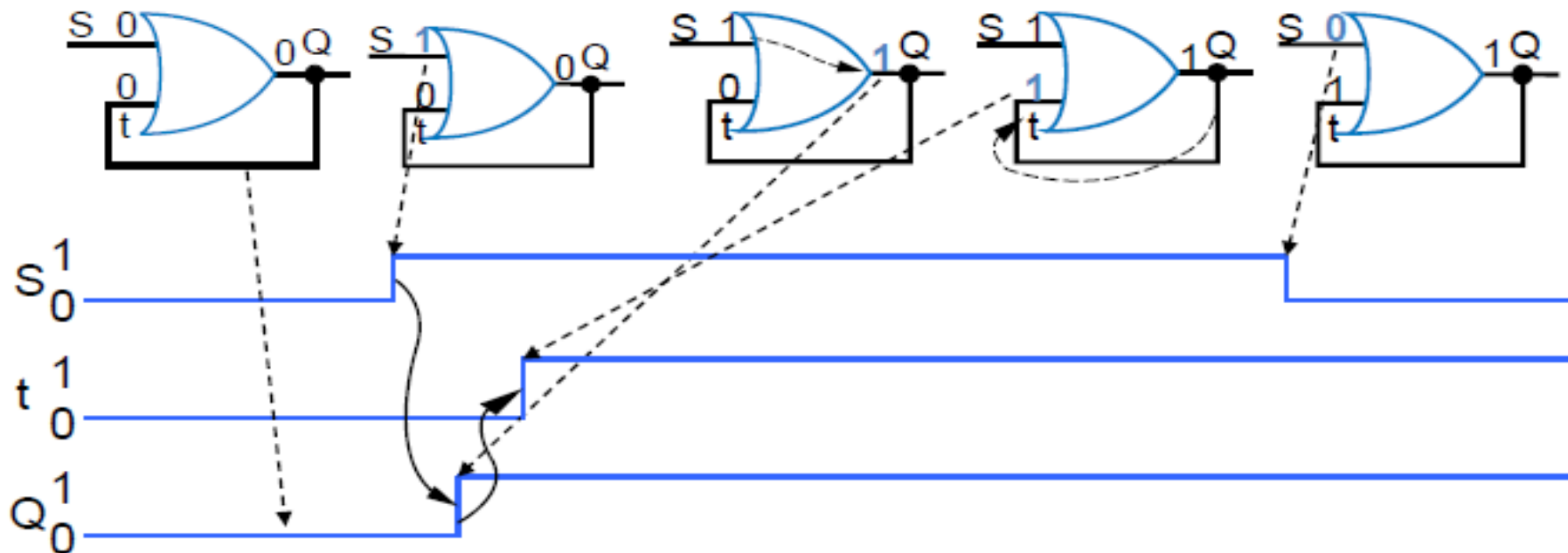
- We need some sort of feedback
 - Does circuit on the right do what we want?
 - No: Once Q becomes 1 (when $S=1$), Q stays 1 forever – no value of S can bring Q back to 0




 

Bit Storage Using an SR Latch

     
 
- Does the circuit to the right, with cross-coupled NOR gates, do what we want?
 - Yes! How did someone come up with that circuit? Maybe just trial and error, a bit of insight...




 

  Example Using SR Latch for Bit Storage


- SR latch can serve as bit storage in previous example of flight-attendant call button
 - Call=1 : sets Q to 1
 - Q stays 1 even after Call=0
 - Cancel=1 : resets Q to 0
- But, there's a problem...



 



Problem with SR Latch

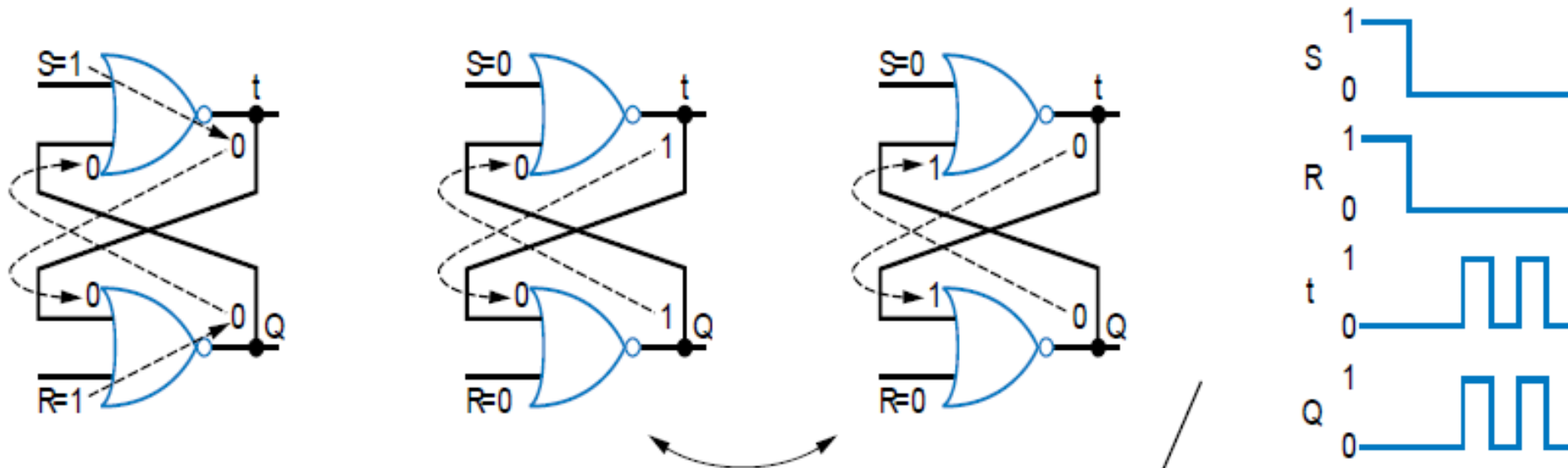- Problem
 - If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take



 
Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



 



Problem with SR Latch

 - Problem not just one of a user pressing two buttons at same time
- Can also occur even if SR inputs come from a circuit that supposedly never sets $S=1$ and $R=1$ at same time
 - But does, due to different delays of different paths




 
The longer path from X to R than to S causes $SR=11$ for short time – could be long enough to cause oscillation



 


Solution: Level-Sensitive SR Latch

  - Add enable input “C” as shown
 - Only let S and R change when C=0
 - Ensure circuit in front of SR never sets $SR=11$, except briefly due to path delays
 - Change C to 1 only after sufficient time for S and R to be stable
 - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch’s S1 R1 inputs.






Level-sensitive
SR latch symbol

 


Solution: Level-Sensitive SR Latch

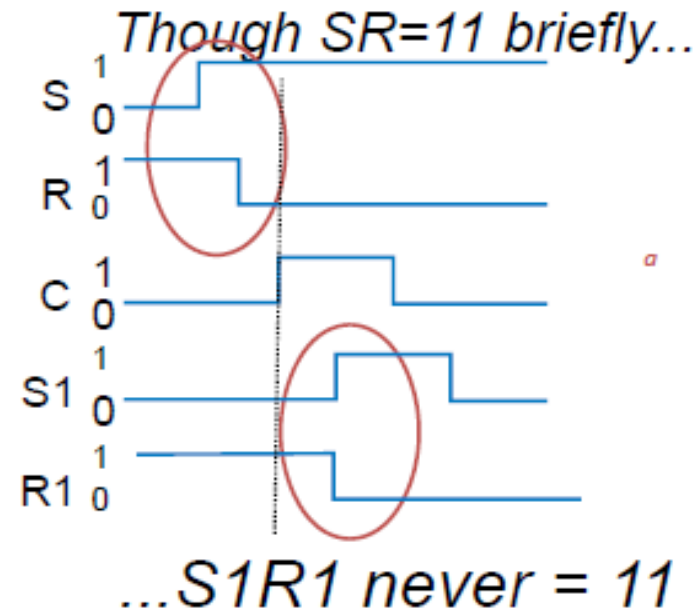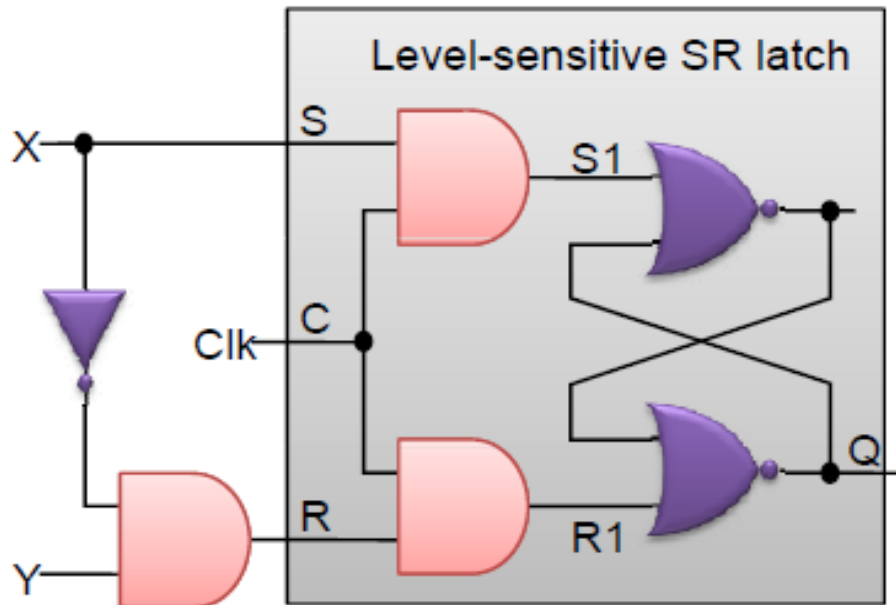- Add enable input “C” as shown
 - Only let S and R change when C=0
 - Ensure circuit in front of SR never sets $SR=11$, except briefly due to path delays
 - Change C to 1 only after sufficient time for S and R to be stable
 - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch’s S1 R1 inputs.



 


Solution: Ensure, Stabilize, Store

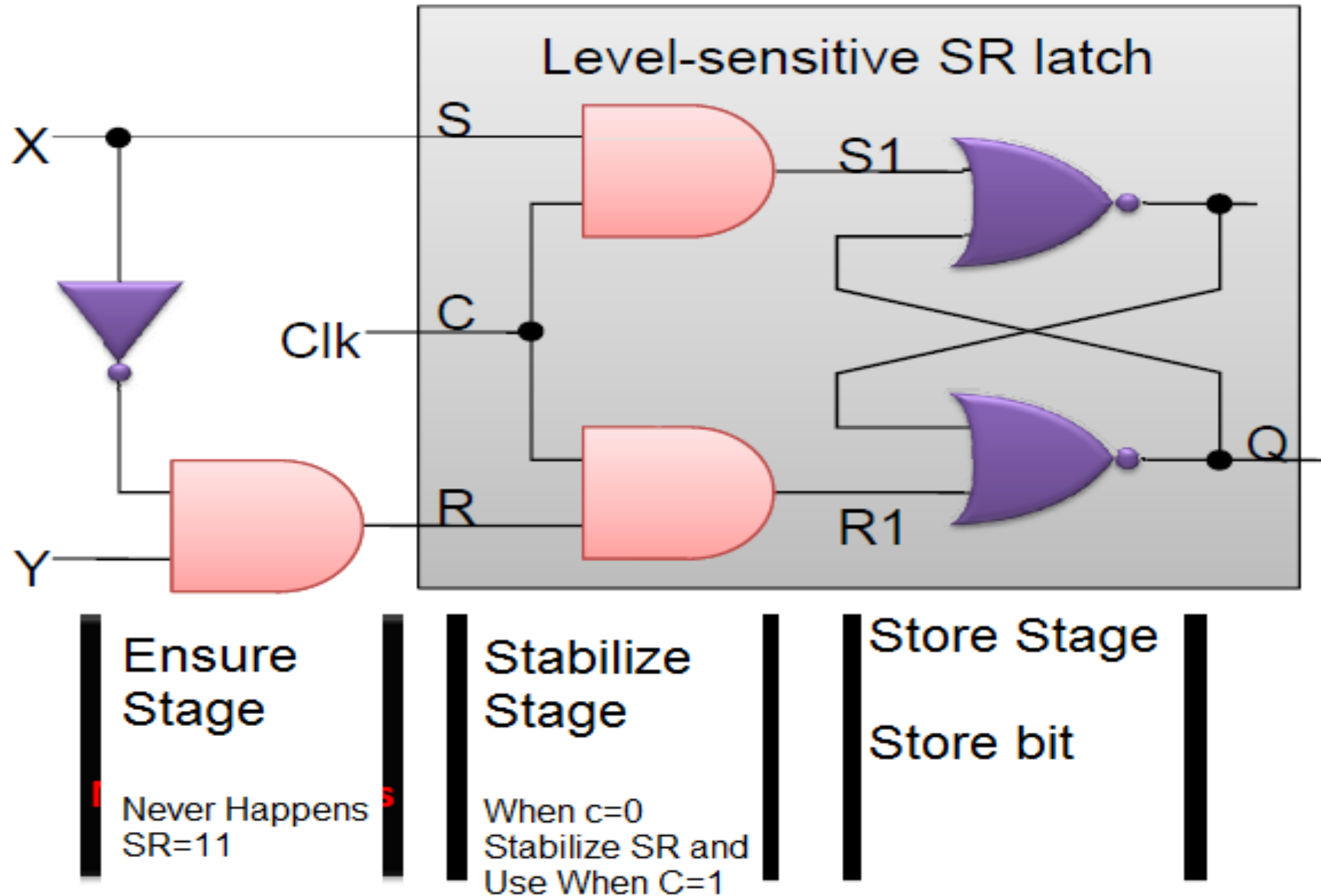




Clocks

 


- **Clock period:** time interval between pulses
 - Above signal: period = 20 ns
- **Clock cycle:** one such time interval
 - Above signal shows 3.5 clock cycles
- **Clock frequency:** $1/\text{period}$
 - Above signal: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$
 - $1 \text{ Hz} = 1/\text{s}$


Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

 

Clock Signals for a Latch



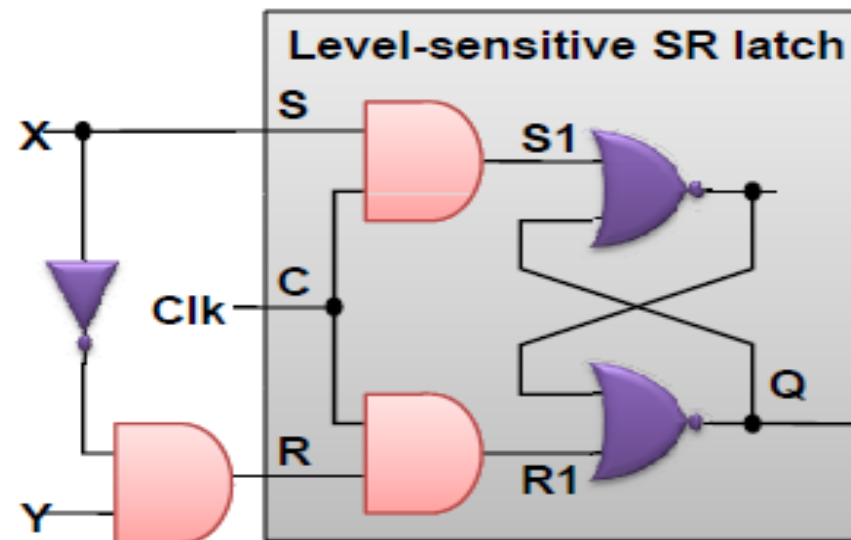
- How do we know when it's safe to set $C=1$?
 - Most common solution –make C pulse up/down
 - $C=0$: Safe to change X, Y $C=1$: Must *not* change X, Y
 - **Clock** signal -- Pulsing signal used to enable latches
 - Because it ticks like a clock
 - Sequential circuit whose storage components all use clock signals: **synchronous** circuit



 


Level-Sensitive D Latch

  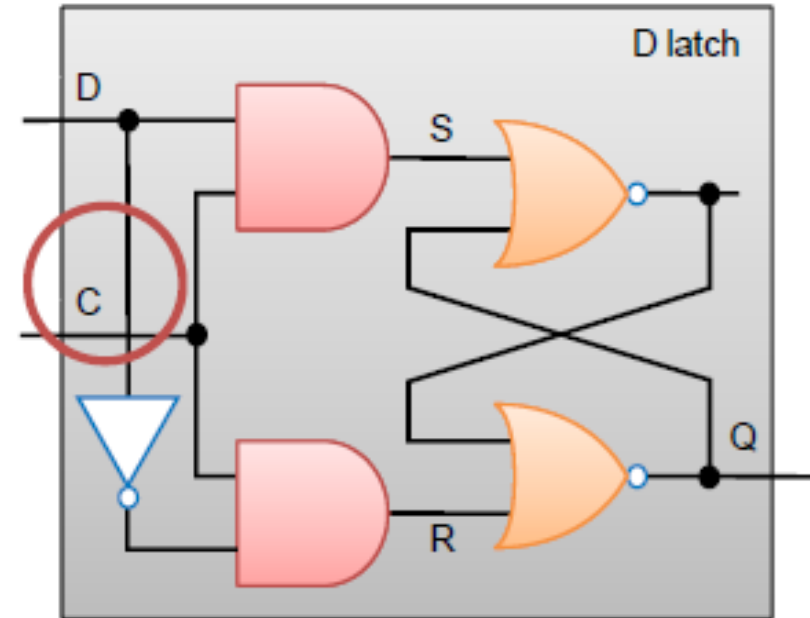- SR latch requires careful design to ensure $SR=11$ never occurs
- D latch relieves designer of that burden
 - Inserted inverter ensures R always opposite of S





D latch symbol

 

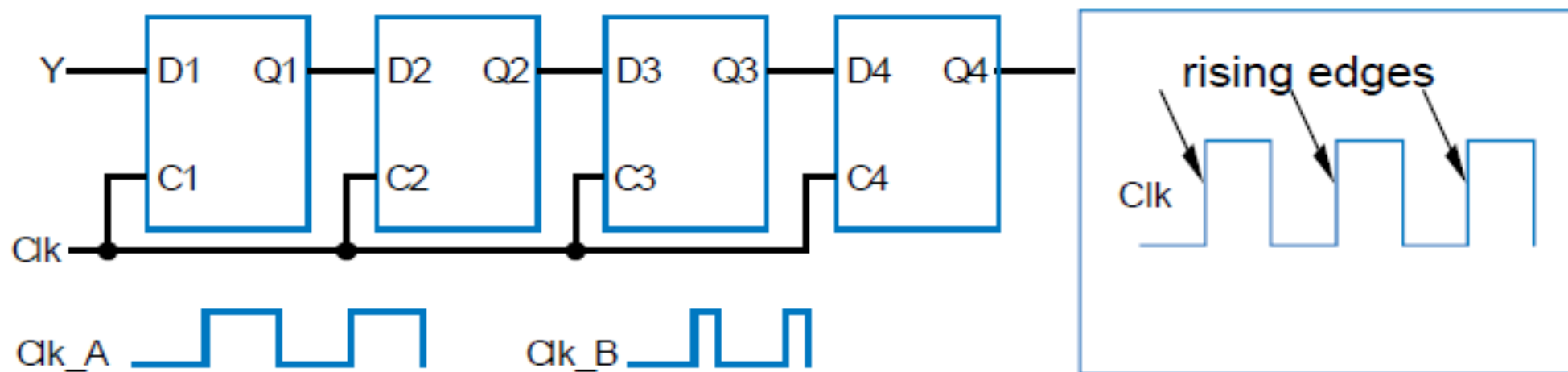Problem with Level-Sensitive D Latch



- D latch still has problem (as does SR latch)
 - When $C=1$, through how many latches will a signal travel?
 - Depends on for how long $C=1$
 - Clk_A -- signal may travel through multiple latches
 - Clk_B -- signal may travel through fewer latches
 - Hard to pick C that is just the right length
 - Can we design bit storage that only stores a value on the rising edge of a clock signal?




 

Master -Slave D Flip-Flop

 
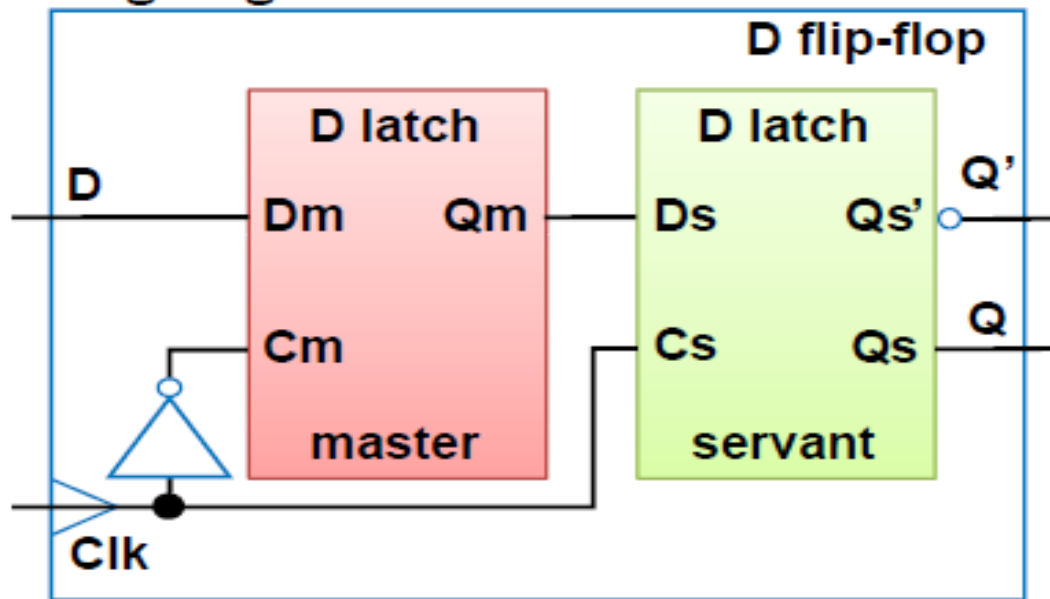
- ***Flip-flop***: stores on clock edge, not level
- Two latches, output of first goes to input of second, master latch has inverted clock signal
- So master loaded when $C=0$, then servant when $C=1$
- When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed -- i.e., value at D during rising edge of C



 

D Flip-Flop

  The triangle means clock input, edge triggered




Symbol for falling-edge triggered D flip-flop

rising edges




falling edges



 


D Flip-Flop

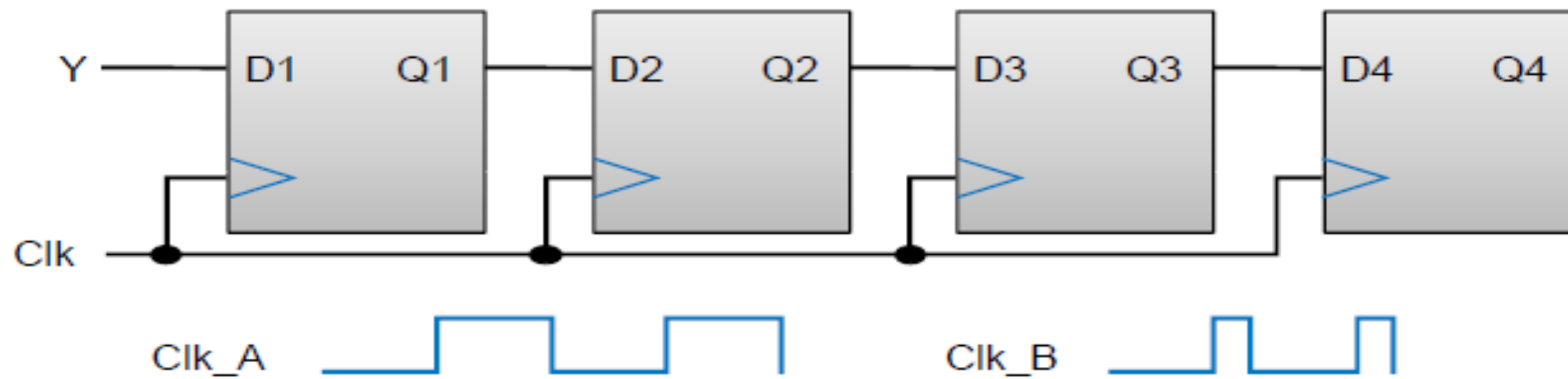- Solves problem of not knowing through how many latches a signal travels when $C=1$
 - Signal travels through exactly one flip-flop, for Clk_A or Clk_B
 - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.




Two latches inside each flip-flop

 


D Flip-Flop

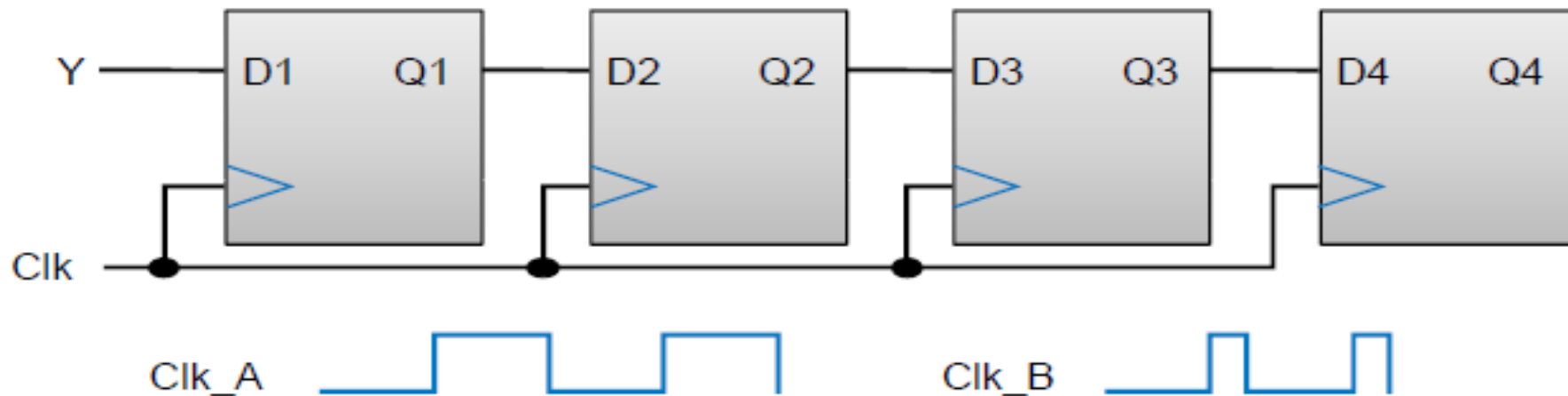- Solves problem of not knowing through how many latches a signal travels when $C=1$
 - Signal travels through exactly one flip-flop, for Clk_A or Clk_B
 - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.





Two latches inside each flip-flop

 


D Latch vs. D Flip-Flop

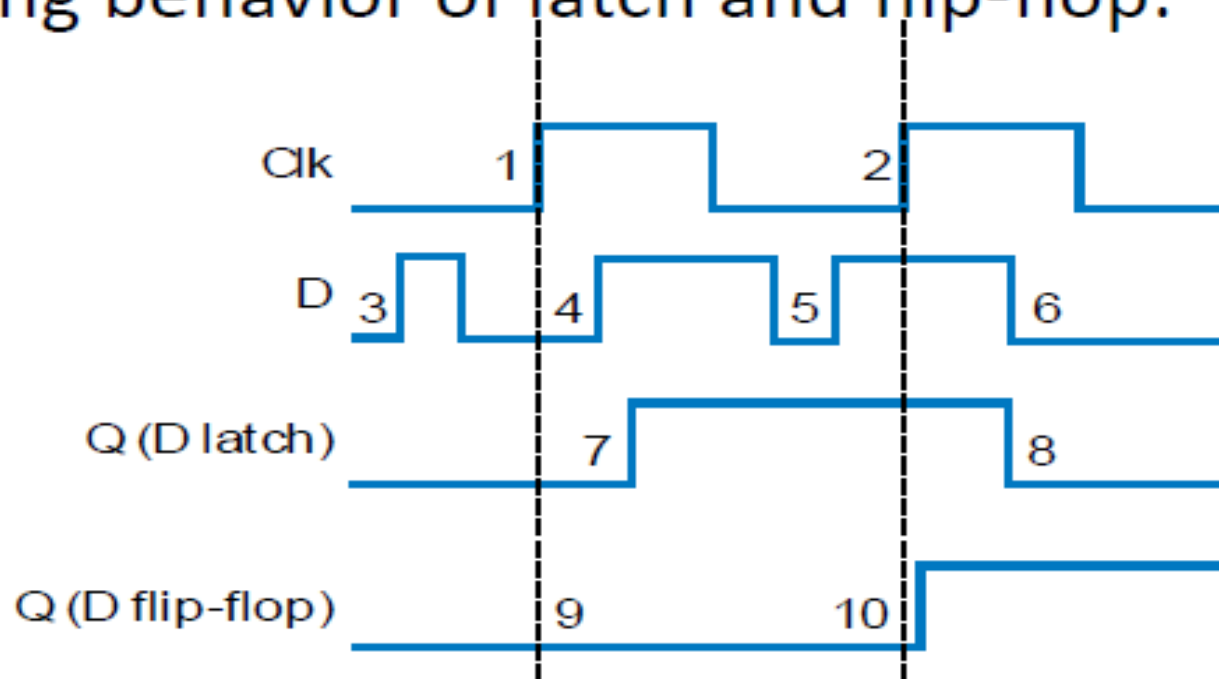- Latch is level-sensitive: Stores D when C=1
- Flip-flop is edge triggered: Stores D when C changes from 0 to 1
 - Saying “level-sensitive latch,” or “edge-triggered flip-flop,” is redundant
 - Two types of flip-flops -- rising or falling edge triggered.
- Comparing behavior of latch and flip-flop:




 

S'R' Latch

 



S'	R'	Q+
0	0	1*0* (Unpredictable)
0	1	1
1	0	0
1	1	Q

 

Conventions

 
- The circuit is *set* means output = 1
- The circuit is *reset* means output = 0
- Flip-flops have two output Q and Q'
- Due to time related characteristic of the flip-flop:
 - Q_t or Q: present state
 - Q_{t+1} or Q^+ : next state



 


4 Type of Flip Flop

 - **SR Flip Flop** : Set/Reset Flip Flop
- **D Flip Flop** : Data Flip Flop to store Bit
- **J-K Flip Flop**: SR with use of the unavoidable $SR=11$ state to Toggle (All input values are useful)
- **T Flip Flop**: Toggle Flip Flop




J-K Flip Flop

 - The JK flip-flop augments the behavior of the SR flip-flop (J=Set, K=Reset) by interpreting the $S = R = 1$ condition as a "flip" or toggle command.




J	K	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '


$$Q^+ = K'Q + JQ'$$

 

Master Slave J-K Flip Flop

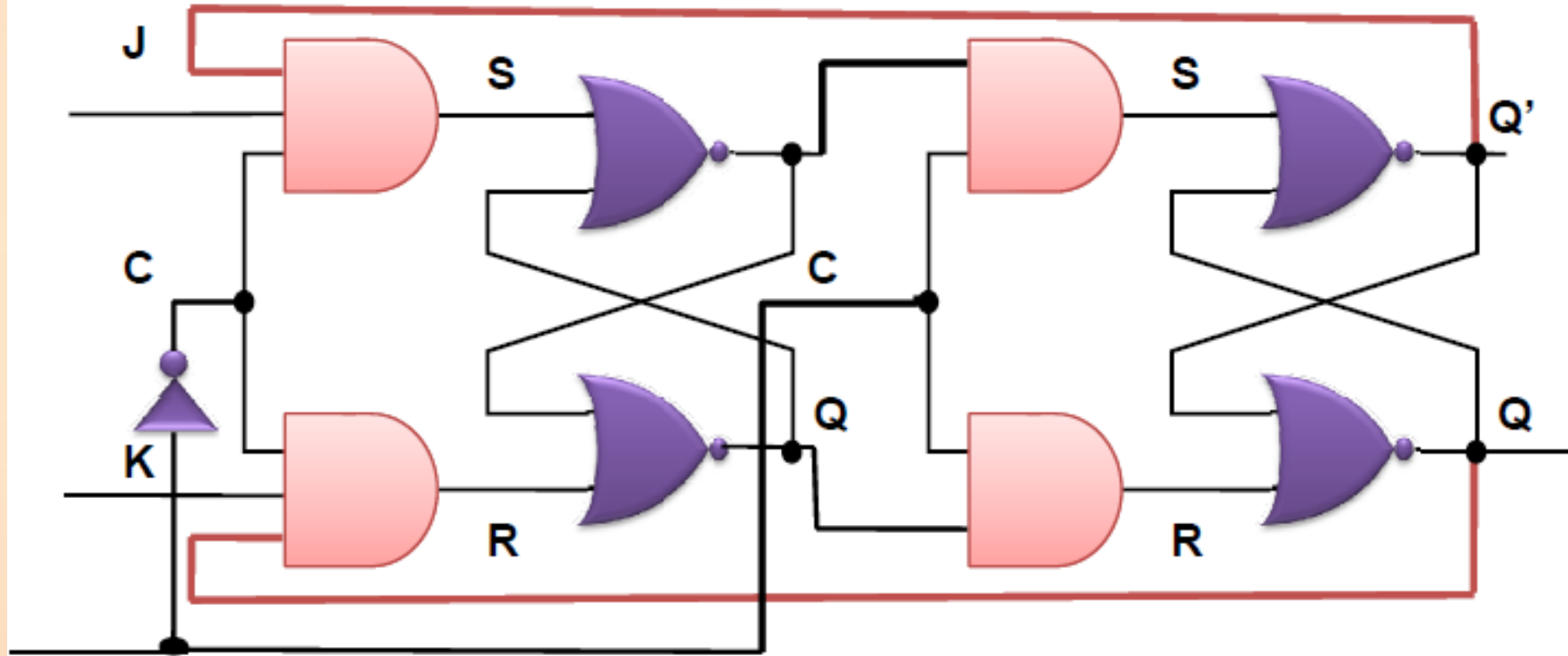

$$Q^+ = K'Q + JQ'$$

 


J-K Flip Flop

- To synthesize a D flip-flop, simply set K equal to the complement of J.
- The JK flip-flop is a universal flip-flop
 - Because it can be configured to work as any FF
 - T flip-flop or D flip-flop or SR flip-flop.

J=T	K=T	Q+
0	0	Qt
0	1	0
1	0	1
1	1	Qt'



J=D	K=D'	Q+
0	0	Qt
0	1	0
1	0	1
1	1	Qt'


J=S	K=R	Q+
0	0	Qt
0	1	0
1	0	1
1	1	Qt'

 

Toggle Flip-Flop: T FF

- $J=K=1$, $Q^+ = Q'$

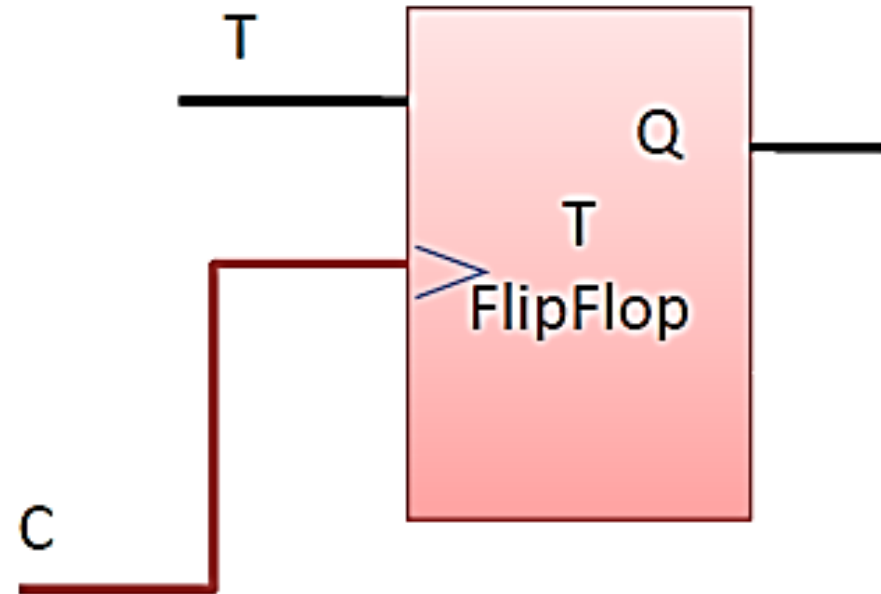 

 

4 Types of Flip-Flops

S	R	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	U




D	Q+
0	0
1	1

J	K	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '




T	Q+
0	Q _t
1	Q _t '

 

Characteristic Equations

 - A descriptions of the next-state table of a flip-flop
- Constructing from the Karnaugh map for Q_{t+1} in terms of the present state and input




Characteristic tables

- The tables that we've made so far are called **characteristic tables**.
 - They show the next state $Q(t+1)$ in terms of the current state $Q(t)$ and the inputs.
 - For simplicity, the control input C is not usually listed.
 - Again, these tables don't indicate the positive edge-triggered behavior of the flip-flops that we'll be using.

J	K	$Q+$
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

D	$Q+$
0	0
1	1

T	$Q+$
0	Q_t
1	Q_t'

 


Characteristic equations

- We can also write **characteristic equations**, where the next state $Q(t+1)$ is defined in terms of the current state $Q(t)$ and inputs.

J	K	Q^+
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

$$Q^+ = K'Q + JQ'$$

$$Q(t+1) = K'Q(t) + JQ'(t)$$

 

Characteristic equations

- We can also write **characteristic equations**, where the next state $Q(t+1)$ is defined in terms of the current state $Q(t)$ and inputs.

D	Q^+
0	0
1	1


$$Q^+ = D$$

$$Q(t+1) = D$$

T	Q^+
0	Q_t
1	Q_t'

$$Q^+ = T'Q + TQ' = T \oplus Q$$
 
$$\begin{aligned} Q(t+1) &= T'Q(t) + TQ'(t) \\ &= T \oplus Q(t) \end{aligned}$$




Characteristic equations


		SR			
		00	01	11	10
Q	0	0	0	-	1
	1	1	0	-	1



$$Q^+ = S + R'Q \quad (SR=0)$$


Flip Flop Type	Characteristic Equation
SR	$Q^+ = S + R'Q \quad (SR=0)$
JK	$Q^+ = JQ' + K'Q$
D	$Q^+ = D$
T	$Q^+ = TQ' + T'Q = T \oplus Q$

 


Shift Register

 


  

 



Shift Register

 


 



Shift Register

 


 


Example

  

 


Example

  

Hold time

Setup time

Maximum CLK Rate
or
Maximum Frequency

 


1-SR-FF


2-D-FF

3-T-FF


4-JK-MS-FF

 

SHIFT REGISTERS

 

Shift Right

 


High to Low Edge




Low to High Edge




Effective Edge

 


Shift Right

 


Shift Left

 

 


Shift Right and Left


X	
0	Shift_Right
1	Shift_Left

 

Shift Right and Left


X	
0	Shift_Right
1	Shift_Left

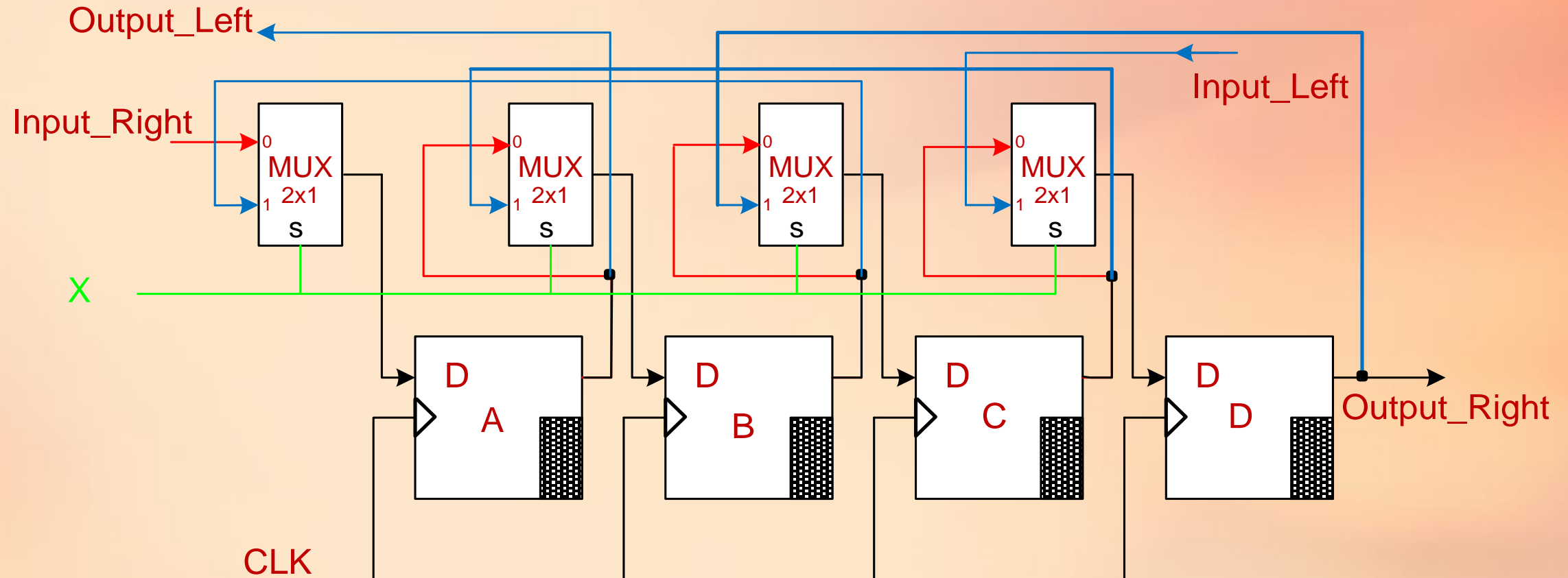


 

Shift Right and Left


X	
0	Shift_Right
1	Shift_Left

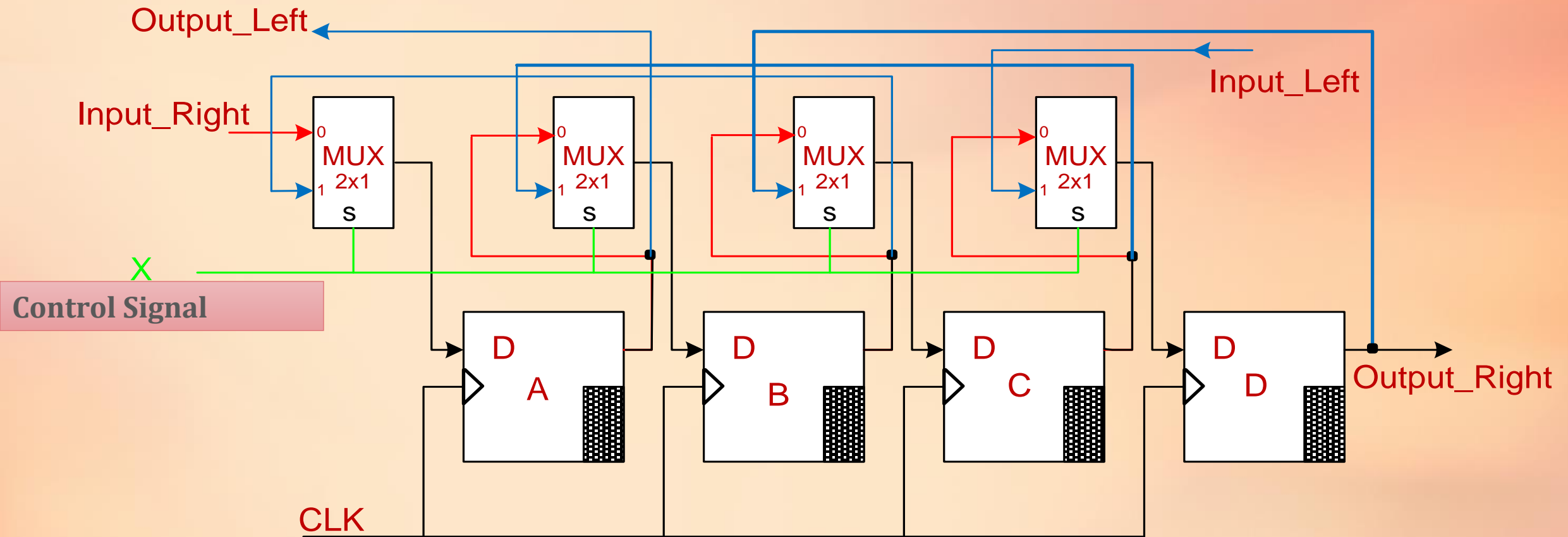

 


☐ **Parallel Load**
(with Asynchronous inputs)

 
☐ **Parallel Load**
(with Synchronous inputs)




□ Parallel Load (Asynchronous pins)

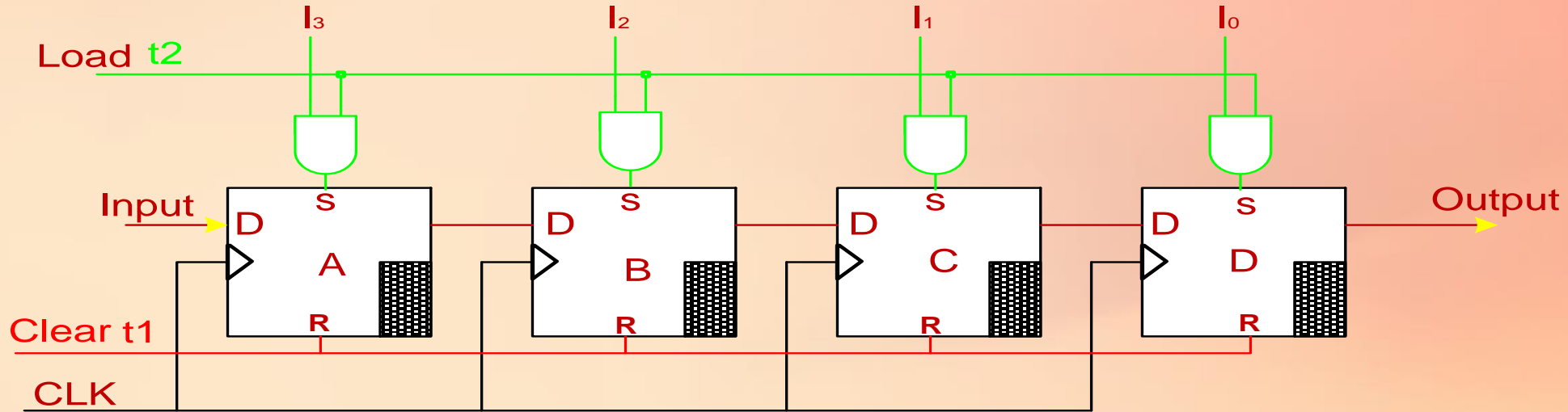

 
S: Preset , Primary Set
R: Clear , Primary Reset




□ Parallel Load (Asynchronous pins)

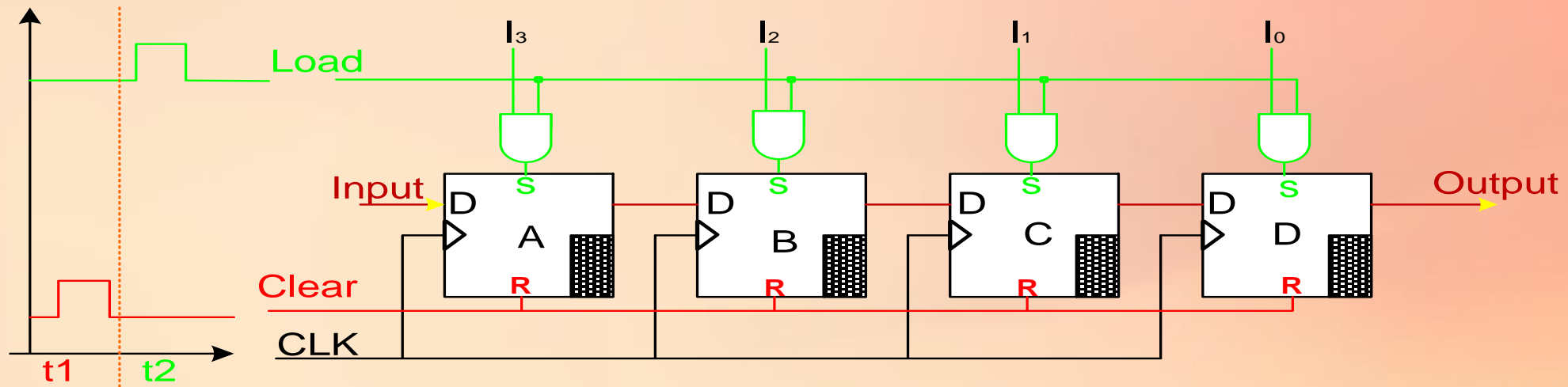


 S: Preset , Primary Set
R: Clear , Primary Reset




□ Parallel Load (Synchronous pins)

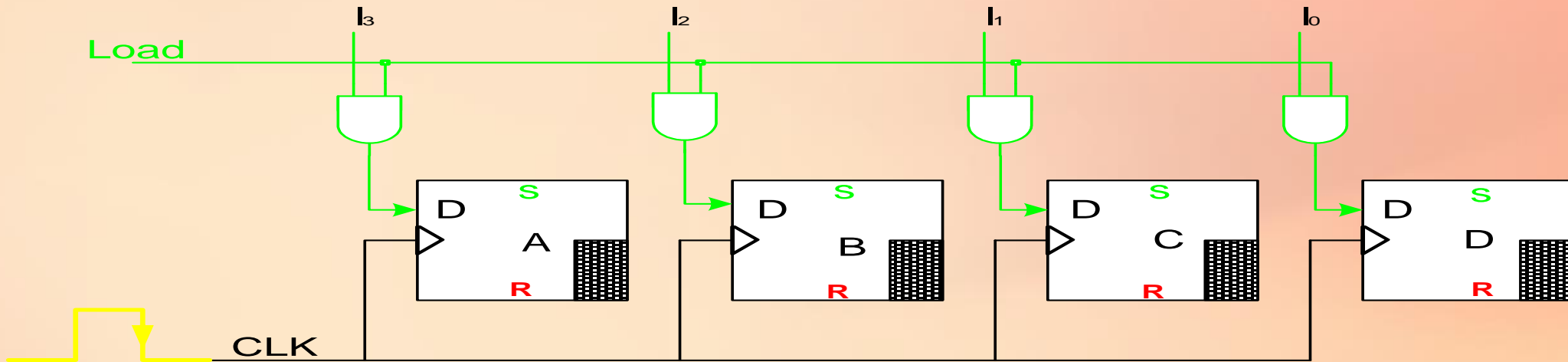



 



❑ Parallel Load (Asynchronous pins)

 


❑ Parallel Load (Synchronous pins)

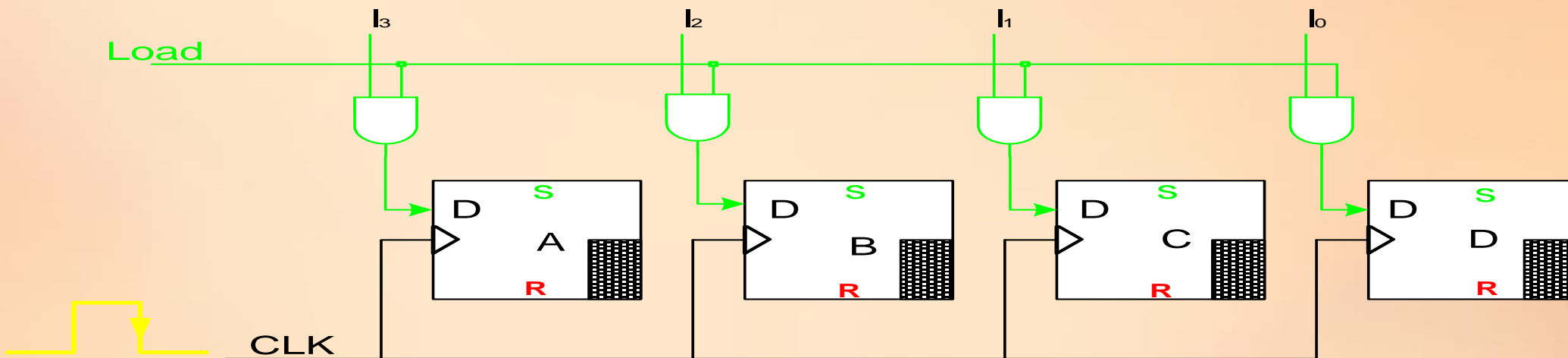


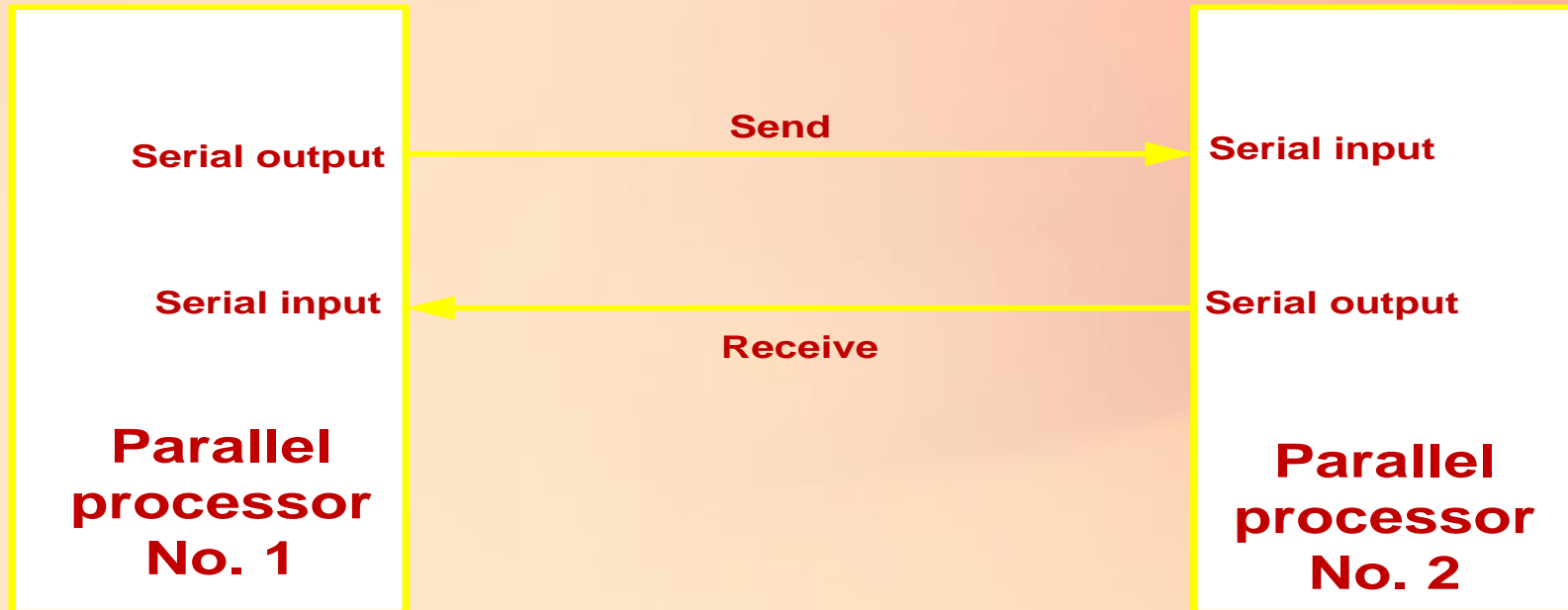 


 


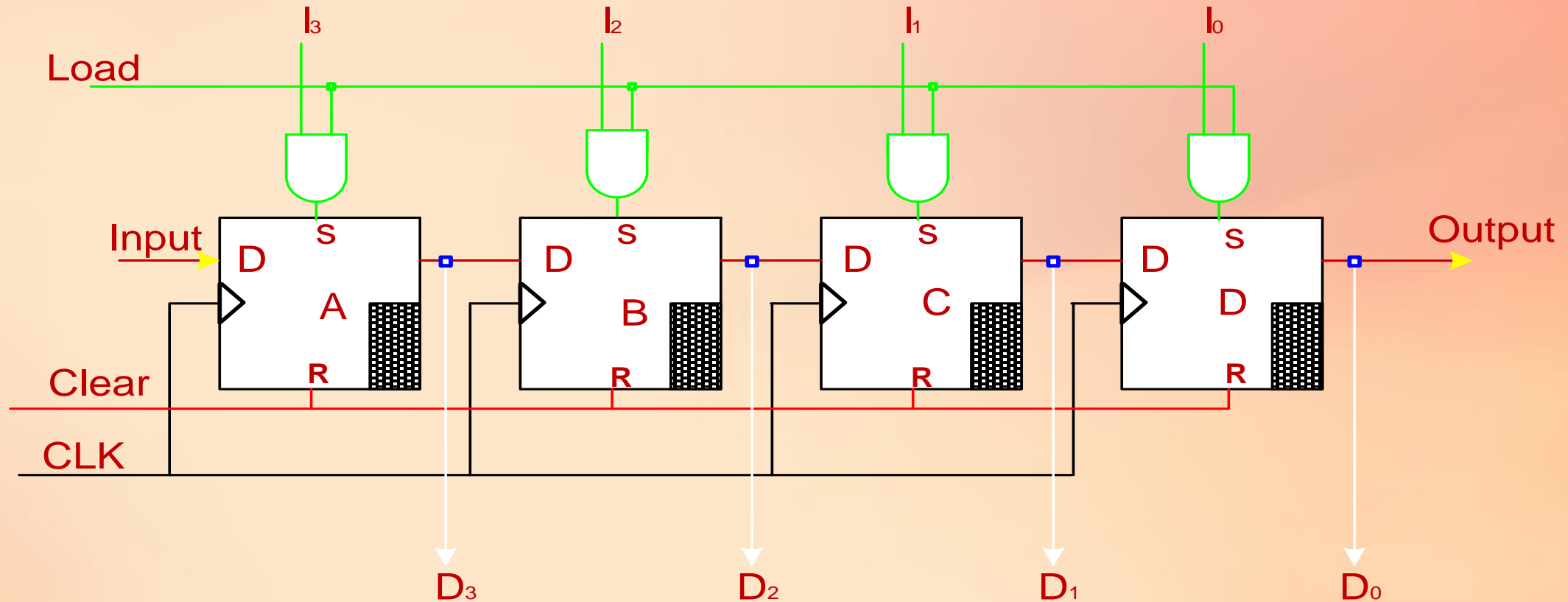
Serial to parallel & Parallel to serial convertor



 



Parallel to serial convertor

 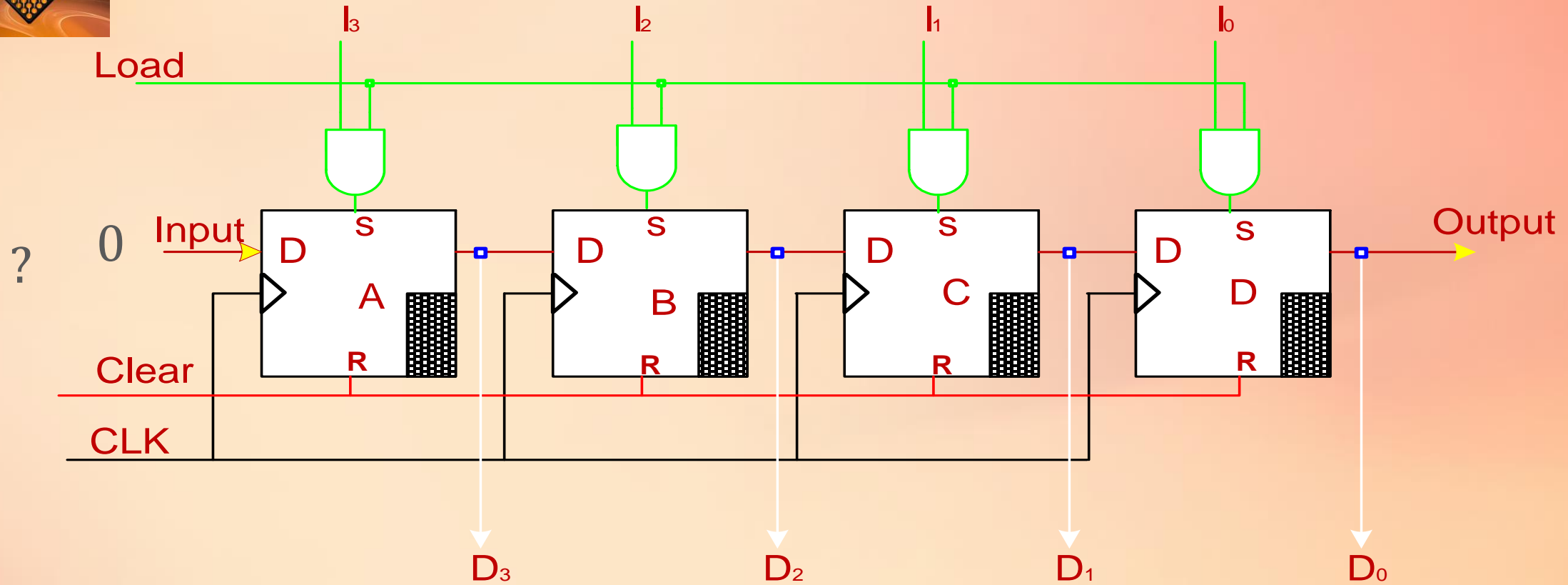

 



Serial to parallel convertor

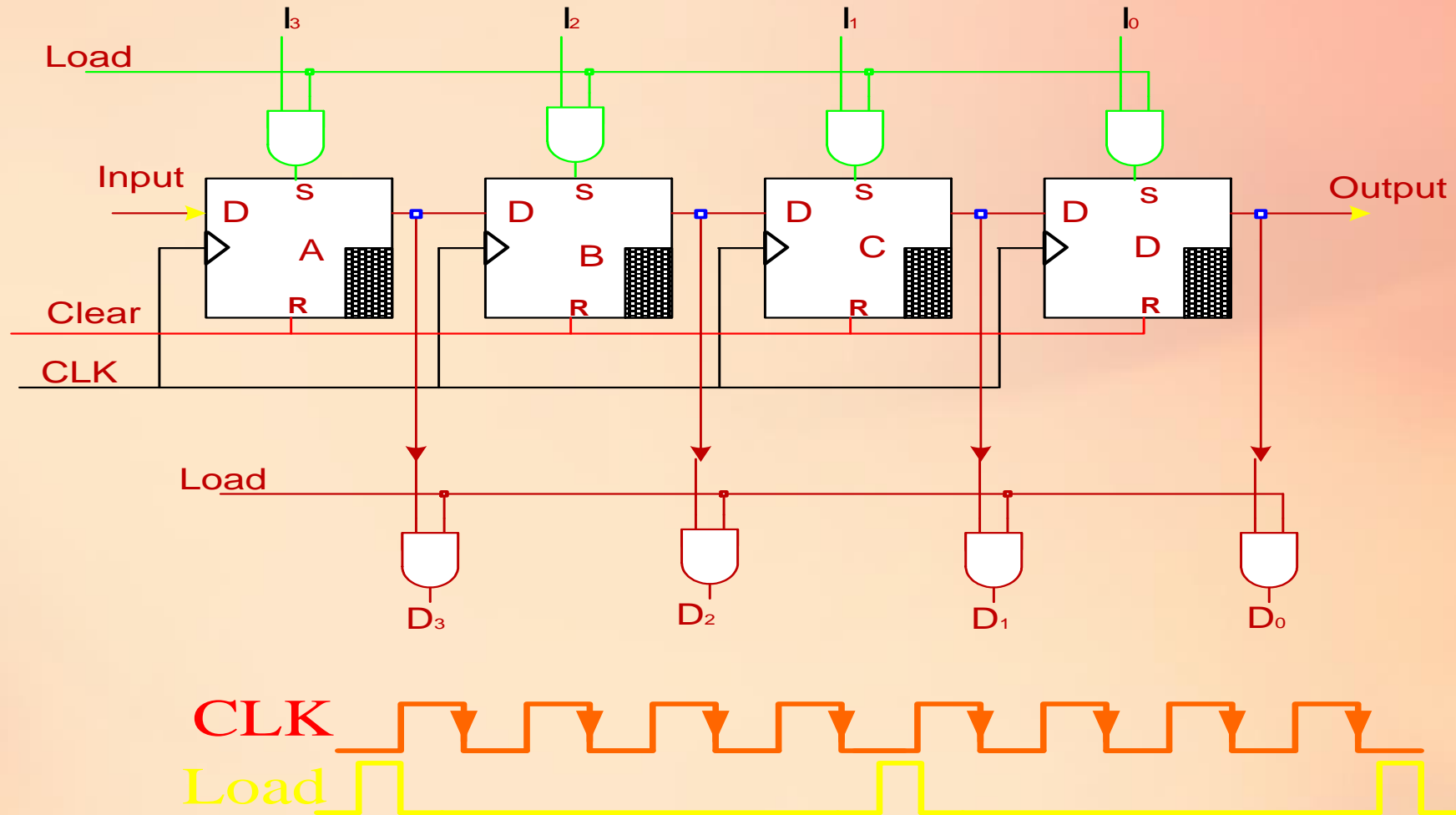


 


Buffer

 


 



Buffer

  


T1

 

Buffer

 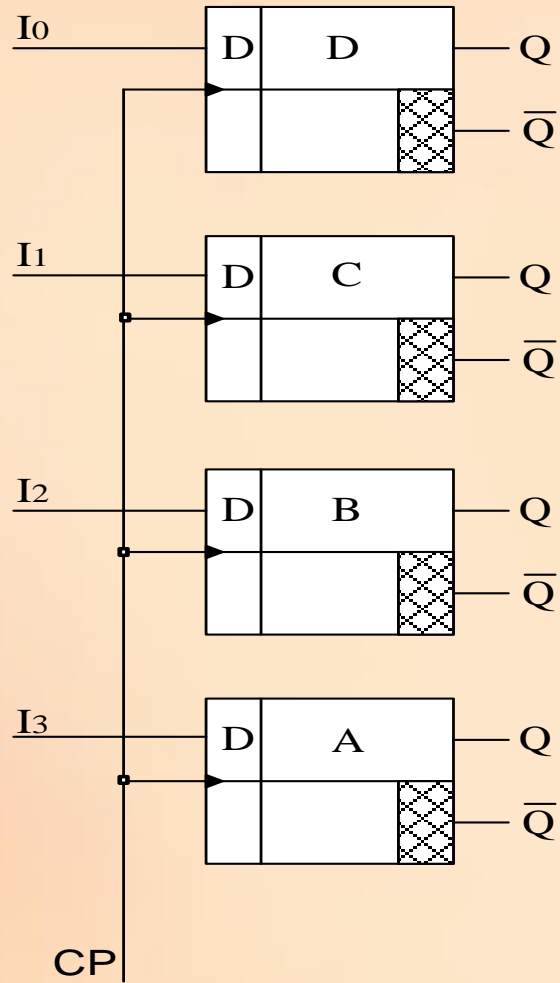

T1

 

T2



THANK YOU