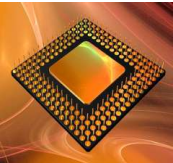


Modern Digital System Design

ECE 2372 / Fall 2018 / Lecture 02

Texas Tech University
Dr. Tooraj Nikoubin

Logic Gates and Boolean Algebra



Logic Functions




- Logical functions can be expressed in several ways:


- * Truth table
- * Logical expressions
- * Graphical form

Logical Equivalence

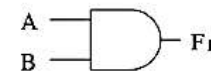
- All three circuits implement $F = A B$ function




(a)

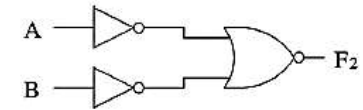

(b)

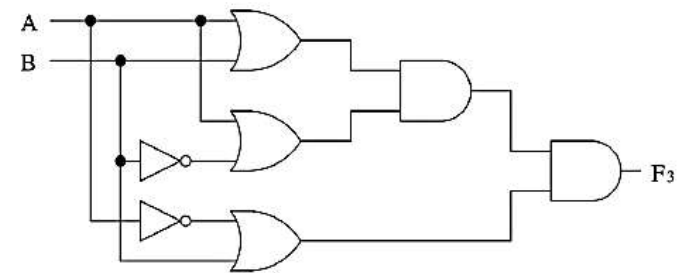


(c)

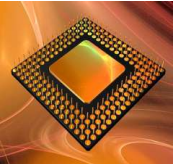

Boolean Algebra






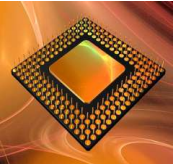
- Computer hardware using binary circuit greatly simplify design
- Binary circuits: To have a conceptual framework to manipulate the circuits algebraically
- George Boole (1813-1864): developed a mathematical structure
 - To deal with binary operations with just two values.



Basic Gates in Binary Circuit

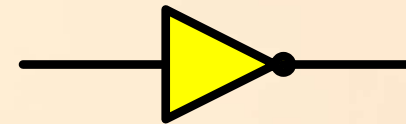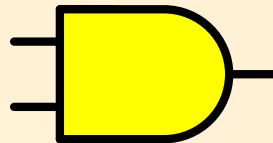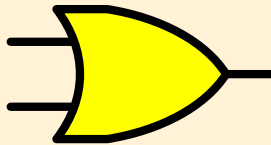
- Element **0** : “FALSE”. Element **1** : “TRUE”.
- ‘+’ operation “OR”, ‘*’ operation “AND” and ‘ ’ operation “NOT”.



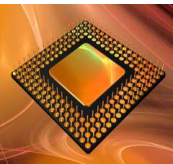

AND Gate


- ‘*’ operation “AND”

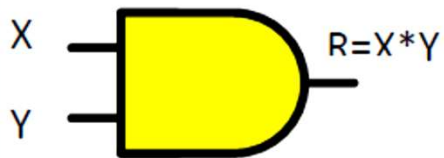

X	Y	R=X AND Y R= X * Y
0	0	0
0	1	0
1	0	0
1	1	1


$$0 * Y = 0$$

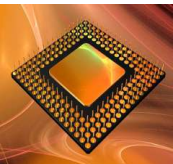One “0” value as a input is enough to set the output “0”



OR Gate


- ‘+’ operation “OR”

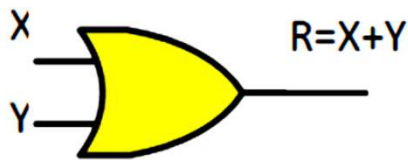

X	Y	R = X OR Y R = X + Y
0	0	0
0	1	1
1	0	1
1	1	1


$$1 + Y = 1$$

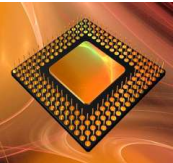One “1” value as a input is enough to set the output “1”




NOT Gate (Inverter)

- ‘ operation “NOT”

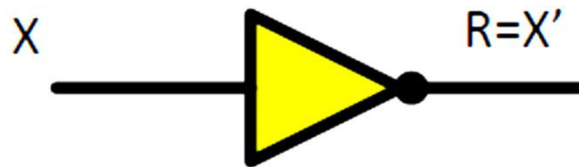


X	R=X' R= NOT X
0	1
1	0

$$Y = \overline{A} = A'$$

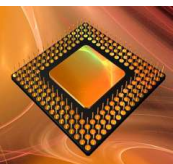


Logic Gates: NAND, NOR

- NAND

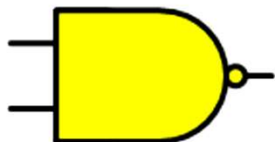


A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

- NOR

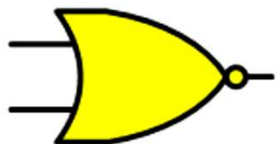


A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

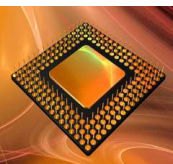


Logic Gates: XOR, XNOR

- XOR

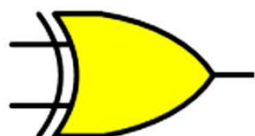

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0


- XNOR

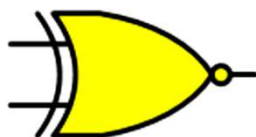

A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

XOR: Exclusive OR

XNOR: Exclusive NOR

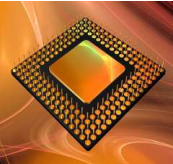

Boolean Algebra Defined




Boolean Algebra B : 5-tuple

$$\{ +, *, ', 0, 1 \}$$

$+$ and $*$ are *binary* operators,

$'$ is a *unary* operator.

$$Y = \overline{A} = A'$$

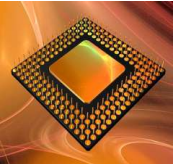

Boolean Algebra Defined



- ***Axiom #1: Closure***

If a and b are Boolean

$(a + b)$ and $(a * b)$ are Boolean.


- ***Axiom #2: Cardinality***

if a is Boolean then a' is Boolean

- ***Axiom #3: Commutative***

$$(a + b) = (b + a)$$

$$(a * b) = (b * a)$$

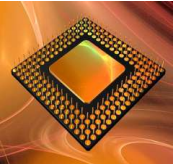

Boolean Algebra Defined



• **Axiom #4: Associative : If a and b are Boolean**

$$(a + b) + c = a + (b + c)$$


$$(a * b) * c = a * (b * c)$$

• **Axiom #5: Distributive**

$$a * (b + c) = (a * b) + (a * c)$$

$$a + (b * c) = (a + b) * (a + c)$$

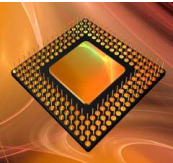2nd one is Not True for Decimal numbers System



Boolean Algebra Defined

- ***Axiom #6: Identity Element :***

B has identity to + and *


0 is identity element for + : $a + 0 = a$

1 is identity element for * : $a * 1 = a$

- ***Axiom #7: Complement Element***

$$a + a' = 1$$

$$a * a' = 0$$

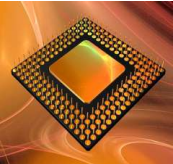

Terminology

- Juxtaposition implies * operation:


$$ab = a * b = a.b$$

- Operator order of precedence is:

$$() > ' > * > +$$


$$a+bc = a+(b*c) \neq (a+b)*c$$

$$ab' = a(b') \neq (a*b)'$$

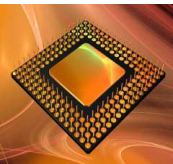

Named Theorems

Idempotent	$a + a = a$	$a * a = a$
Boundedness	$a + 1 = 1$	$a * 0 = 0$
Absorption	$a + (a * b) = a$	$a * (a + b) = a$
Associative	$(a + b) + c =$ $a + (b + c)$	$(a * b) * c =$ $a * (b * c)$
Involution	$(a')' = a$	
DeMorgan's	$(a + b)' = a' * b'$	$(a * b)' = a' + b'$

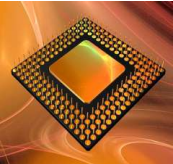

Logical Expression Simplification

- Three basic methods

- * **Algebraic manipulation**


- » Use Boolean laws to simplify the expression
 - Difficult to use
 - Don't know if you have the simplified form

- * **Karnaugh map method**

- » Graphical method
 - » Easy to use
 - Can be used to simplify logical expressions with a few variables

- * **Quine-McCluskey method**

- » Tabular method
 - » Can be automated

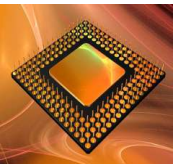

Simplification Theorem

- Uniting :

$$XY + XY' = X$$

$$X(Y+Y')=X.1=X$$

$$(X + Y)(X + Y') = X$$

$$XX+XY'+YX+YY'=X+X(Y+Y')+0=X$$

- Absorption:

$$X + XY = X$$

$$X(1+Y)=X.1=X$$


$$X(X + Y) = X$$

$$XX+XY=X+XY=X$$

- Adsorption

$$(X + Y')Y = XY, \quad XY' + Y = X + Y$$

$$XY+YY'=XY+0=XY$$

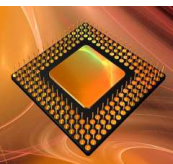

N-bit Boolean Algebra

Single bit to *n-bit* Boolean Algebra

Let $a = 1101010$, $b = 1011011$

$$a + b = 1101010 + 1011011$$


$$\begin{array}{r} a + b = 1101010 + \\ 1011011 \\ \hline 1111011 \end{array}$$

$$a * b = 1101010 * 1011011$$

$$\begin{array}{r} a * b = 1101010 * \\ 1011011 \\ \hline 1001010 \end{array}$$

$$a' = 1101010' = 0010101$$
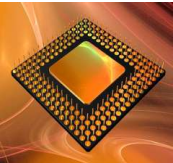
$$\begin{array}{r} a' = 1101010' \\ \hline 0010101 \end{array}$$



Proof by Truth Table

- Consider the distributive theorem:

$$a + (b * c) = (a + b) * (a + c)$$


Is it true for a two bit Boolean Algebra?

- Can prove using a truth table

–How many possible combinations of a , b , and c are there?

- Three variables, each with two values


$$-2 * 2 * 2 = 2^3 = 8$$

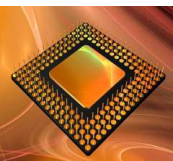

Proof by Truth Table

a	b	c	$b * c$	$a + (b * c)$	$a + b$	$a + c$	$(a + b) * (a + c)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

$$a + (b * c) = (a + b) * (a + c)$$

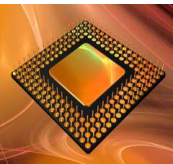


Proof using Theorems

Use the properties of Boolean Algebra to proof

$$(x + y)(x + x) = x$$

Warning, make sure you use the laws precisely

$(x + y)(x + x)$	Given
$(x + y)x$	Idempotent
$x(x + y)$	Commutative
x	Absorption

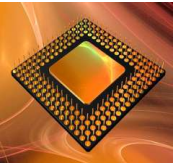

Converting to Boolean Equations

Convert the following English statements to a Boolean a equation

– **Q1. a is 1 and b is 1.**

Answer: $F = a \text{ AND } b = ab$

– **Q2. either of a or b is 1.**

Answer: $F = a \text{ OR } b = a+b$

– **Q3. both a and b are not 0.**


Answer:

– (a) Option 1: $F = \text{NOT}(a) \text{ AND } \text{NOT}(b) = a'b'$

– (b) Option 2: $F = a \text{ OR } b = a+b$

– **Q4. a is 1 and b is 0.**

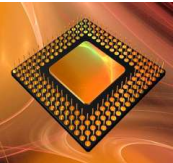Answer: $F = a \text{ AND } \text{NOT}(b) = ab'$



Complete sets

- * A set of gates is complete


- » if we can implement any logical function using only the type of gates in the set
 - You can use as many gates as you want

- * Some example complete sets

- » {AND, OR, NOT} ← Not a minimal complete set
- » {AND, NOT}
- » {OR, NOT}
- » {NAND}
- » {NOR}

- * Minimal complete set


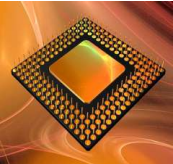
- A complete set with no redundant elements.



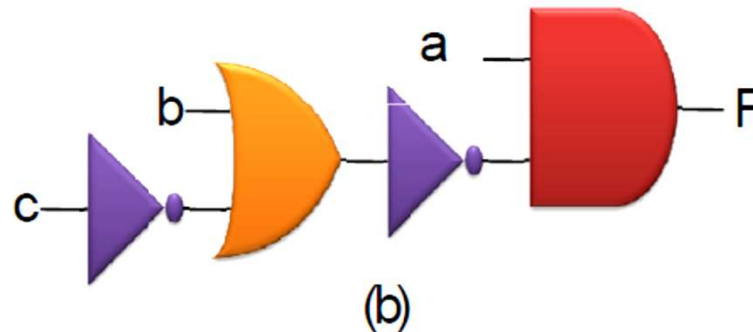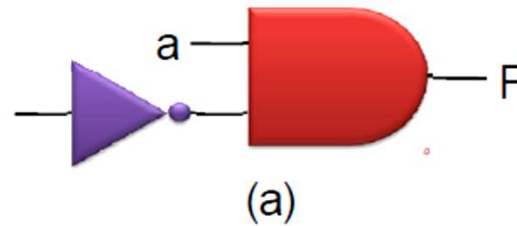Example: Converting a Boolean Equation to a Circuit of Logic Gates


Q: Convert the following equation to logic gates:


$$F = a \text{ AND NOT}(b \text{ OR NOT}(c))$$





Some Circuit Drawing Conventions

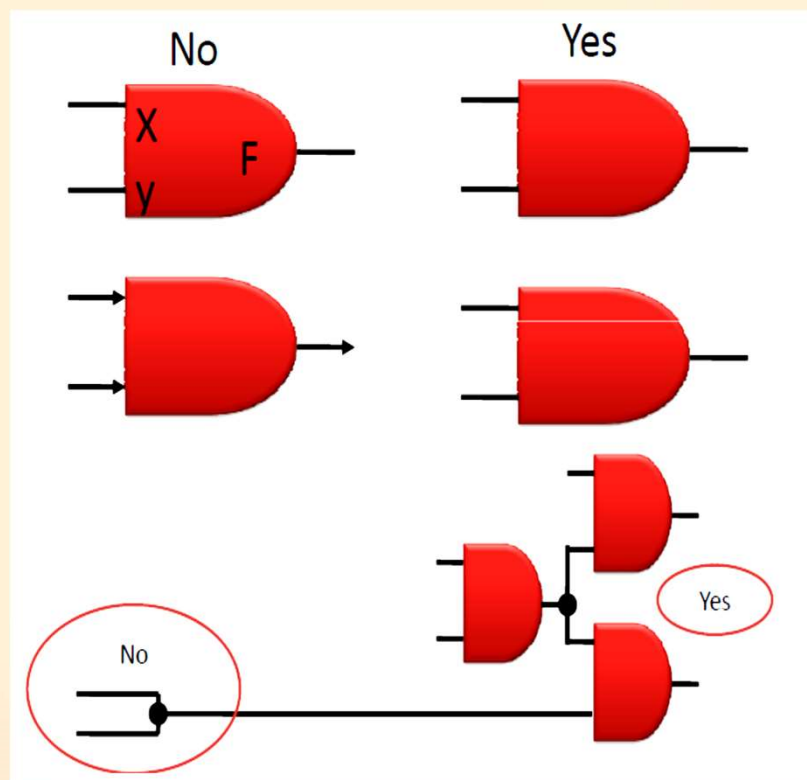

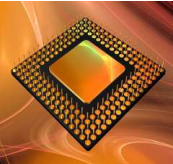

Duality examples



$$x + 0 = x$$

$$x + x' = 1$$

$$A + B'C$$


$$A'B' + AB$$

$$x.1 = x$$

$$x . x' = 0$$

$$A. (B'+C)$$

$$(A'+B').(A+B)$$

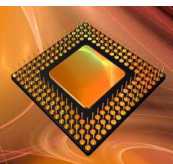



NAND & NOR are universal




$$(xx)' = x'$$

$$((xy)')' = xy$$

$$(x'y')' = x+y$$

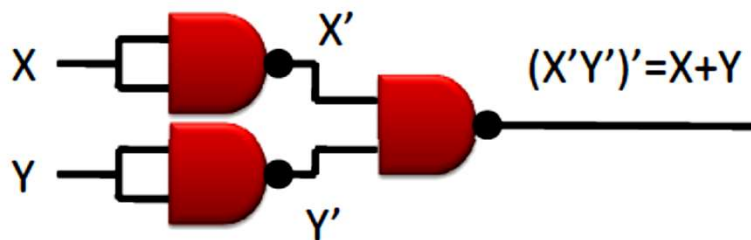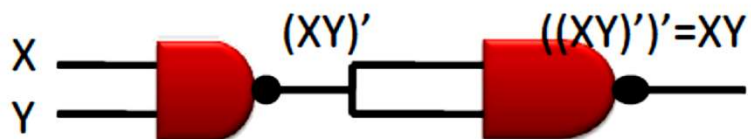

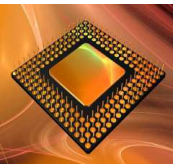




NAND & NOR are universal




$$(x+x)' = x'$$



$$((x+y)')' = x+y$$


$$(x'+y')' = x.y$$

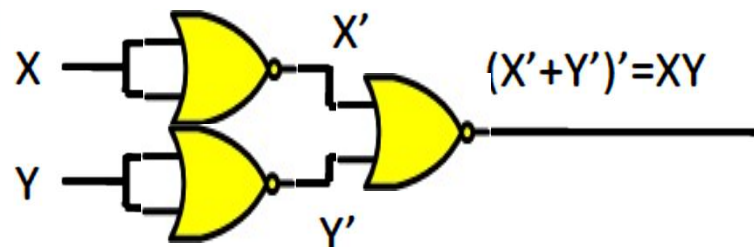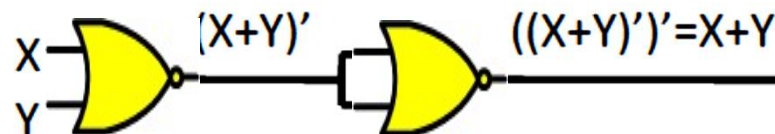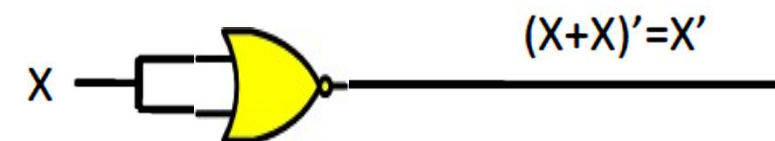




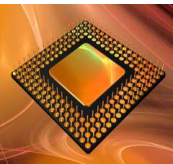


Multi-input gate

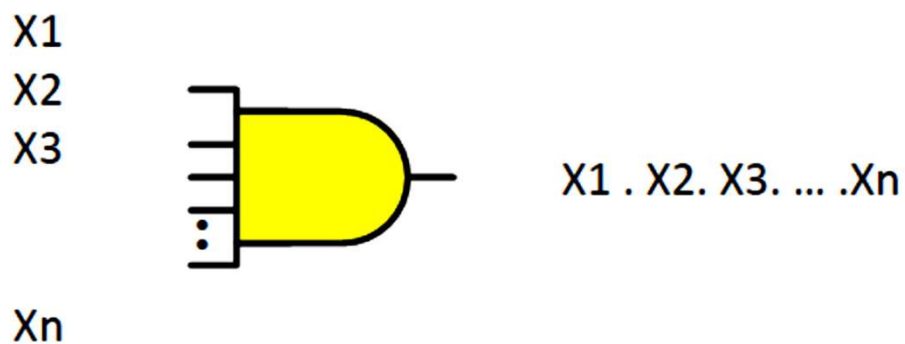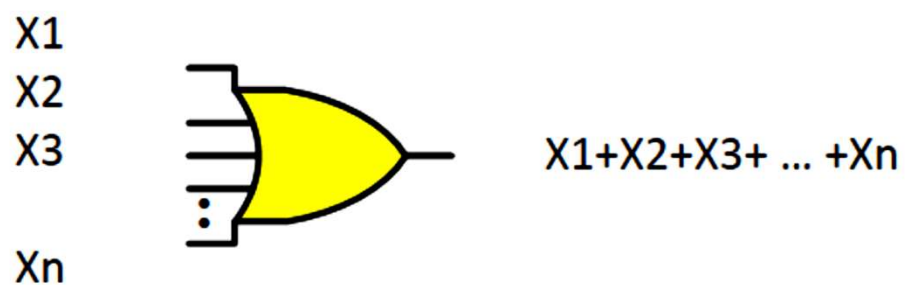


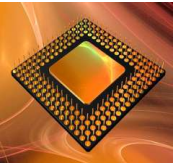

Effect of 0 & 1 on logic gates

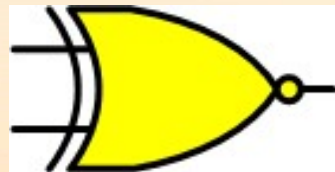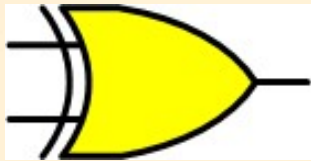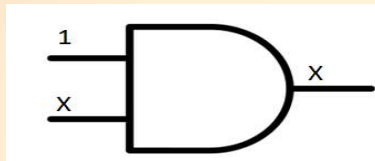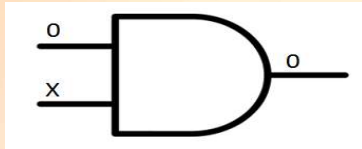

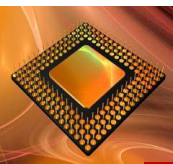0 & 1
for OR Logic Gates
for AND Logic Gates
for XOR Logic Gates
for XNOR Logic Gates



Canonical form or Standard Form



- Canonical forms

- Sum of minterms (SOM)
- Product of maxterms (POM)

- Standard forms (may use less gates)


- Sum of products (SOP)
- Product of sums (POS)

Example : 3 –Input Majority Function

$F = ab + a'$ (already sum of products : SOP)

$F = ab + a'(b + b')$ (expanding term)

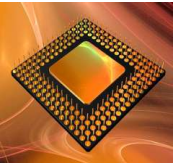$F = ab + a'b + a'b'$ (it is canonical form : SOM)



Shannon Expansion



- $F(X, Y, Z) = X \cdot F(1, Y, Z) + X' \cdot F(0, Y, Z)$

Example:

$$XY + X'Z + YZ$$


$$= X \cdot (1 \cdot Y + 0 \cdot Z + YZ) + X' \cdot (0 \cdot Y + 1 \cdot Z + YZ)$$

$$= X \cdot (Y + YZ) + X' \cdot (Z + YZ)$$

$$= X \cdot (Y(1 + Z)) + X' \cdot (Z(1 + Y))$$

$$= X(Y \cdot 1) + X'(Z \cdot 1)$$

$$= XY + X'Z$$

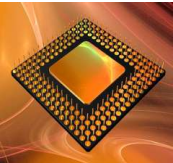

Consensus Theorem


- $XY + X'Z + YZ = XY + X'Z$

$$\begin{aligned} &XY + X'Z + YZ \\ &= xy + x'z + (x + x')yz \\ &= xy + x'z + xyz + x'yz \\ &= xy + xyz + x'z + x'yz \\ &= xy(1 + z) + x'z(1 + y) \\ &= xy + x'z \end{aligned}$$

Consensus (collective opinion) of $X.Y$ and $X'.Z$ is $Y.Z$

- $(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$


Duality

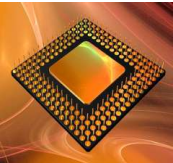

Principle of Duality




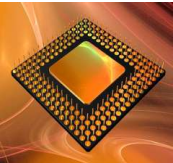
- Dual of a statement S is obtained
 - By interchanging * and +
 - By interchanging 0 and 1
- Dual of $(a*1)*(0+a') = 0$ is $(a+0)+(1*a') = 1$



Basic building block:

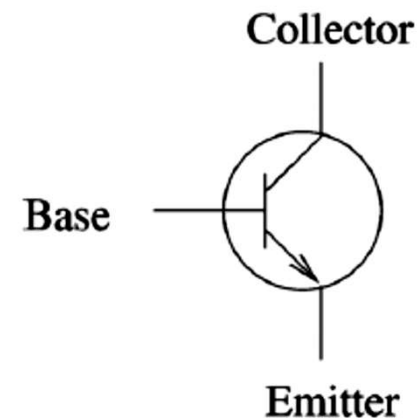
- » Transistor
- Three connection points
 - * Base
 - * Emitter
 - * Collector
- Transistor can operate
 - * Linear mode
 - » Used in amplifiers
 - * Switching mode
 - » Used to implement digital circuits




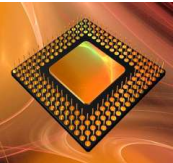

Basic building block:


Logic Chips

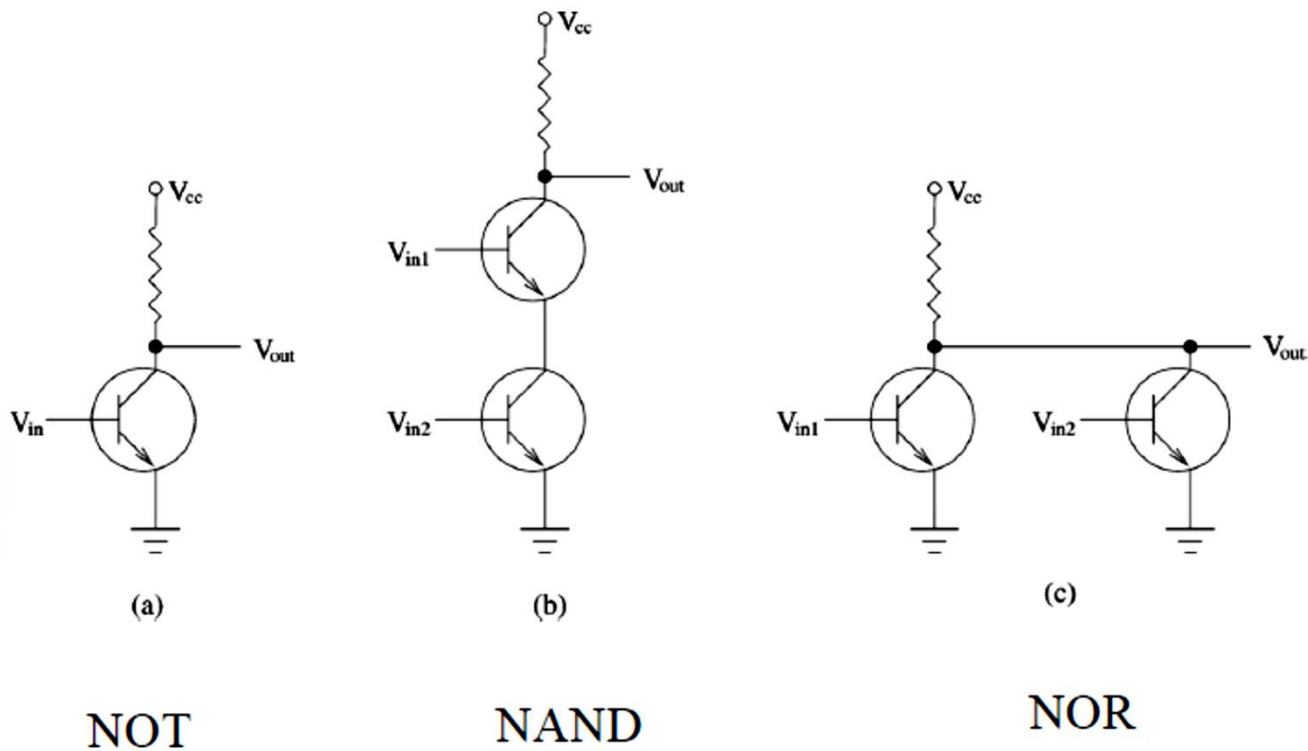


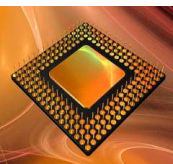

Level of voltages for Low and High

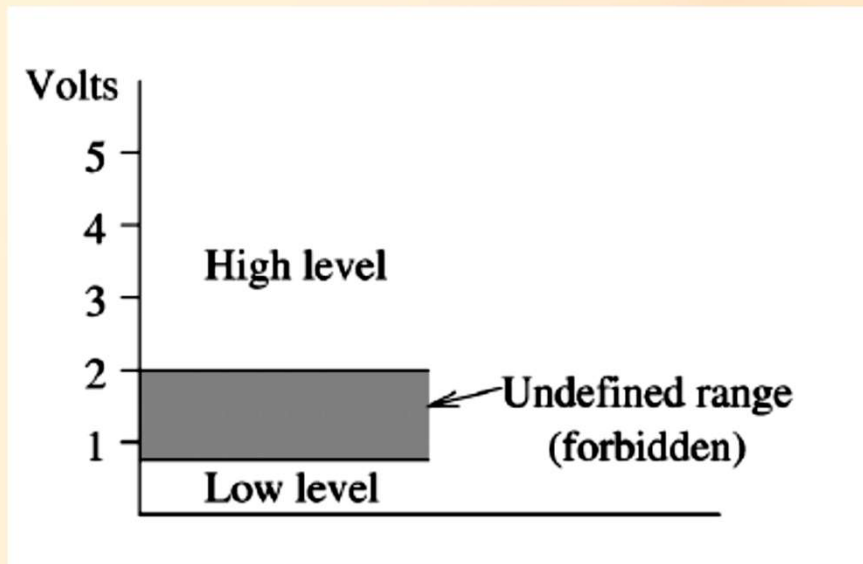
- Low voltage level: $< 0.4V$
- High voltage level: $> 2.4V$
- Positive logic:
 - * Low voltage represents 0
 - * High voltage represents 1
- Negative logic:
 - * High voltage represents 0
 - * Low voltage represents 1
- Propagation delay
 - * Delay from input to output
 - * Typical value: 5-10 ns



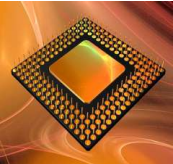


Integration levels

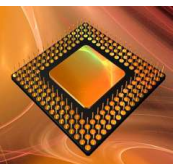- * SSI (small scale integration)
 - » Introduced in late 1960s
 - » 1-10 gates (previous examples)
- * MSI (medium scale integration)
 - » Introduced in late 1960s
 - » 10-100 gates
- * LSI (large scale integration)
 - » Introduced in early 1970s
 - » 100-10,000 gates
- * VLSI (very large scale integration)
 - » Introduced in late 1970s
 - » More than 10,000 gates




Logic Chips (SSI)

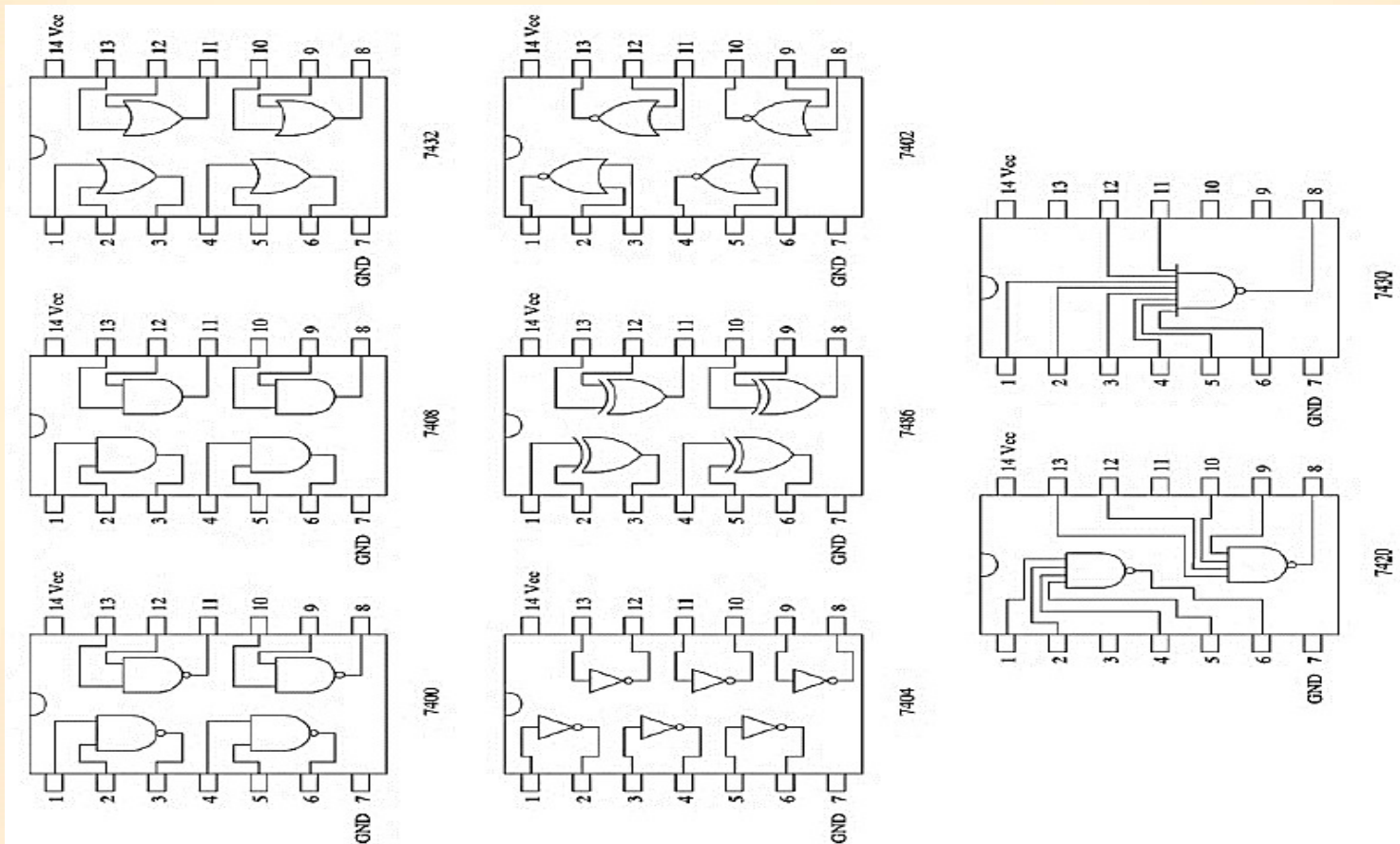

SSI: small scale integration

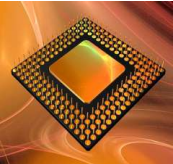
ECE 2372 / Dr. Tooraj Nikoubin / Fall 2018 / Lecture 2 / Logic Gates & Boolean Algebra



Review



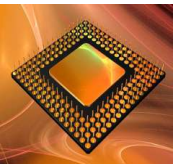1. $A_1 \cdot (A_1 + A_2) = A_1$
2. $A_1 \cdot (A_1' + A_2) = A_1 \cdot A_2$
3. $A_1 + (A_1' \cdot A_2) = A_1 + A_2$
4. $A_1 \cdot A_2 + (A_1 \cdot A_2') = A_1$
5. $(A_1 + A_2) \cdot (A_1 + A_2') = A_1$




Review



$0 \cdot 0 = 0$	$X \cdot X = X$
$0 \cdot 1 = 0$	$X \cdot X' = 0$
$1 \cdot 0 = 0$	$X' \cdot X = 0$
$1 \cdot 1 = 1$	$X' \cdot X' = X'$

$0 + 0 = 0$	$X + X = X$
$0 + 1 = 1$	$X + X' = 1$
$1 + 0 = 1$	$X' + X = 1$
$1 + 1 = 1$	$X' + X' = X'$

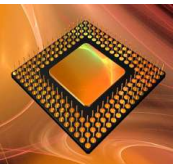

Review




1. $\overline{A + B} = \bar{A} \cdot \bar{B}$

2. $\overline{\bar{Y}} = Y$

3. $\overline{A \cdot B} = \bar{A} + \bar{B}$

$$\overline{AC + \bar{B}D} = \bar{A}\bar{C} \cdot (\bar{B}D)$$

$0 \cdot X = 0$	$0 + X = X$
$0 \cdot X' = 0$	$0 + X' = X'$
$1 \cdot X = X$	$1 + X = 1$
$1 \cdot X' = X'$	$1 + X' = 1$

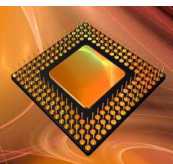


Review



Boolean Algebra

<u>Boolean identities</u>		
Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \overline{x} = 0$	$x + \overline{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) =$ $(x + y)(x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

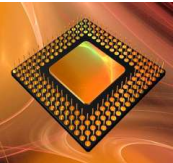


Review



Boolean Algebra (cont'd)

- Boolean identities (cont'd)

Name	AND version	OR version
Involution	$\overline{\overline{x}} = x$	---
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) =$ $(x + y) + z$
de Morgan	$\overline{x \cdot y} = \overline{x} + \overline{y}$	$\overline{x + y} = \overline{x} \cdot \overline{y}$

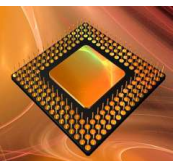

Laws and Theorems of Boolean Algebra



Operations with 0 and 1:

1. $X + 0 = X$

2. $X + 1 = 1$

Idempotent laws:

3. $X + X = X$

Involution law:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

Commutative laws:

6. $X + Y = Y + X$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

1D. $X \cdot 1 = X$

2D. $X \cdot 0 = 0$

3D. $X \cdot X = X$

5D. $X \cdot X' = 0$

6D. $XY = YX$

7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

8D. $X + YZ = (X + Y)(X + Z)$

Simplification theorems:

9. $XY + XY' = X$

9D. $(X + Y)(X + Y') = X$

10. $X + XY = X$

10D. $X(X + Y) = X$

11. $(X + Y')Y = XY$

11D. $XY' + Y = X + Y$

DeMorgan's laws:

12. $(X + Y + Z + \dots)' = X'Y'Z' \dots$

12D. $(XYZ \dots)' = X' + Y' + Z' + \dots$

Duality:

13. $(X + Y + Z + \dots)^D = XYZ \dots$

13D. $(XYZ \dots)^D = X + Y + Z + \dots$

Theorem for multiplying out and factoring:


14. $(X + Y)(X' + Z) = XZ + X'Y$

14D. $XY + X'Z = (X + Z)(X' + Y)$

Consensus theorem:

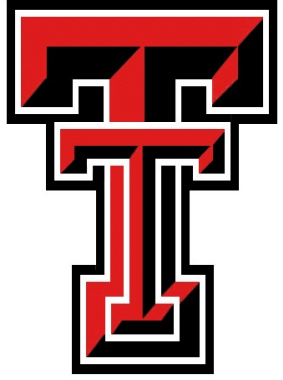15. $XY + YZ + X'Z = XY + X'Z$

15D. $(X + Y)(Y + Z)(X' + Z)$
 $= (X + Y)(X' + Z)$



Thank You