



# Modern Digital System Design

## ECE 2372 SECOND TEST

Texas Tech University  
ECE Department  
Dr. Tooraj Nikoubin

Spring 04/11/2016

**First Name:** .....

**Last Name:** .....

**R#:** .....

« 1 » **a)** Use a 8 to 1 multiplexer and a minimum number of external gates to realize the following function.

**b)** Use a 4 to 1 multiplexer and a minimum number of external gates to realize the following function.

$$Q = F(w, x, y, z) = \sum_m(0, 3, 4, 5, 7, 8, 10, 14) + \sum_d(2, 6, 11)$$


« 2 » **a)** Implement a full adder using one 3 to 8 decoder active high outputs and minimum logic gates. **b)** Implement a full adder using one 3 to 8 decoder with active low outputs and minimum logic gates.

- « 3 » **a)** Implement a 8 to 1 multiplexer with 4 to 1 multiplexers.
- b)** Implement a 4 to 16 decoder with 2 to 4 decoders with enable input.


« 4 » **a)** Implement a 12bit binary adder with 4-bit binary adder blocks.

**b)** Implement a comparator for two 2-bit binary numbers with 4-bit Adder block.


 
« 5 » Find the Minterm numbers and output function of following circuit.



 B) Find the Maxterm numbers and the output function for following circuit.



  « 6 » Find the output Functions for Following circuits:



« 7 » **a)** Design one digit BCD adder, with 4-bit binary adder blocks and logic gates.

**b)** Implement one bit full adder with suitable PLA.



GOOD LUCK





# Modern Digital System Design

## ECE 2372 SECOND TEST

Texas Tech University  
ECE Department  
Dr. Tooraj Nikoubin

Fall 10/24/2016

**First Name:** .....

**Last Name:** .....

**R#:** .....

« 1 » **a)** Use a 4 to 1 multiplexer and a minimum number of external gates to realize the following function.

**b)** Use a 8 to 1 multiplexer and a minimum number of external gates to realize the following function.

$$Q = F(w, x, y, z) = \sum_m(0, 1, 5, 7, 8, 9, 11, 12, 14) + \sum_d(2, 6)$$

« 2 » **a)** Implement following functions (Q1, Q2 & Q3) using one 3 to 8 decoder active high outputs and minimum logic gates. **b)** Implement following functions (Q1, Q2 & Q3) using one 3 to 8 decoder with active low outputs and minimum logic gates.

$$Q1 = F(x, y, z) = \sum_m(0, 1, 3, 7,)$$

$$Q2 = F(x, y, z) = \sum_m(0, 2, 5, 6,)$$


$$Q3 = F(x, y, z) = \sum_m(1, 4, 5, 7,)$$

- « 3 » **a)** Implement a 16 to1 multiplexer with 4 to 1 multiplexers.
- b)** Implement a 5 to 32 decoder with 3 to 8 decoders with enable input.


« 4 » **a)** Implement a 10bit binary adder with 4-bit binary adder blocks.

**b)** Use circuit (a) to implement a comparator for two 2-bit binary numbers with 6-bit Adder block.  
(Redraw the circuit for this part)

 
« 5 » Find the Minterm numbers and output function of following circuit.



 B) Find the Maxterm numbers and the output function for following circuit.



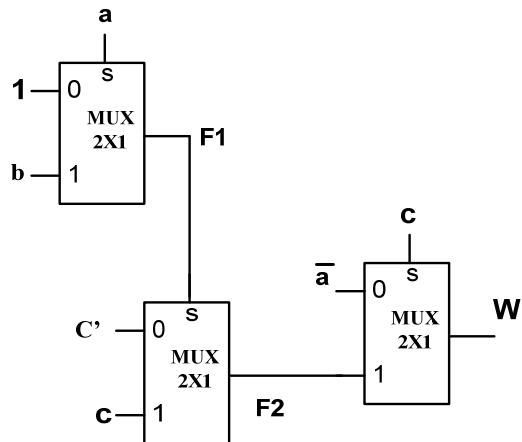« 6 » a) Find the output Functions for Following circuits:



b) Implement the following function using only 2-to-1 MUXes:

$$R = ab' h' + bch' + eg' h + fgh.$$

c) Repeat part (b) using only tri-state buffers.

« 7 » **a)** Design one digit BCD adder, with 4-bit binary adder blocks and logic gates.

**b)** Implement 2-bit full binary adder with suitable PLA. ( $A=a_1a_0$  &  $B=b_1b_0$ )



GOOD LUCK