




Modern Digital System Design

ECE 2372 / Fall 2018 / Lecture 09

Texas Tech University
Dr. Tooraj Nikoubin

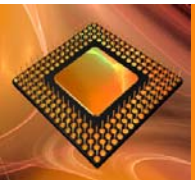
ADD, SUB, Adders, Subtractors &
Comparator, ROM, PLA



Add operation for two bits




0 +		1 +		0 +		1 +	
0		0		1		1	
0	0	0	1	0	1	1	0
C	S	C	S	C	S	C	S

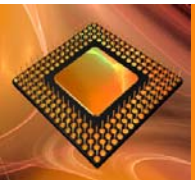

Add operation for two bits




0 +	
0	
0	
0	0
C	S

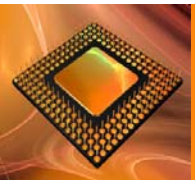

Add operation for two bits




0 +		1 +	
0		0	
0		0	
0	0	0	1
C	S	C	S

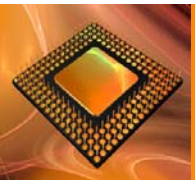

Add operation for two bits




0 +		1 +		0 +	
0		0		1	
0		0		0	
0	0	0	1	0	1
C	S	C	S	C	S

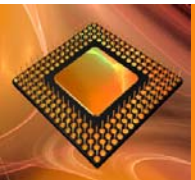

Add operation for two bits




0 +		1 +		0 +		0 +	
0		0		1		0	
0		0		0		1	
0	0	0	1	0	1	0	1
C	S	C	S	C	S	C	S

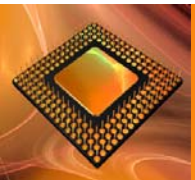

Add operation for three bits




1 +	0 +	1 +	1 +
1	1	0	1
0	1	1	1
1 0	1 0	1 0	1 1
C S	C S	C S	C S

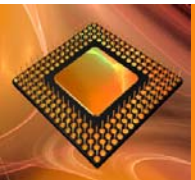

SUB operation for two bits




0 -		1 -		1 0 -		1 -	
0		0		1		1	
0	0	0	1	1	1	0	0
B	D	B	D	B	D	B	D

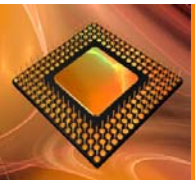

SUB operation for three bits




0 -	1 -	1 0 -	1 -
0	0	0	0
0	0	1	1
0 0	0 1	1 1	0 0
B D	B D	B D	B D

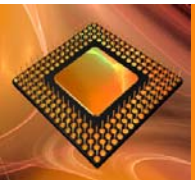

SUB operation for three bits




0	-
1	
1	
B	D

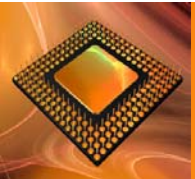

SUB operation for three bits



1	0	-
	1	
	1	
B	D	

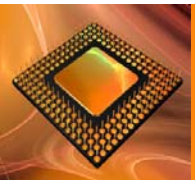


SUB operation for three bits



1	0	-		
	1			
	1			
1	0			
B	D			


	1	-		
	1			
	1			
B	D			

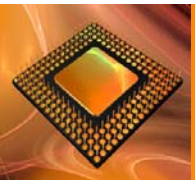

SUB operation for three bits




1	0	-	1	1	-
	1			1	
	1			1	
1	0				
B	D		B	D	

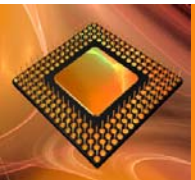


SUB operation for three bits




1	0	-	1	1	-
	1			1	
	1			1	
1	0		1	1	
B	D		B	D	

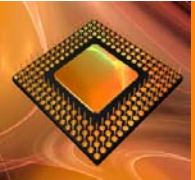

Half Adder

 


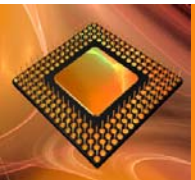

Half Adder




b	a	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

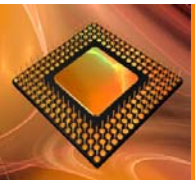



Half Adder




b	a	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 



$$S = a \oplus b$$
$$C = ab$$

  

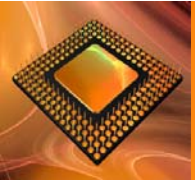

Half Adder

 


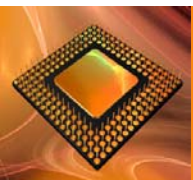


Full Adder



Ci	b	a	C0	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 


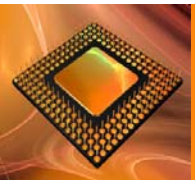

Full Adder




Ci	b	a	C0	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

$$S = \sum m(1,2,4,7)$$

$$C_o = \sum m(3,5,6,7)$$

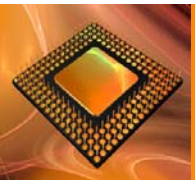

Full Adder



Sum


	A		
b	1		1
		1	
			1
	C _i		


$$S = a \oplus b \oplus C_i$$

Carry


	A		
b		1	1
			1
	C _i		


$$C_o = ab + aC_i + bC_i$$

 

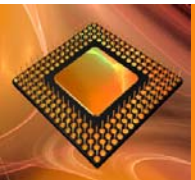



4 Bit Binary Adder

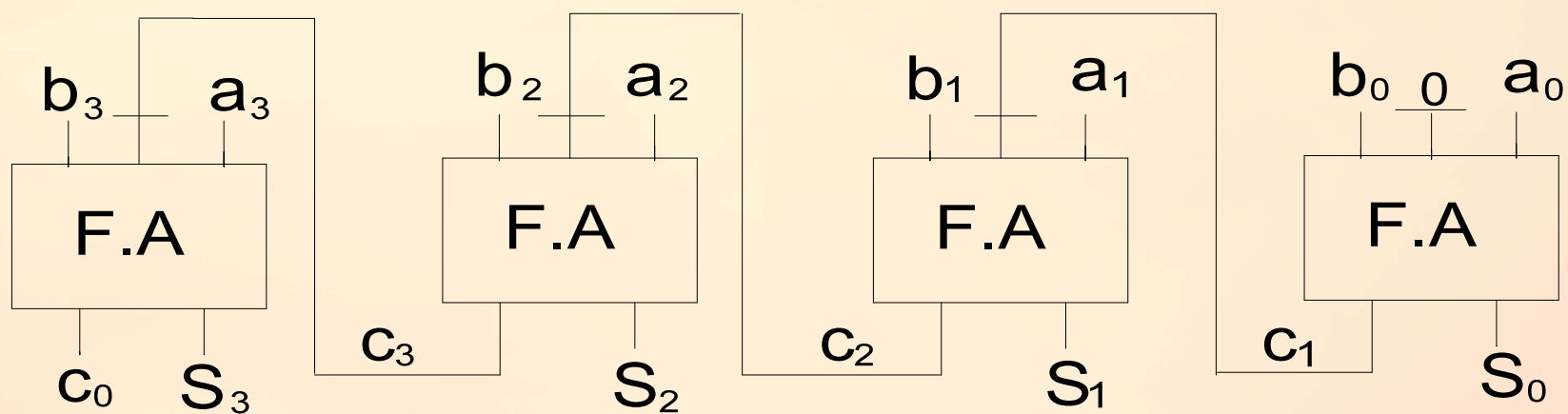

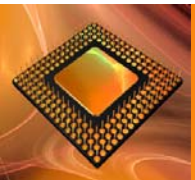

4 Bit Binary Adder

 


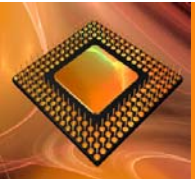


4 Bit Binary Adder




4 bit Binary Adder

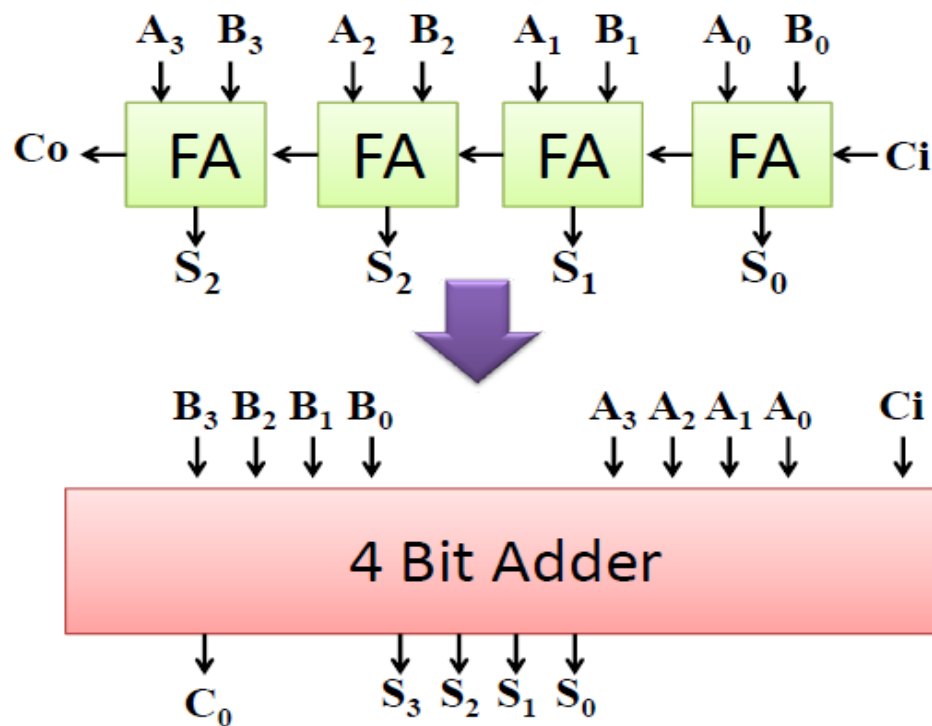


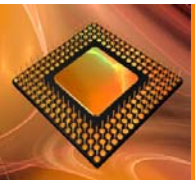



Half Subtractor

 


b	a	B	D
0	0	0	0
0	1	0	1
1	0	1	1
1	1	0	0

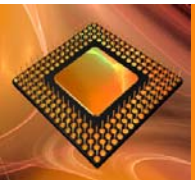


Half Subtractor

  

b	a	B	D
0	0	0	0
0	1	0	1
1	0	1	1
1	1	0	0

 

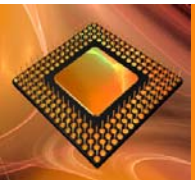
$$\begin{aligned} D &= a \oplus b \\ B &= \overline{a}b \end{aligned}$$




Full Subtractor



B_i	b	a	B_0	D
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

 


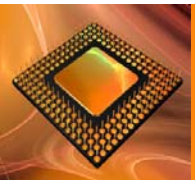

Full Subtractor




B_i	b	a	B_0	D
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

 

$$D = a \oplus b \oplus B_i$$

$$B_o = \bar{a}b + \bar{a}B_i + bB_i$$

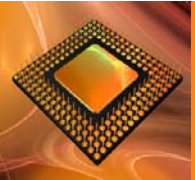



Full Subtractor




$$D = a \oplus b \oplus B_i$$


$$B_o = \bar{a}b + \bar{a}B_i + bB_i$$

 

 

Example for 4 Bit Adder

 


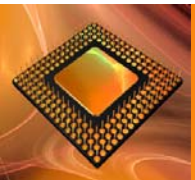


Example for 4 Bit Adder



$$a = 1110 \quad b = 1011$$

 


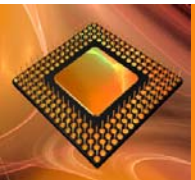


Example for 4 Bit Adder



$$a = 1\ 1\ 1\ 0 \qquad b = 1\ 0\ 1\ 1$$

 


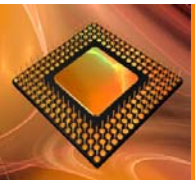

Example for 4 Bit Adder




$$a = 1110 \quad b = 1011$$

 




 Example for 4 Bit Adder

$$a = 1 \ 1 \ 1 \ 0 \qquad b = 1 \ 0 \ 1 \ 1$$




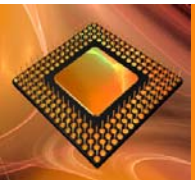


Example for 4 Bit Adder



$$a = 1\ 1\ 1\ 0 \quad b = 1\ 0\ 1\ 1$$

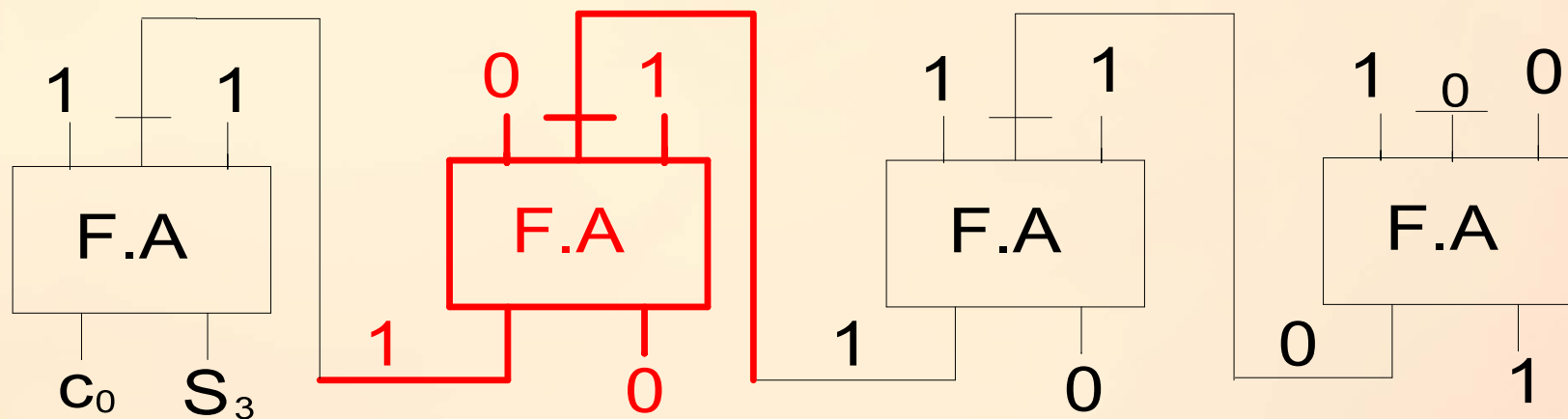


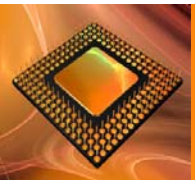


Example for 4 Bit Adder






$a = 1\ 1\ 1\ 0$ $b = 1\ 0\ 1\ 1$

 


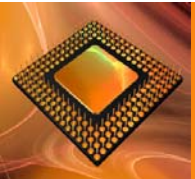


Example for 4 Bit Adder

   


$$A - B = A + \overline{B} + 1$$

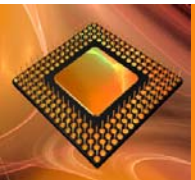



4 Bit Adder Comparator

 

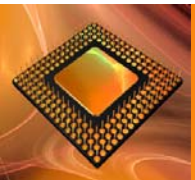



4 Bit Adder Comparator

 

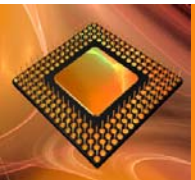


8 Bit Adder Comparator

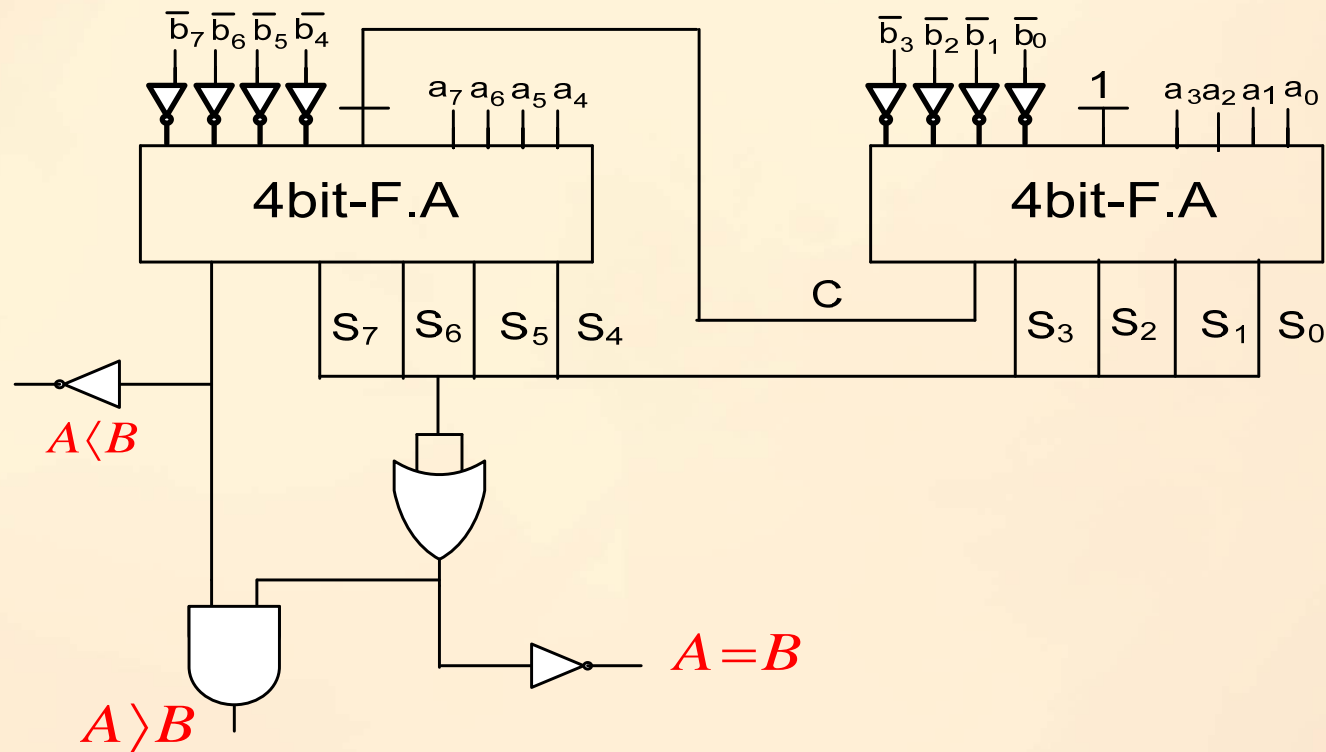


 



Add/Sub Module Design



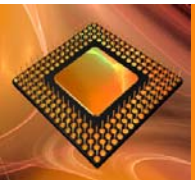


Three State Buffer

 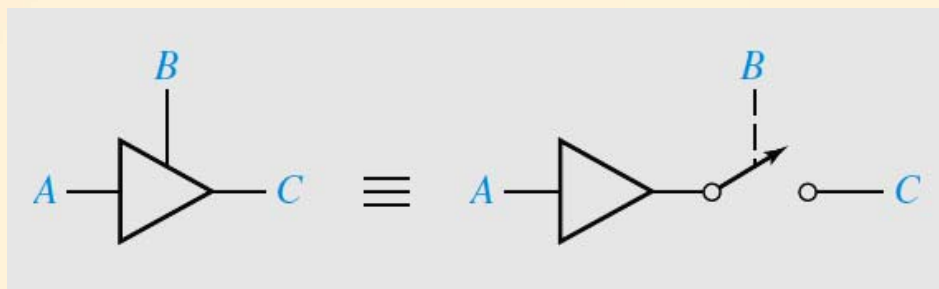

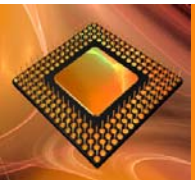

Three State Buffer

 

B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0


(b)

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z


(c)


B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

(d)

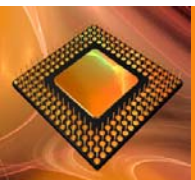



Three State Buffer

 




The bus symbol A 


control input:

 

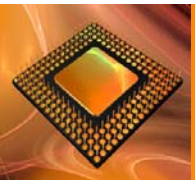


 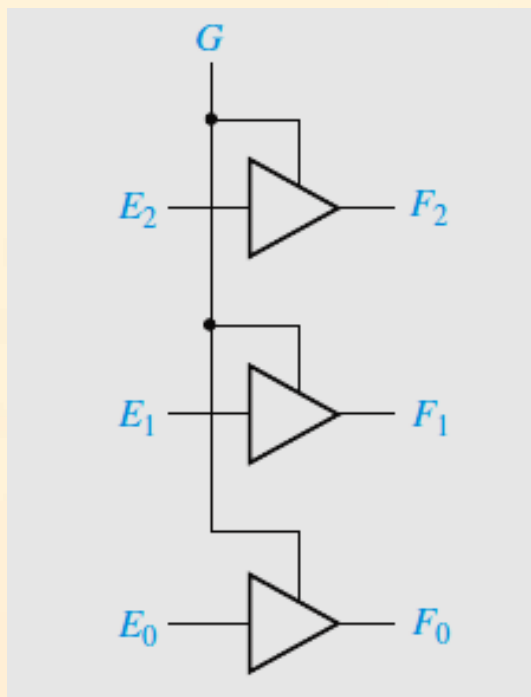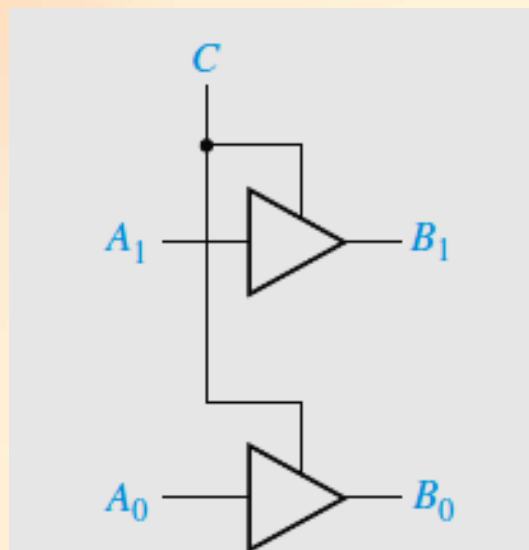
Using bus notation, draw an equivalent circuit for:



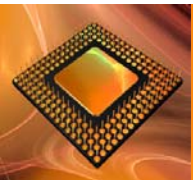



Read Only Memory (ROM)

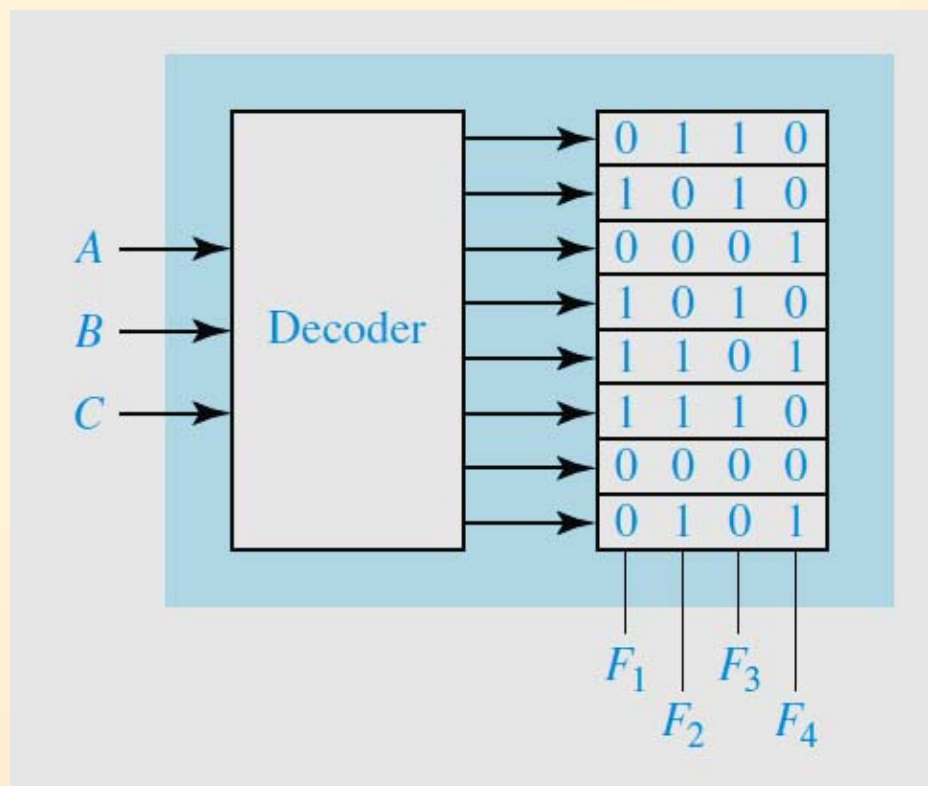

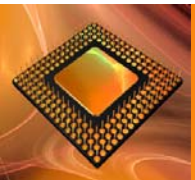



Read Only Memory (ROM)

 

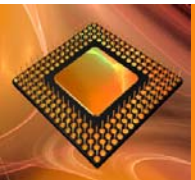



Read Only Memory (ROM)

 

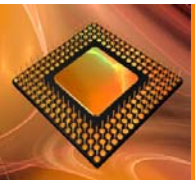


Read Only Memory (ROM)

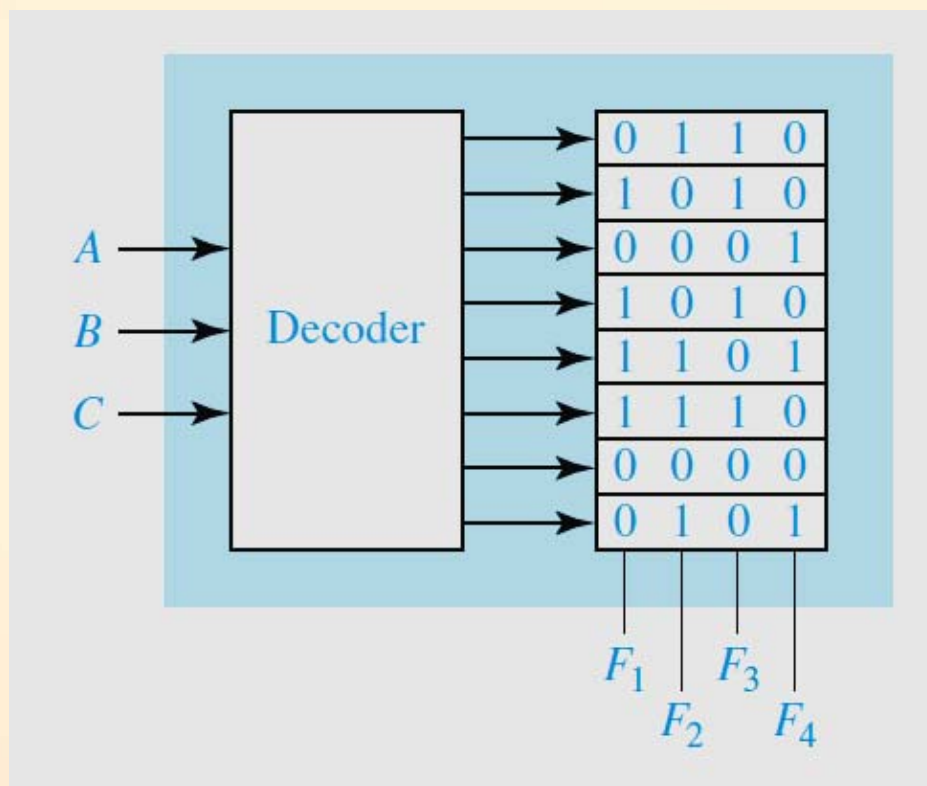

 

Read Only Memory (ROM)

 


(a) Block diagram


A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

Typical Data
Stored in
ROM
(2^3 words of
4 bits each)

(b) Truth table for ROM

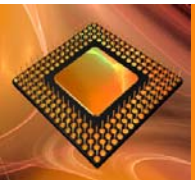


Read Only Memory (ROM)

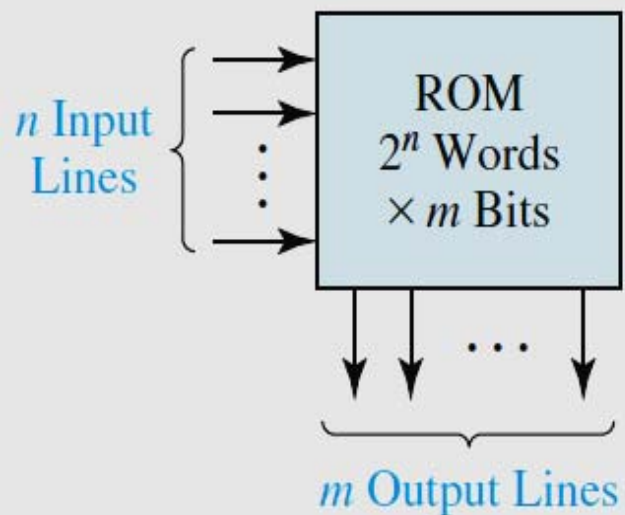



n Input Variables	m Output Variables
00 ... 00	100 ... 110
00 ... 01	010 ... 111
00 ... 10	101 ... 101
00 ... 11	110 ... 010
...	...
11 ... 00	001 ... 011
11 ... 01	110 ... 110
11 ... 10	011 ... 000
11 ... 11	111 ... 101

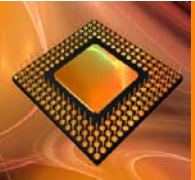Typical Data Array Stored in ROM
(2^n words of m bits each)



Read Only Memory (ROM)

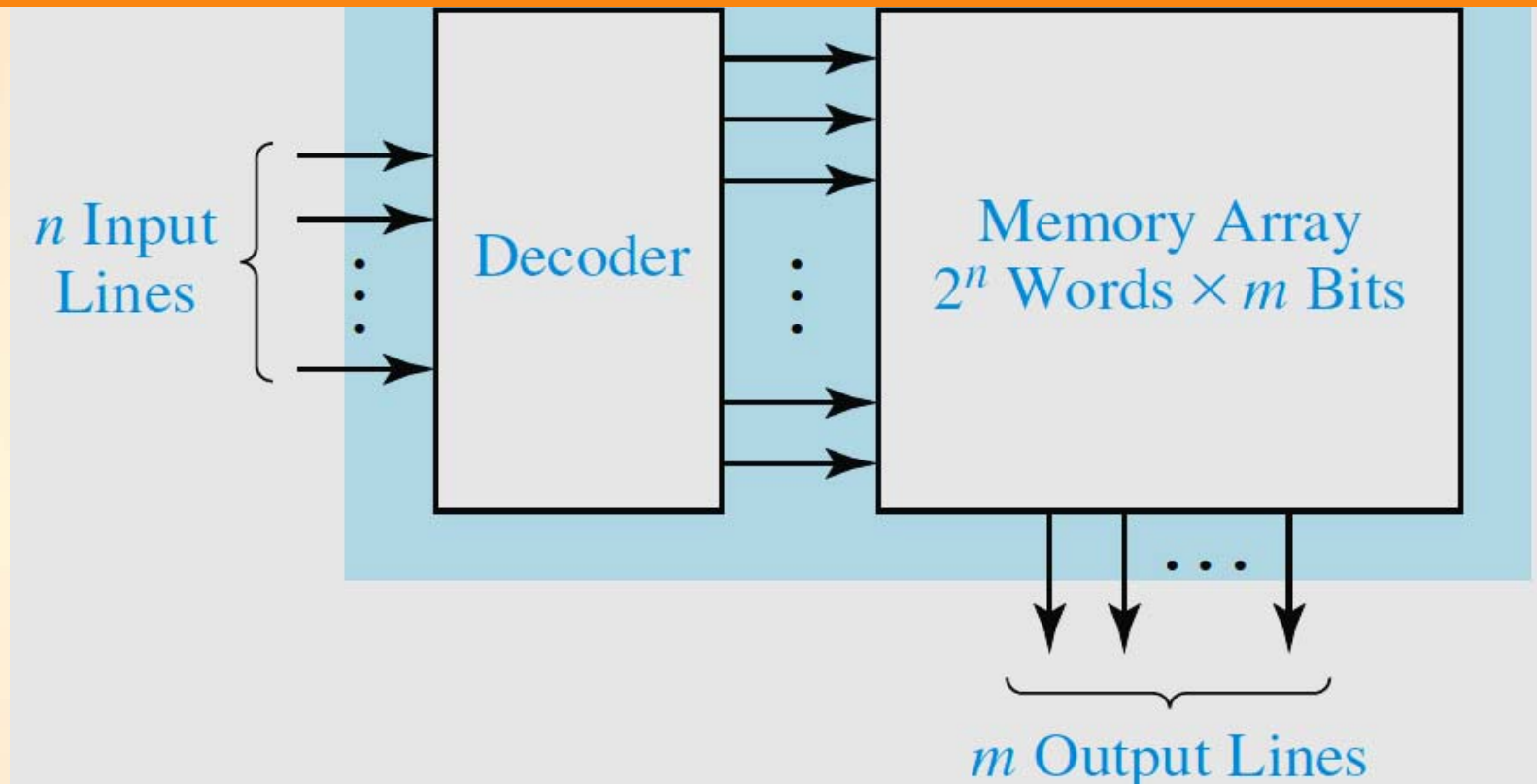


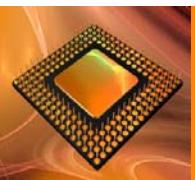


Read Only Memory (ROM)





Input				Hex Digit	ASCII Code for Hex Digit						
W	X	Y	Z		A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	1	1	0	0	0	0
0	0	0	1	1	0	1	1	0	0	0	1
0	0	1	0	2	0	1	1	0	0	1	0
0	0	1	1	3	0	1	1	0	0	1	1
0	1	0	0	4	0	1	1	0	1	0	0
0	1	0	1	5	0	1	1	0	1	0	1
0	1	1	0	6	0	1	1	0	1	1	0
0	1	1	1	7	0	1	1	0	1	1	1
1	0	0	0	8	0	1	1	1	0	0	0
1	0	0	1	9	0	1	1	1	0	0	1
1	0	1	0	A	1	0	0	0	0	0	1
1	0	1	1	B	1	0	0	0	0	1	0
1	1	0	0	C	1	0	0	0	0	1	1
1	1	0	1	D	1	0	0	0	1	0	0
1	1	1	0	E	1	0	0	0	1	0	1
1	1	1	1	F	1	0	0	0	1	1	0

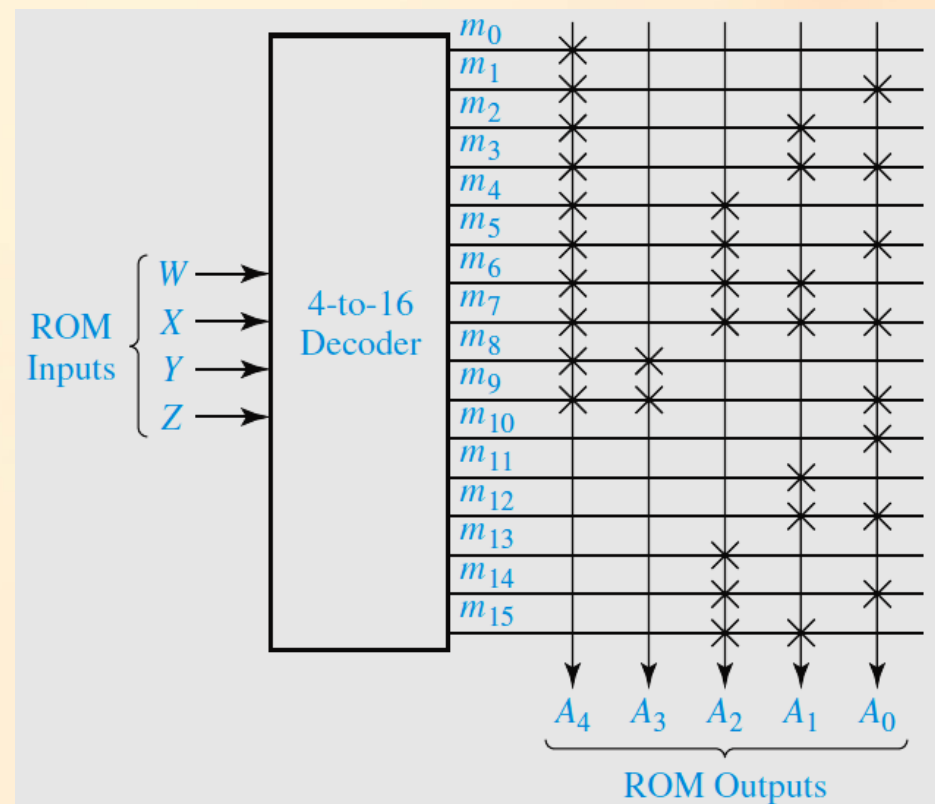

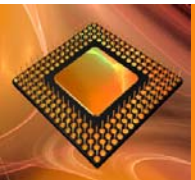


Programmable Logic Array

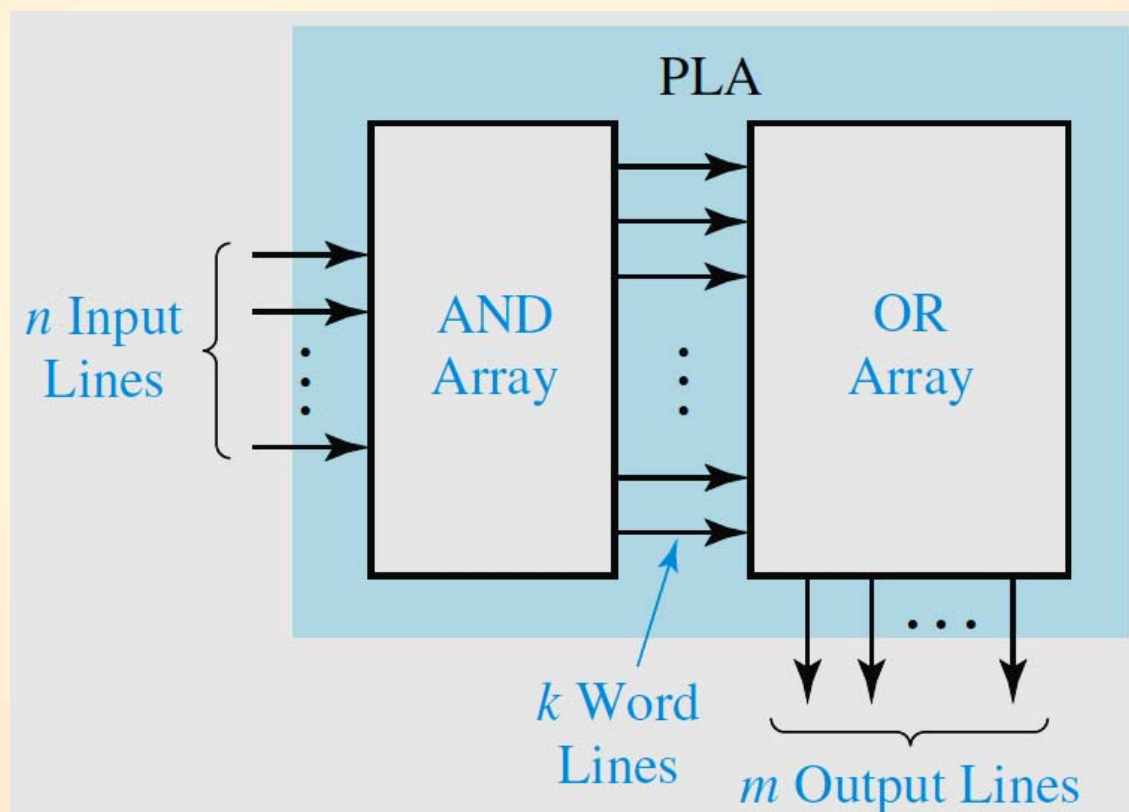


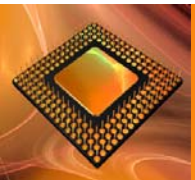


Programmable Logic Array

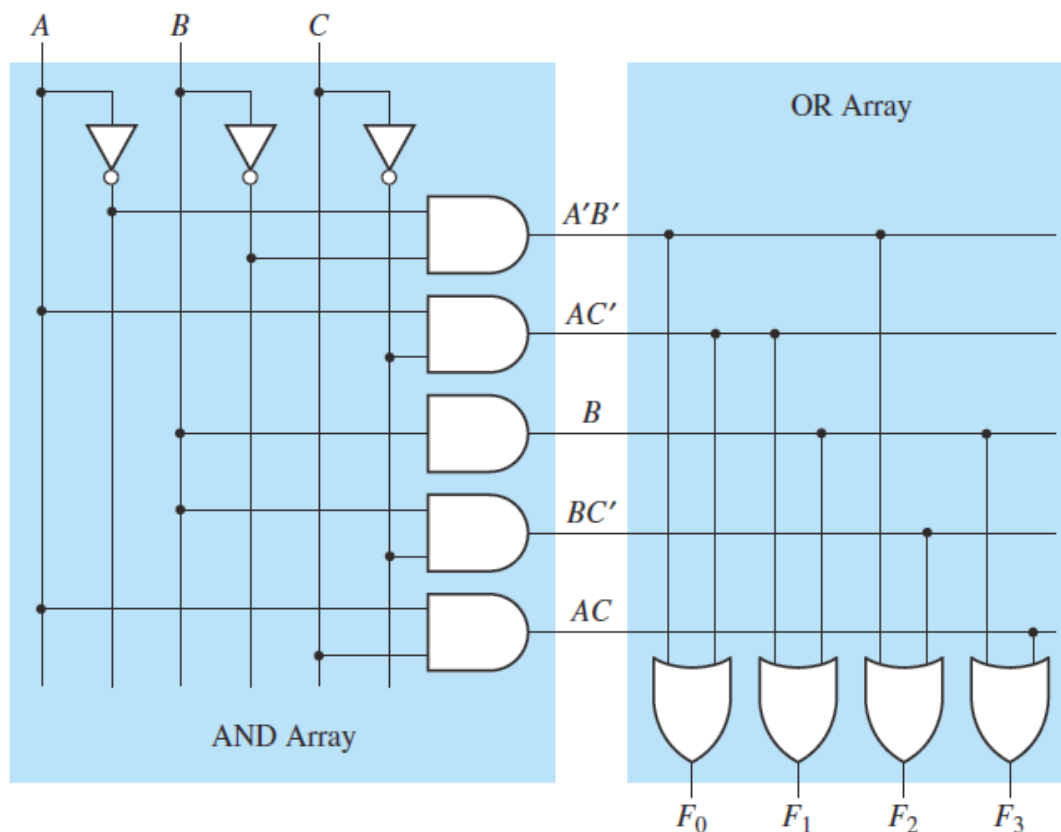


Product Term	Inputs A B C	Outputs F ₀ F ₁ F ₂ F ₃	
A'B'	0 0 -	1 0 1 0	$F_0 = A'B' + AC'$
AC'	1 - 0	1 1 0 0	$F_1 = AC' + B$
B	- 1 -	0 1 0 1	$F_2 = A'B' + BC'$
BC'	- 1 0	0 0 1 0	$F_3 = B + AC$
AC	1 - 1	0 0 0 1	

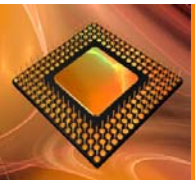


Programmable Logic Array

 


General structure of a PLA

 

Customary schematic for PLA

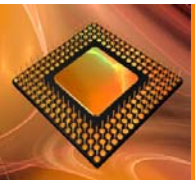


Programmable Logic Array

 


(b) PLA structure


a	b	c	d	f_1	f_2	f_3
0	1	–	1	1	1	0
1	1	–	1	1	0	1
1	0	0	–	1	0	1
–	0	1	–	1	0	0
–	–	1	–	0	1	0
–	1	1	–	0	0	1

(a) PLA table

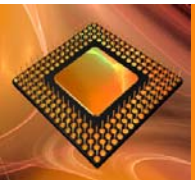


Programmable Logic Array

 

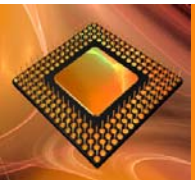

Programmable Logic Array

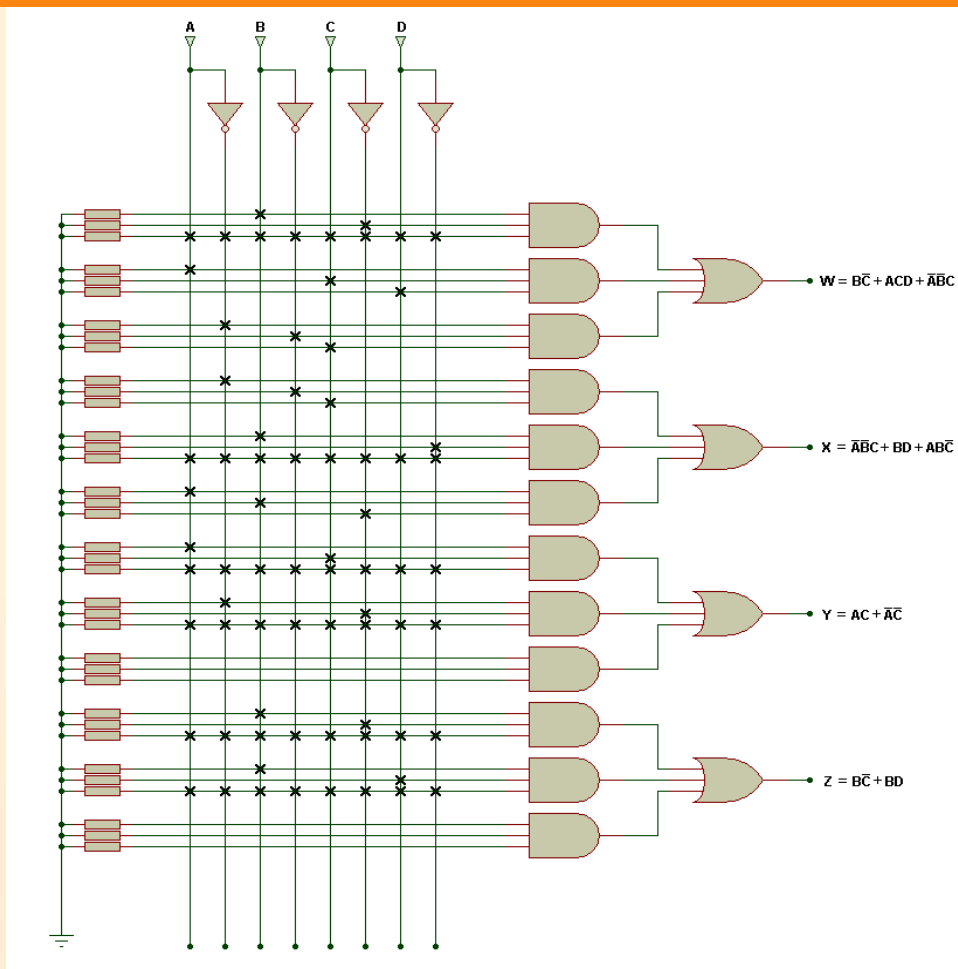



THANK YOU