




Modern Digital System Design

ECE 2372 / Fall 2018 / Lecture 15


Texas Tech University
Dr. Tooraj Nikoubin

Finite State Machines

 


Outline

 
- **Finite State Machine**
 - Describe the sequential behavior using a **FSM**
 - **Example of FSM**
 - Convert a finite state machine to a **Controller** – a sequential circuit having
 - **A register and Combinational logic**



Sequential Circuit: FSM

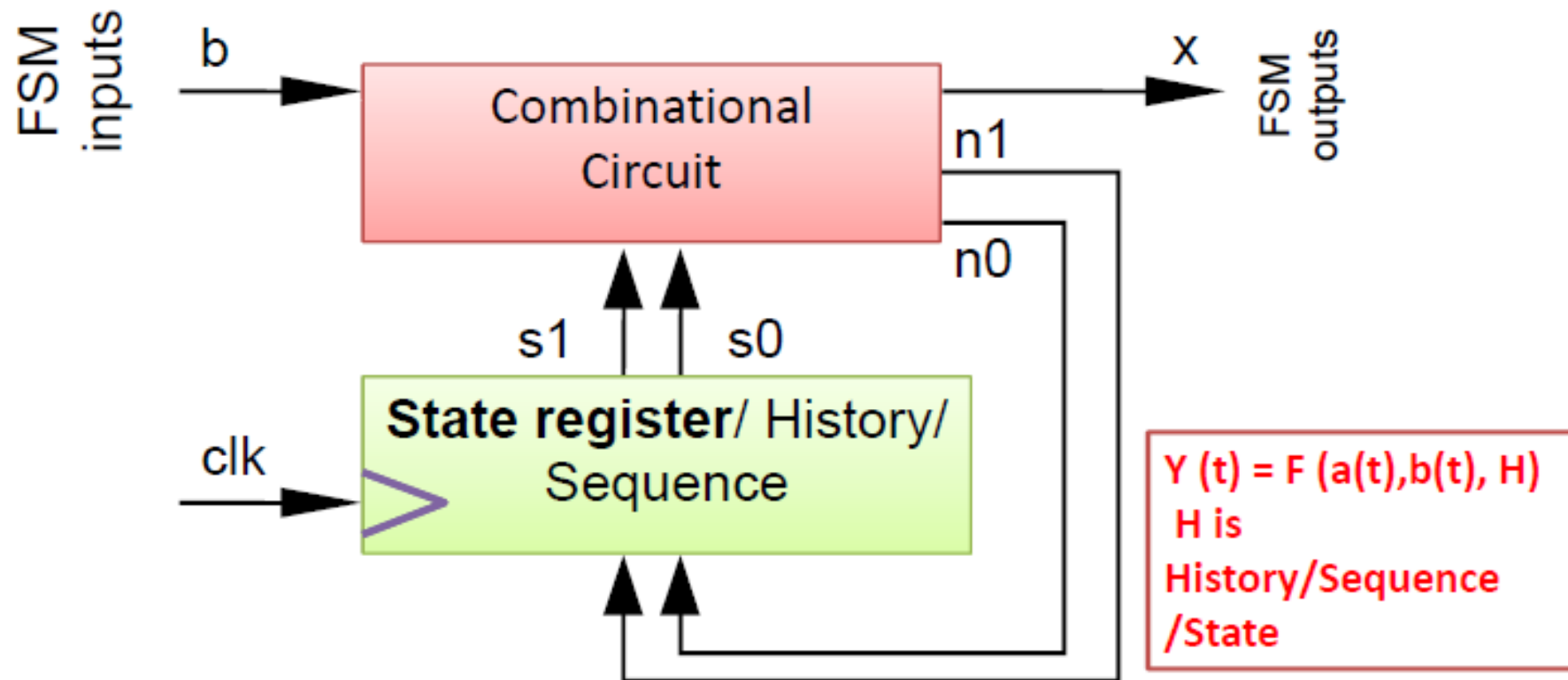


 Formally Describe/mathematically Describe
Boolean Algebra: Working Combinational Circuit
Finite State Machine: Working of Sequential Circuit




Need Better Way to Design Sequential Circuits

 - Trial and error : not a good design method
 - Will we be able to “guess” a circuit that works for other desired behavior?
 - How about counting up from 1 to 9?
 - Pulsing an output for 1 cycle every 10 cycles?
 - Detecting the sequence 1 3 5 in binary on a 3-bit input?




Need a Better Way to Design Sequential Circuits

 - Combinational circuit design process had two important things
 1. A formal way to describe desired circuit behavior
 - Boolean equation, or truth table
 2. A well-defined process to convert that behavior to a circuit
- We need those things for sequence circuit design




Finite State Machine

 - Finite-State Machine (FSM)
 - A way to describe desired behavior of sequential circuit
 - Akin to Boolean equations for combinational behavior
 - List states, and transitions among states






Finite State Machine: Example

 - Example: Make x change toggle (0 to 1, or 1 to 0) every clock cycle
- Two states: “Off” ($x=0$), and “On” ($x=1$)
- Transition from Off to On, or On to Off, on rising clock edge
- Arrow with no starting state points to initial state (when circuit first starts)





Finite State Machine: Example

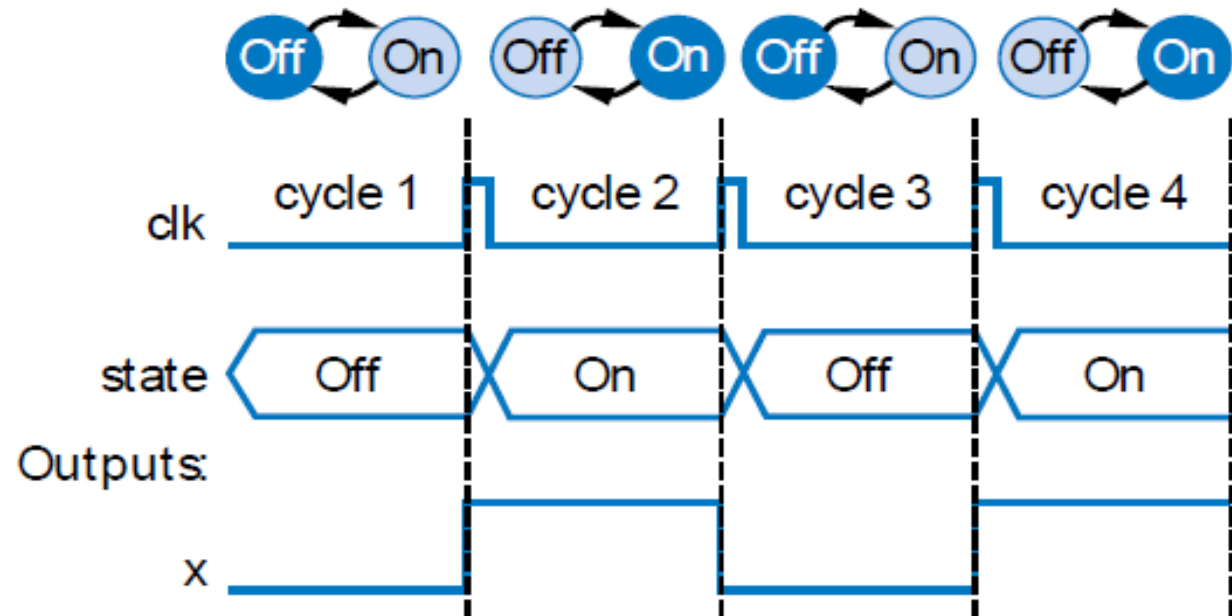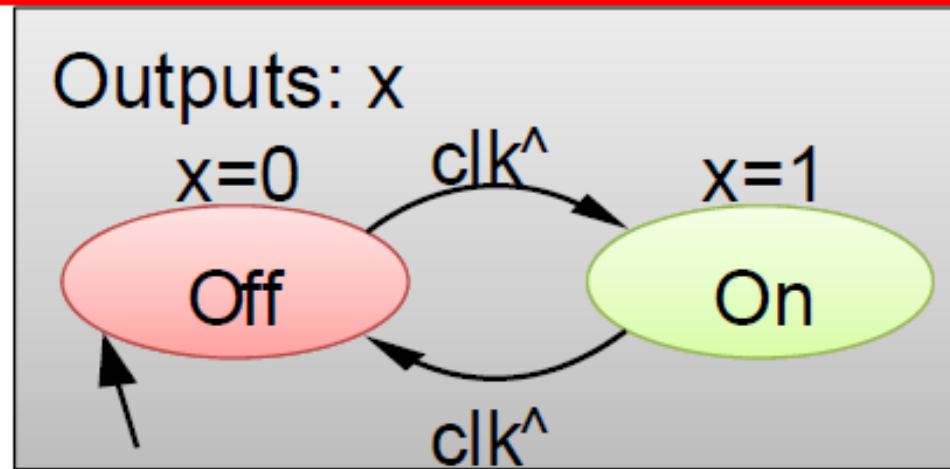

 


Controller for On-Off


Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0

 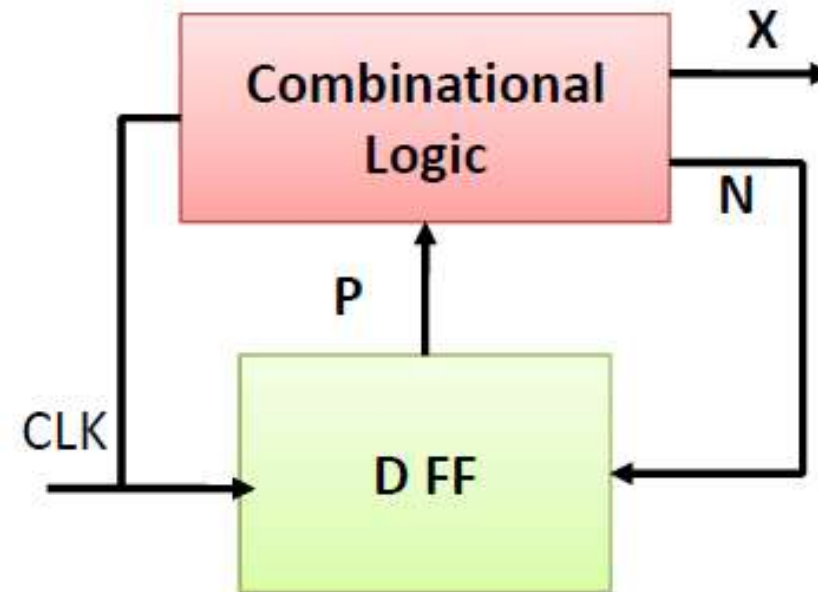

 Think of Clock Enable: only **Rising Edge (RE)**
Above one may not work: Level Sensitive





Rising Edge: Clock implicit

 

FSM Example: 0,1,1,1,repeat

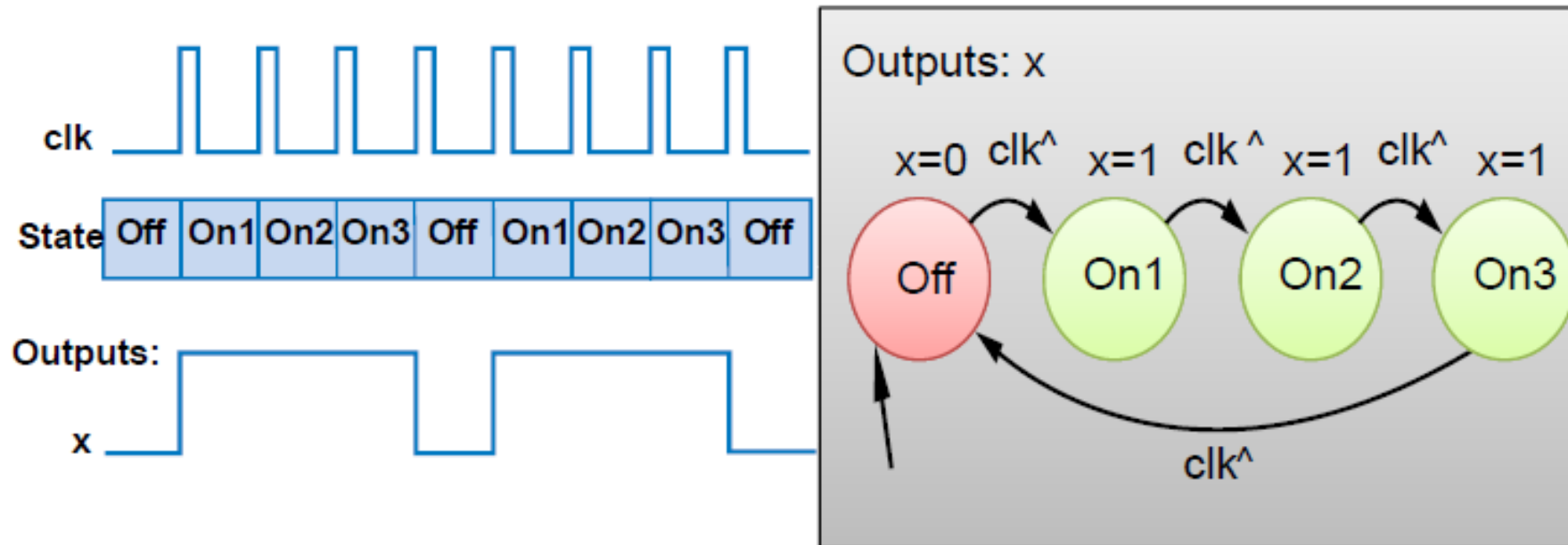
- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state



 



Extend FSM to Three-Cycles High Laser Timer

 - Four states: Wait in “Off” state while b is 0 (b')
- When $b=1$ (& rising clock edge), transition to On1
 - Sets $X=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed



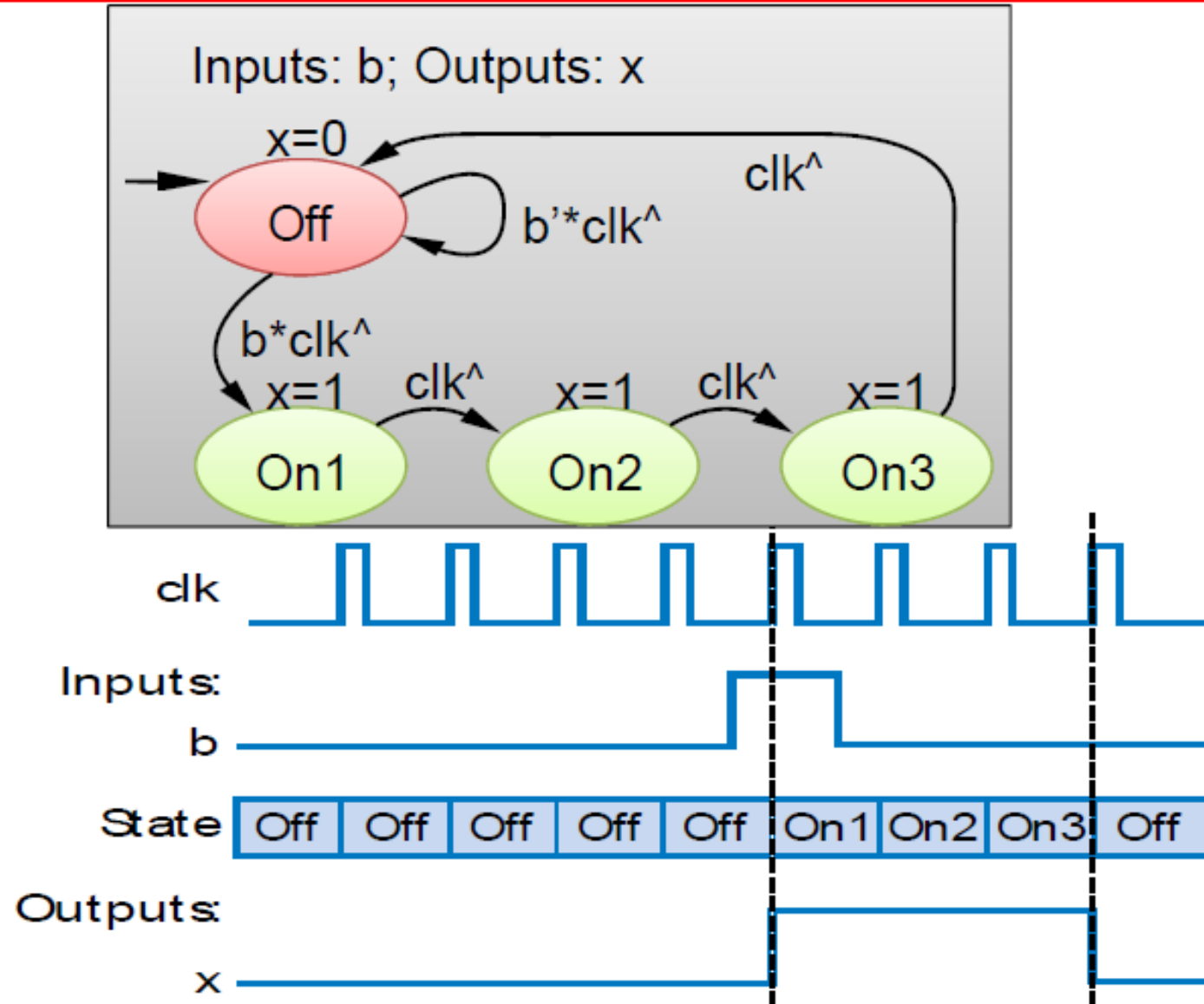
Extend FSM to Three-Cycles High Laser Timer




 



FSM Simplification: Rising Clock Edges Implicit

 - Showing rising clock on every transition: cluttered
- Make implicit -- assume every edge has rising clock
- What if we wanted a transition *without* a rising edge
 - Asynchronous FSMs -- less common, and advanced topic
 - We consider *synchronous* FSMs
 - **All transition on rising edge**



  
FSM Simplification: Rising Clock Edges Implicit



 


FSM Definition

 - **Set of states**
 - Ex: {Off, On1, On2, On3}
- **Set of inputs & set of outputs**
 - Ex: Inputs: {x}, Outputs: {b}
- **Initial state**
 - Ex: “Off”
- **Set of transitions**
 - Describes next states, Ex: Has 5 transitions
- **Set of actions**
 - Sets outputs while in states
 - Ex: $x=0$, $x=1$, $x=1$, and $x=1$




We often draw FSM graphically,
known as *state diagram*

 
Can also use table (state table), or
textual languages



FSM Example: Code Detector

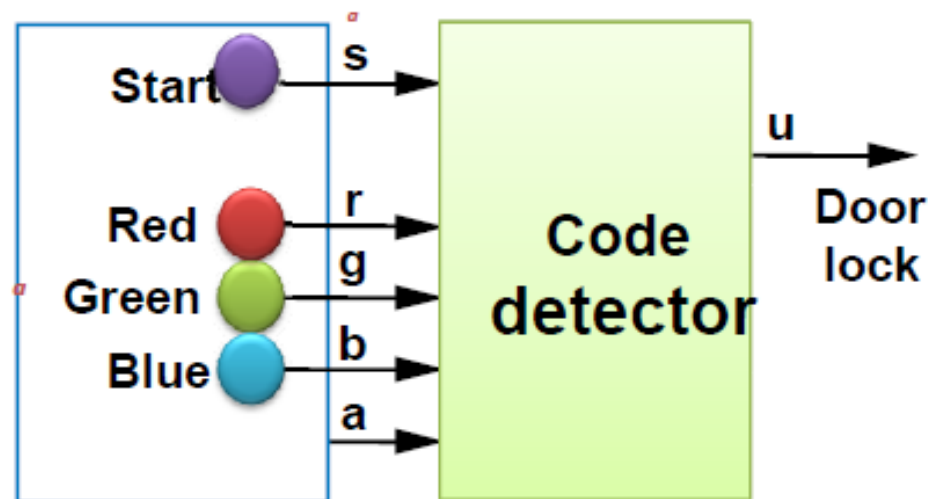
- Unlock door ($u=1$) only when buttons pressed in sequence:
 - **start, then red, blue, green, red**
- Input from each button: s, r, g, b
 - Also, output a indicates that some colored button pressed



 


FSM Example: Code Detector

 - Wait for start ($s=1$) in “Wait”,
- **Once started (“Start”)**
 - If see red, go to “Red1”
 - Then, if see blue, go to “Blue”, Then, if see green, go to “Green”, Then, if see red, go to “Red2”
 - In that state, open the door ($u=1$)
 - Wrong button at any step, return to “Wait”




FSM Example: Code Detector

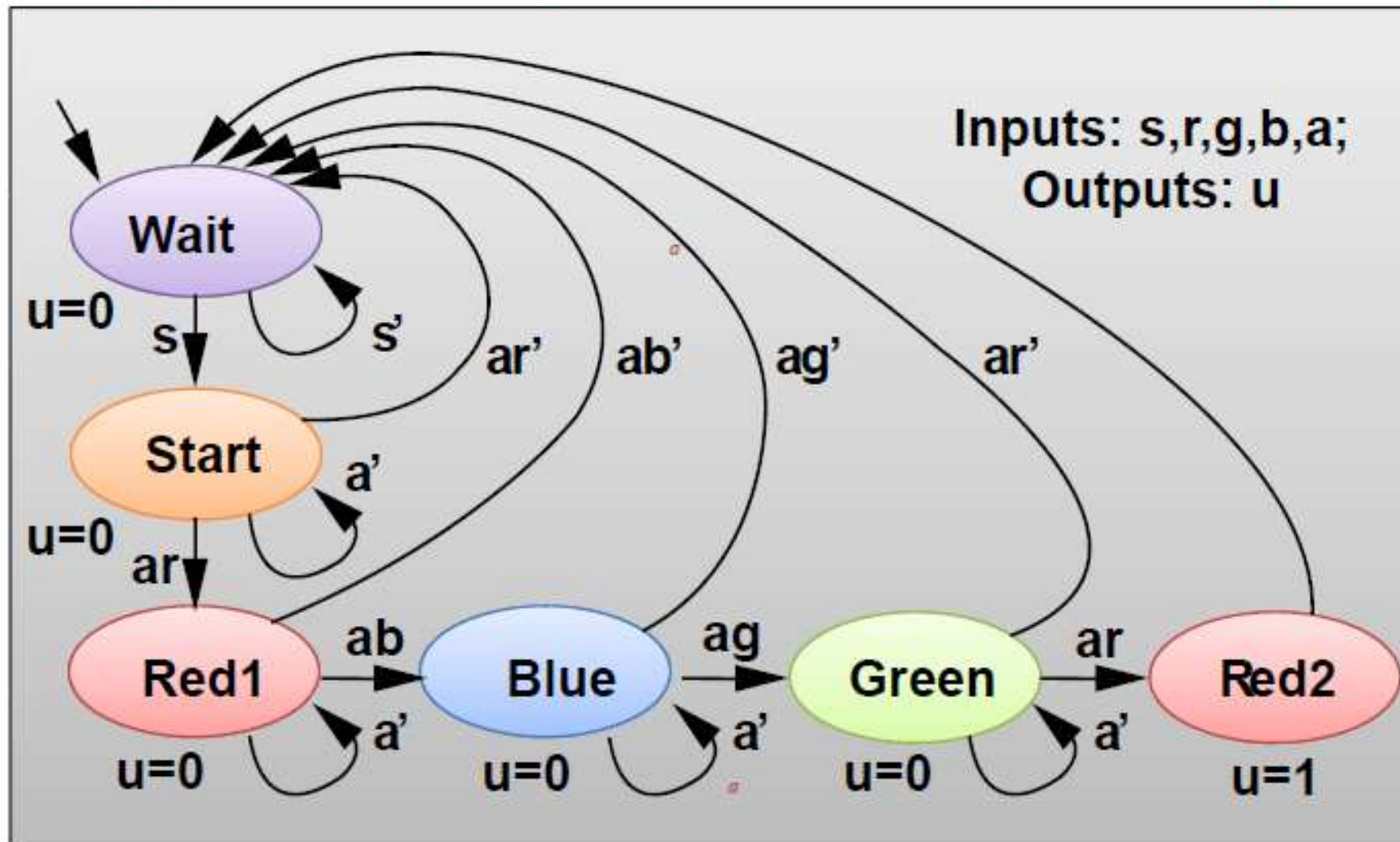


Q: Can you trick this FSM to open the door, without knowing the code?


A: Yes, hold all buttons simultaneously

 


Improve FSM for Code Detector

 

 
- **New transition conditions** detect if wrong button pressed, returns to “Wait”
- FSM provides formal, concrete means to accurately define desired behavior



 
Finite State Machines : Design of digital lock (011)




$$2^3 = 8 \leftarrow$$

 



State Machines : **State Diagram**

 

 



State Machines : **State Diagram**

 

 


State Machines : **State Diagram**

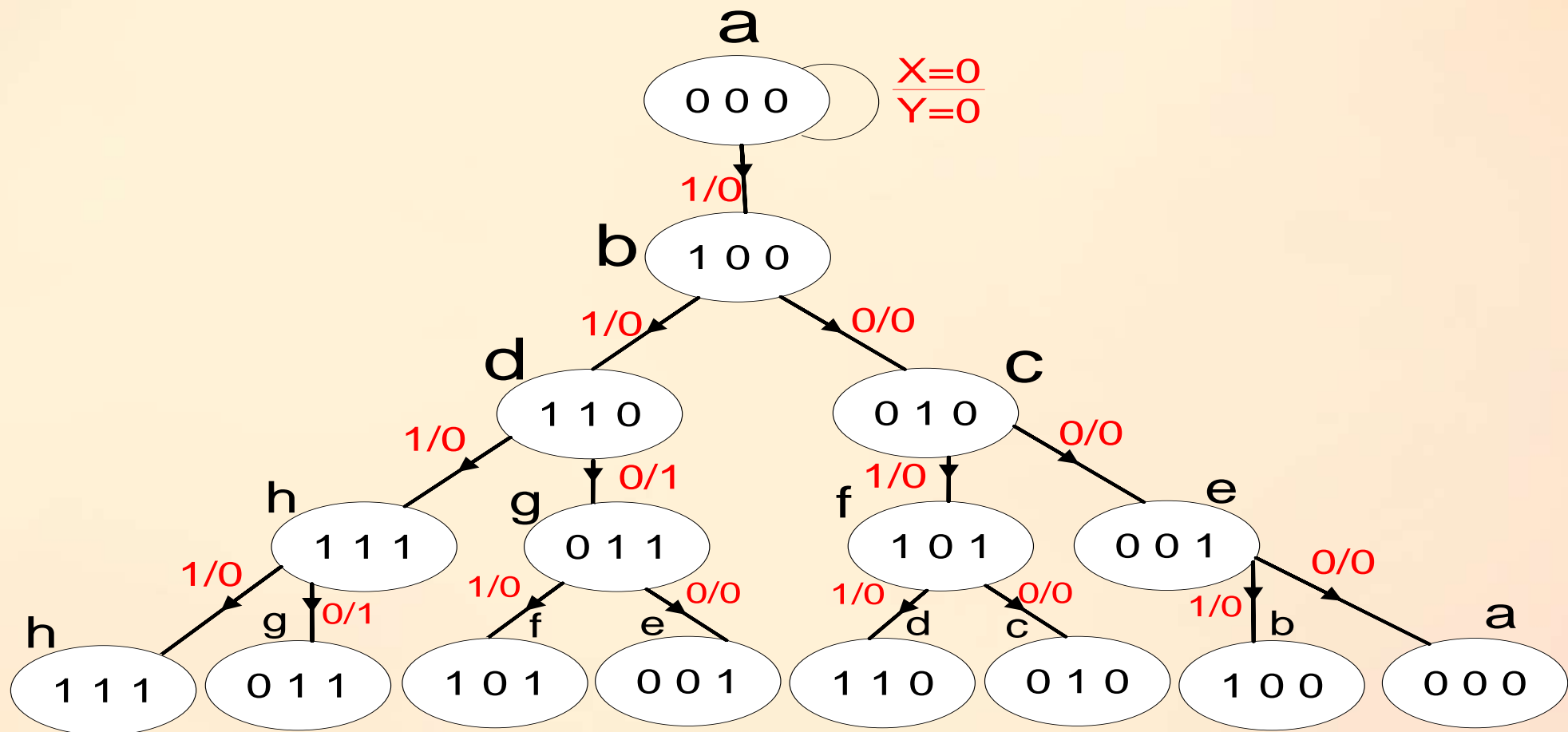


 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1

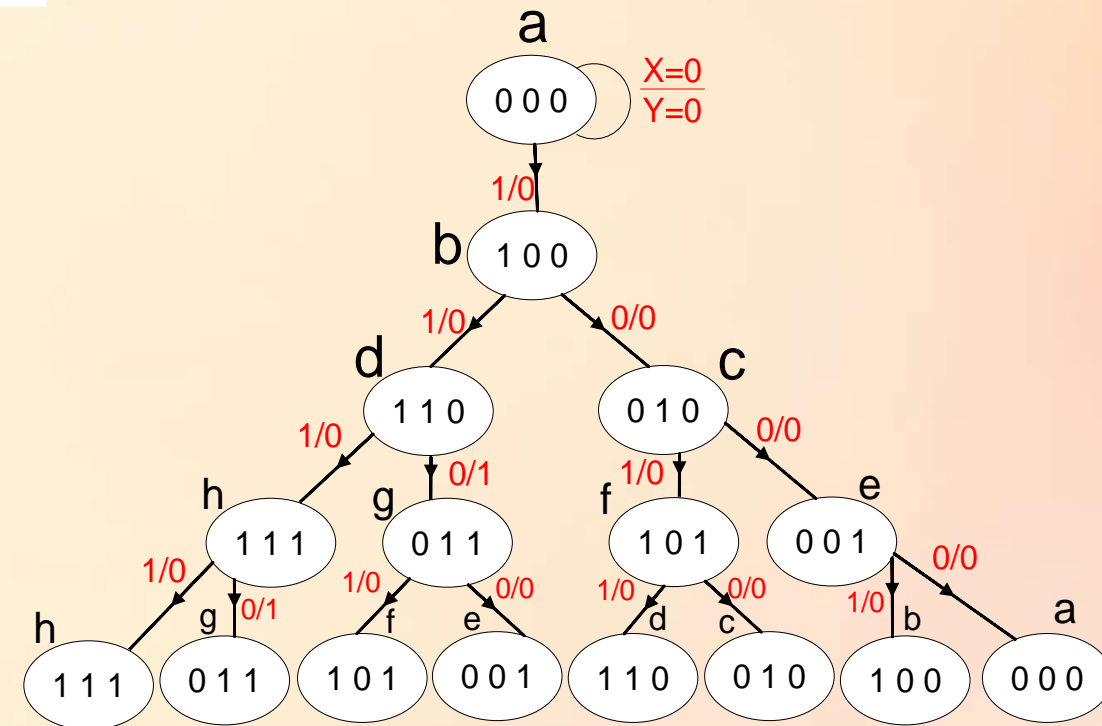


 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
f	c	d	0	0

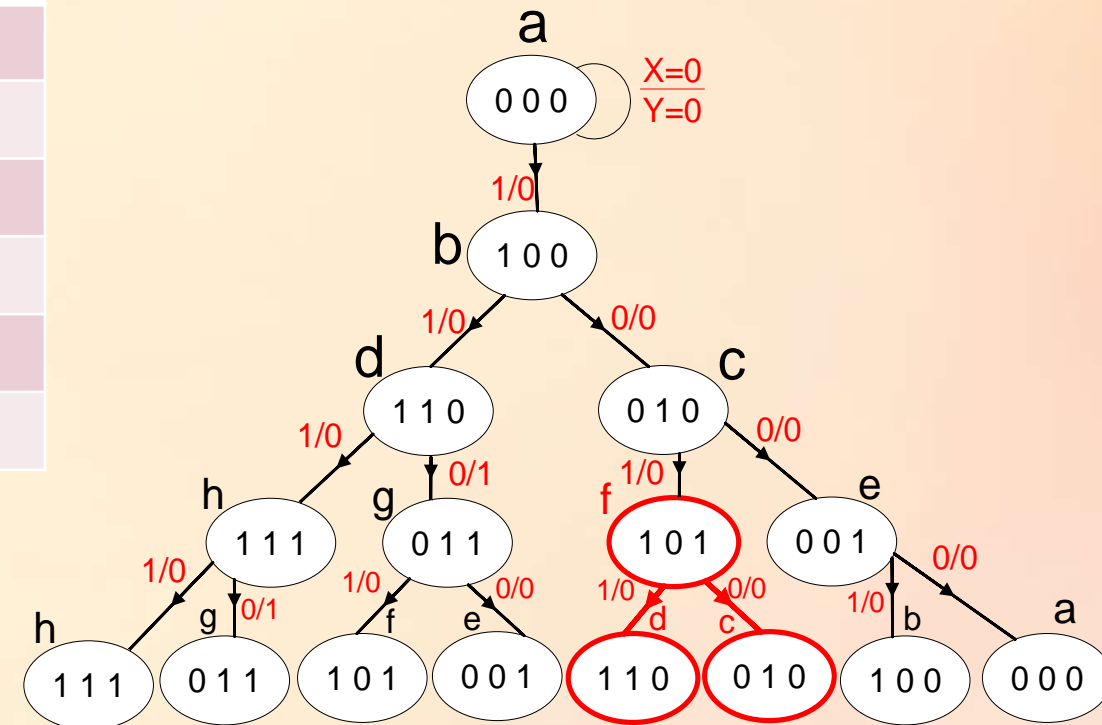


 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
f	c	d	0	0
g	e	f	0	0

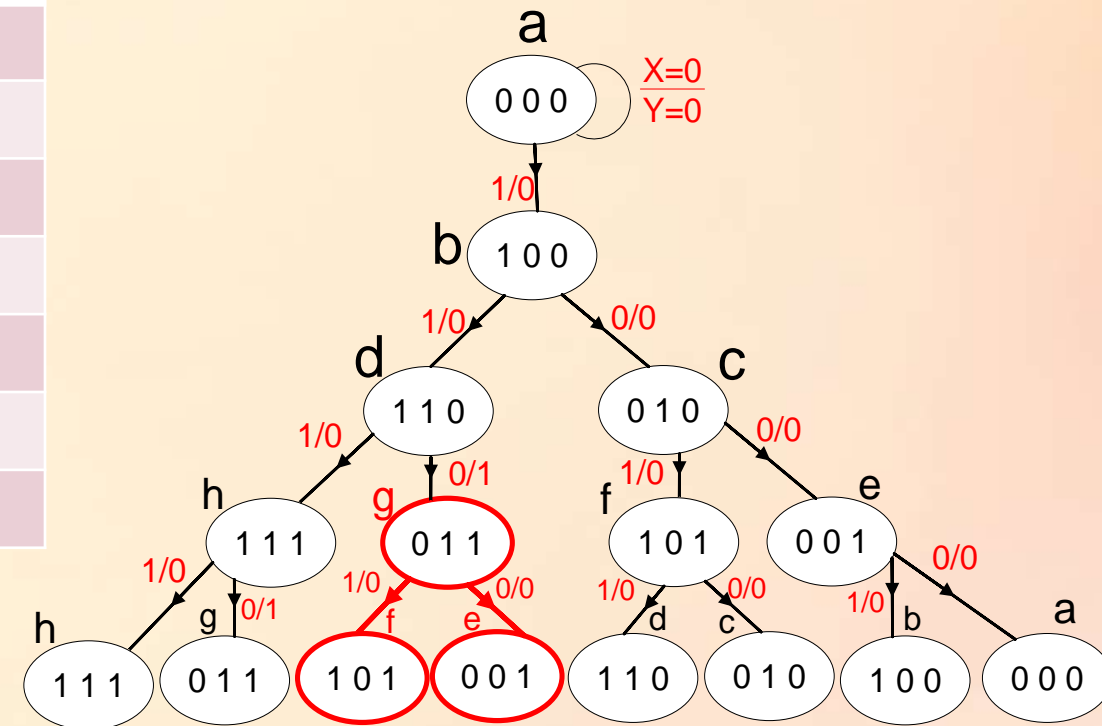


 

State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
f	c	d	0	0
g	e	f	0	0
h	g	h	1	0

 


 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
f	c	d	0	0
g	e	f	0	0
h	g	h	1	0

b←

 

State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
g	e	f	0	0
h	g	h	1	0

 


State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
g	e	f	0	0
h	g	h	1	0


c



 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
h	g	h	1	0

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0
h	g	h	1	0

d ←

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0

 

State Machines : **State Diagram**


a ←

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0
e	a	b	0	0

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0

 

State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	f	0	0
d	g	h	1	0


***f** → b*

 

State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	b	0	0
d	g	h	1	0


g \rightarrow ***c***

 

State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	b	0	0
d	c	h	1	0


$h \rightarrow d$

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	e	b	0	0
d	c	d	1	0

$e \rightarrow a$

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	b	0	0
d	c	d	1	0

 

State Machines : **State Diagram**


a ←

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	b	0	0
d	c	d	1	0

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
d	c	d	1	0

 

State Machines : **State Diagram**


n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
d	c	d	1	0

c \rightarrow ***a***

 


State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	a	d	0	0
d	a	d	1	0

 


State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	a	d	0	0
d	a	d	1	0

 


State Machines : **State Diagram**

n	n+1		(y)Out put	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	a	d	0	0
d	a	d	1	0

 


	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


		x=0	x=1	x=0	x=1
A	B	AB	AB	y	
0	0	00	01	0	0
0	1	00	10	0	0
1	0	00	10	1	0

 


State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


		x=0	x=1		
A	B	AB	AB	y	
0	0	00	01	0	0
0	1	00	10	0	0
1	0	00	10	1	0
 
$$J_B = \begin{matrix} X & A & B \\ & & \\ & & \end{matrix} 100$$




State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


		x=0	x=1		
A	B	AB	AB	y	
0	0	00	01	0	0
0	1	00	10	0	0
1	0	00	10	1	0
 
$$K_B = \begin{matrix} X & A & B \\ 001 + 101 \end{matrix}$$




State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 


		x=0	x=1		
A	B	AB	AB	y	
0	0	00	01	0	0
0	1	00	10	0	0
1	0	00	10	1	0

$$J_A = \overset{X \ A \ B}{101}$$

 


State Machines : **State Diagram**

	A	B
a	0	0
b	0	1
d	1	0
X	1	1

 

		x=0	x=1		
A	B	AB	AB	y	
0	0	00	01	0	0
0	1	00	10	0	0
1	0	00	10	1	0

 
$$K_A = \begin{matrix} X & A & B \\ & 0 & 1 & 0 \end{matrix}$$



State Machines : **State Diagram**

			X	
	0	2	6	4
B	1	3	7	5
		A		

			X	
B		X	X	
		A		

 


State Machines : **State Diagram**



$$J_B = 100$$

			X
B		X	X
		A	

 


State Machines : **State Diagram**



$$J_B = 100$$

		X	
B			1
		X	X
		A	

 


State Machines : **State Diagram**



$$J_B = 100 = \overline{A} \overline{B} X$$

			X
			1
B		X	X
		A	

 


State Machines : **State Diagram**



$$J_B = 100 = \overline{A} \overline{B} X$$

$$K_B = 001 + 101$$

			X
			1
B		X	X
		A	

 

State Machines : **State Diagram**

$$J_B = 100 = \overline{A} \overline{B} X$$


$$K_B = 001 + 101 = B$$

$$J_A = 101 = BX$$

$$K_A = 010 = A \overline{X}$$

$$Y = 010$$

		X	
B		1	
		X	X
		A	

 

State Machines : **State Diagram**



$$J_B = 100 = \overline{A} \overline{B} X$$


$$K_B = 001 + 101 = B$$

$$J_A = 101 = BX$$

$$K_A = 010 = A \overline{X}$$

$$Y = 010$$

		X	
B		1	
		X	X
		A	

 

State Machines : **State Diagram**



$$J_B = 100 = \overline{A} \overline{B} X$$


$$K_B = 001 + 101 = B$$

$$J_A = 101 = BX$$

$$K_A = 010 = A \overline{X}$$

$$Y = 010 = A \overline{X}$$

			X
	1		
B	X	X	
		A	

 

State Machines : **State Diagram**




$$J_B = 100 = \overline{A} \overline{B} X$$


$$K_B = 001 + 101 = B$$

$$J_A = 101 = BX$$


$$K_A = 010 = A \overline{X}$$


$$Y = 010 = A \overline{X}$$

 

 

State Machines : **State Diagram**

 

 

State Machines : **State Diagram**



$$J_B = 100 = \overline{A} \overline{B} X = \overline{A} X$$


$$K_B = 001 + 101 = B = 1$$

$$J_A = 101 = BX$$


$$K_A = 010 = A \overline{X} = \overline{X}$$


$$Y = 010 = A \overline{X}$$

With simplification

 

State Machines : **State Diagram**

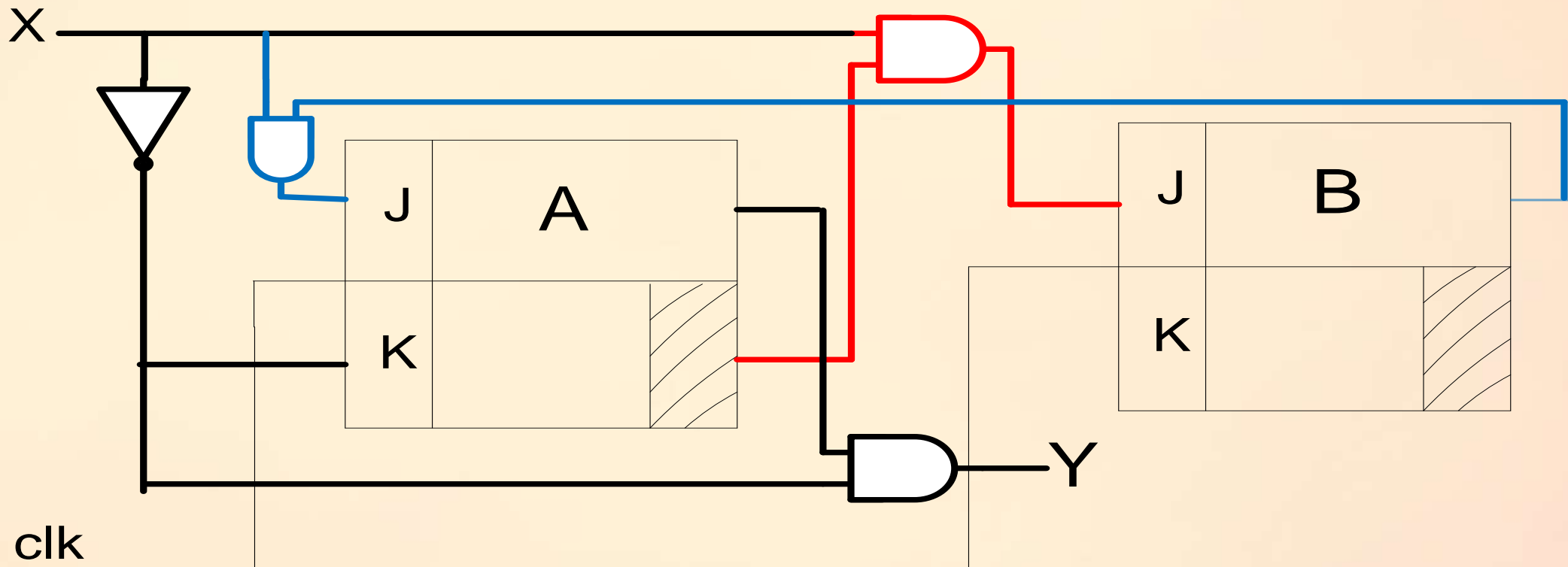

 


State Machines : **State Diagram**




Up-Down counter with input controller :


If $x=“0”$ then count up counter.

If $x=“1”$ then count down counter.

 



State Machines : **State Diagram**

 

 



State Machines : **State Diagram**

 

 



State Machines : **State Diagram**

 

 

State Machines : **State Diagram**

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a
c	d	b

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a
c	d	b
d	e	c

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a
c	d	b
d	e	c
e	f	d

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a
c	d	b
d	e	c
e	f	d
f	g	e

 


 


State Machines : **State Diagram**

State Table

	x=0	x=1
a	b	h
b	c	a
c	d	b
d	e	c
e	f	d
f	g	e
g	h	f

 


 


State Machines : **State Diagram**

State Table


	x=0	x=1
a	b	h
b	c	a
c	d	b
d	e	c
e	f	d
f	g	e
g	h	f
h	a	g

 

 

State Machines : **State Diagram**


	A	B	C
a	0	0	0
b	0	0	1
c	0	1	0
d	0	1	1
e	1	0	0
f	1	0	1
g	1	1	0
h	1	1	1

 

State Machines : **State Diagram**

			X=0			X=1		
A	B	C	A	B	C	A	B	C
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0


$$J_A = 1000 + 0011$$

 

State Machines : **State Diagram**

			X=0			X=1		
A	B	C	A	B	C	A	B	C
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0


$$K_A = 1100 + 0111$$

 

State Machines : **State Diagram**

			X=0			X=1		
A	B	C	A	B	C	A	B	C
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0


$$J_B = 1000 + 0001 + 1100 + 0101$$

 

State Machines : **State Diagram**

			X=0			X=1		
A	B	C	A	B	C	A	B	C
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0

$$K_B = 1010 + 0011 + 1110 + 0111$$

 


State Machines : **State Diagram**



$$J_C = 0000 + 1000 + 0010 + 1010 + 0100 + 1100 + 0110 + 1110$$
 
$$K_C = 0001 + 1001 + 0011 + 1011 + 0101 + 1101 + 0111 + 1111$$



State Machines : **State Diagram**



$$J_A = 1000 + 0011$$


$$K_A = 1100 + 0111$$

$$J_B = 1000 + 0001 + 1100 + 0101$$

$$K_B = 1010 + 0011 + 1110 + 0111$$

$$J_C = 0000 + 1000 + 0010 + 1010 + 0100 + 1100 + 0110 + 1110$$
 
$$K_C = 0001 + 1001 + 0011 + 1011 + 0101 + 1101 + 0111 + 1111$$



State Machines : **State Diagram**



$$J_A = 1000 + 0011 = X \overline{A} \overline{B} \overline{C} + \overline{X} \overline{A} B C$$


$$K_A = 1100 + 0111 = X A \overline{B} \overline{C} + \overline{X} A B C$$

$$J_B = 1000 + 0001 + 1100 + 0101 = X \overline{B} \overline{C} + \overline{X} \overline{B} C$$

$$K_B = 1010 + 0011 + 1110 + 0111 = X B$$

$$J_C = 0000 + 1000 + 0010 + 1010 + 0100 + 1100 + 0110 + 1110 = \overline{C}$$
 
$$K_C = 0001 + 1001 + 0011 + 1011 + 0101 + 1101 + 0111 + 1111 = C$$



State Machines : **State Diagram**



$$J_A = 1000 + 0011 = X \overline{A} \overline{B} \overline{C} + \overline{X} \overline{A} B C = X \overline{B} \overline{C} + \overline{X} B C$$


$$K_A = 1100 + 0111 = X A \overline{B} \overline{C} + \overline{X} A B C = X \overline{B} \overline{C} + \overline{X} B C$$

$$J_B = 1000 + 0001 + 1100 + 0101 = X \overline{B} \overline{C} + \overline{X} \overline{B} C = X \overline{C} + \overline{X} C = X \oplus C$$


$$K_B = 1010 + 0011 + 1110 + 0111 = X B = X$$



$$J_C = 0000 + 1000 + 0010 + 1010 + 0100 + 1100 + 0110 + 1110 = \overline{C} = 1$$
 
$$K_C = 0001 + 1001 + 0011 + 1011 + 0101 + 1101 + 0111 + 1111 = C = 1$$




State Machines : **State Diagram**

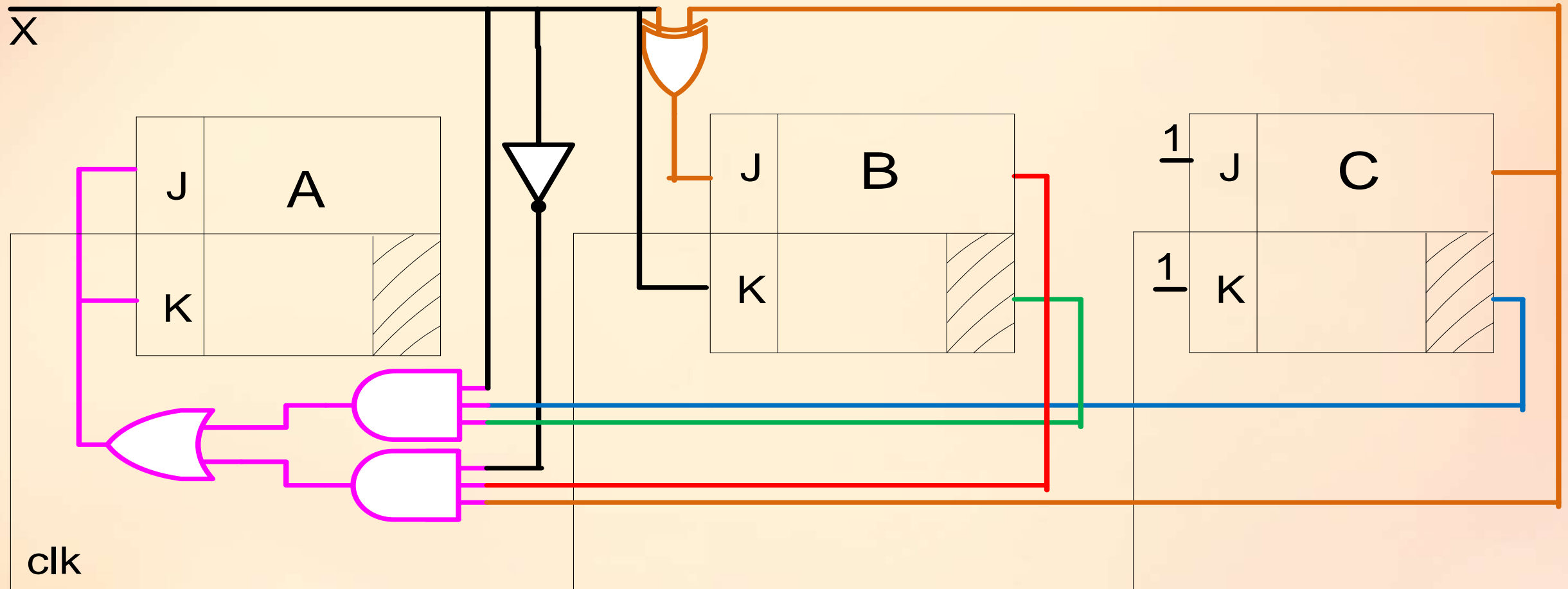


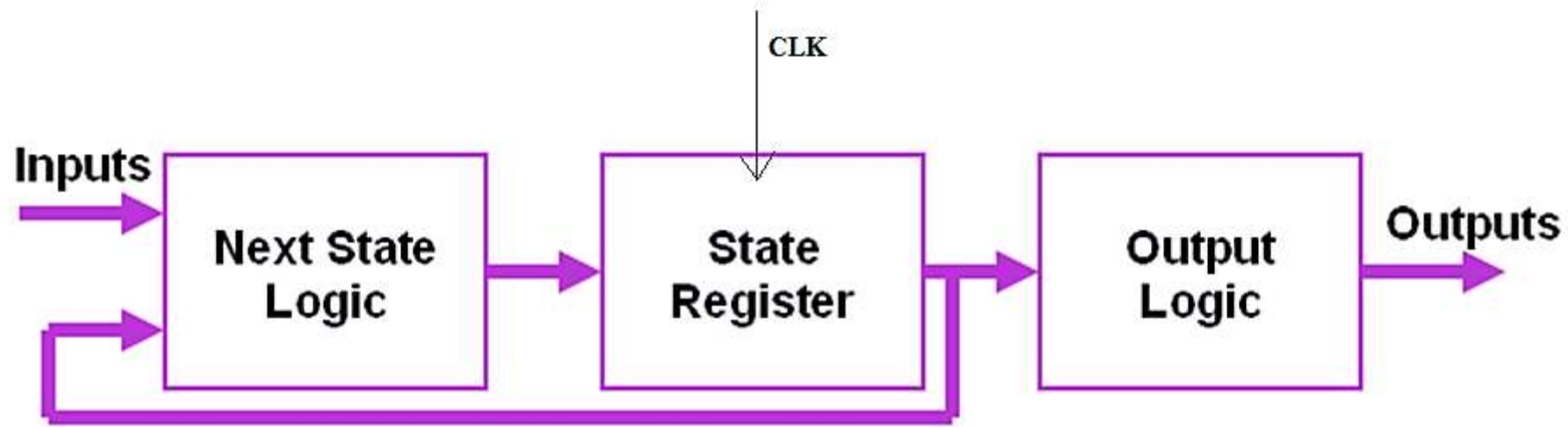
 


Moore State Machine

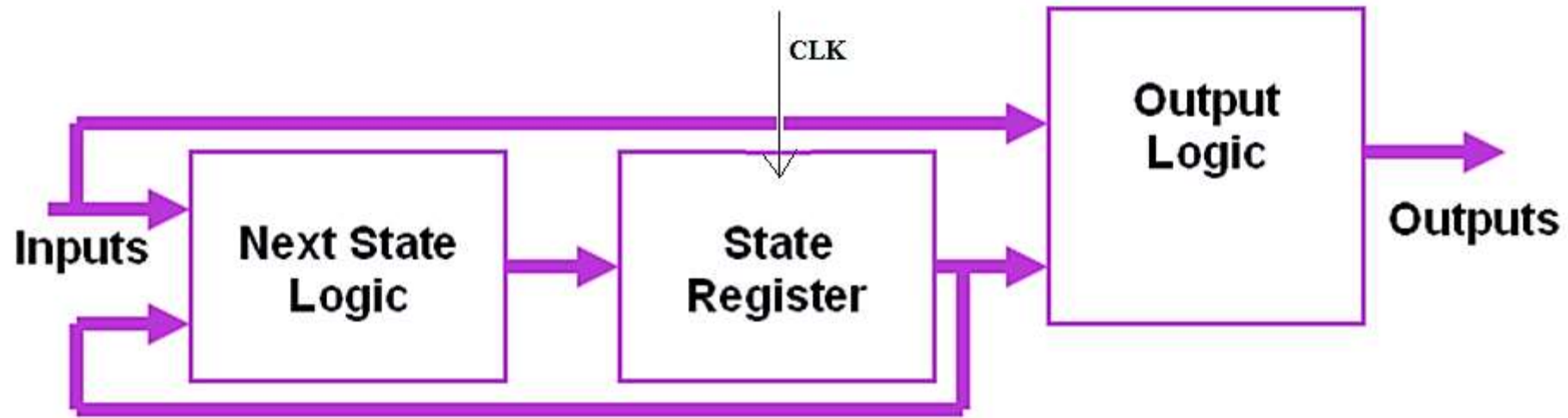



Mealy State Machine



 


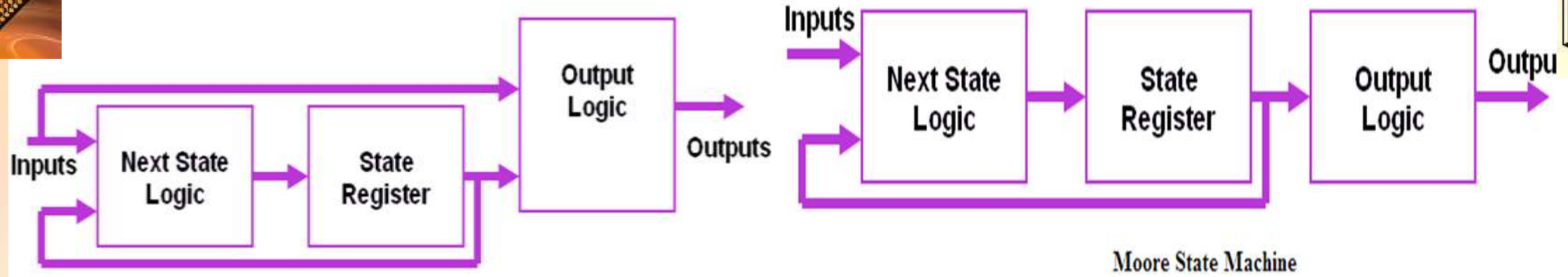 

Mealy State Machine



Moore State Machine

  

   


Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S0				
S1				
S2				
S3				
S4				
S5				


Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S0				
S1				
S2				
S3				
S4				
S5				

  

Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S0	s1	s4	0	0
S1	s1	s2	0	0
S2	s3	s4	1	0
S3	s5	s2	0	0
S4	s3	s4	0	0
S5	s1	s2	0	1

 


Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S0	s1	s4	0	0
S1	s1	s2	0	0
S2	s3	s4	1	1
S3	s5	s2	1	1
S4	s3	s4	0	0
S5	s1	s2	0	0


 


 Example:



Given the following timing chart for sequential circuit, construct as much of the state table as possible. Is this a Mealy or Moore machine? In the chart X_1 and X_2 are independent input signals and Z_1 and Z_2 are output signals. (X_2X_1/Z_2Z_1)





Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00								
01								
10								
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01								
10								
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01								
10							10	
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01								
10						01	10	
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		
10						01	10	
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		00
10						01	10	
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		00
10						01	10	11
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		00
10						01	10	11
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		00
10						01	10	11
11								

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00							01	
01						00		00
10						01	10	11
11							10	

  



Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00			10				01	
01						00		00
10						01	10	11
11							10	

  


Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00			10				01	
01						00		00
10		01				01	10	11
11							10	

  

Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1 00	X2X1 01	X2X1 10	X2X1 11	X2X1 00	X2X1 01	X2X1 10	X2X1 11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00			10				01	
01				10		00		00
10		01				01	10	11
11							10	

  


Present State (Q2Q1)	Next State (Q2Q1)				Output (Z2,Z1)			
	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1	X2X1
	00	01	10	11	00	01	10	11
	Q2Q1	Q2Q1	Q2Q1	Q2Q1	Z2Z1	Z2Z1	Z2Z1	Z2Z1
00			10				01	
01				10		00		00
10		01	11			01	10	11
11							10	

 



Determine the state graph of following state table:

Present State	Next State		Output (Z)	
	X = 0	X = 1	X = 0	X = 1
000	100	101	1	0
001	100	101	0	1
010	000	000	1	0
011	000	000	0	1
100	111	110	1	0
101	110	110	0	1
110	011	010	1	0
111	011	011	0	1

 

 Determine the state table of following state graph:



 


14.34 A sequential circuit has an input (X) and an output (Z). The output is the same as the input was two clock periods previously. For example,

$X = 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 1$

$Z = 0\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0$

 The first two values of Z are 0. Find a Mealy state graph and table for the circuit.




14.34 A sequential circuit has an input (X) and an output (Z). The output is the same as the input was two clock periods previously. For example,


$X = 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1$

$Z = 0\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0$

The first two values of Z are 0. Find a Mealy state graph and table for the circuit.

n		$n+1$		Z	
AB		$X=0$	$X=1$	$X=0$	$X=1$
	0 0	0 0	1 0	0	0
	0 1	0 0	1 0	1	1
	1 0	0 1	1 1	0	0
	1 1	0 1	1 1	1	1

go to output

 

14.34 A sequential circuit has an input (X) and an output (Z). The output is the same as the input was two clock periods previously. For example,

$X = 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1$


$Z = 0\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0$

The first two values of Z are 0. Find a Mealy state graph and table for the circuit.

	n		$n+1$		z	
	X	B	X	B	X	B
	0	0	0	0	0	0
	0	1	0	0	1	1
	1	0	0	1	0	0
	1	1	0	1	1	1

New input data

go to output

 

The direction of data is left to right
It could be right to left too.





14.34 A sequential circuit has an input (X) and an output (Z). The output is the same as the input was two clock periods previously. For example,

$X = 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1$

$Z = 0\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0$

  The first two values of Z are 0. Find a Mealy state graph and table for the circuit.



The direction of data is left to right
It could be right to left too.

A	B	
0	0	a
0	1	b
1	0	c
1	1	d

n	n+1		Z	
	X=0	X=1	X=0	X=1
a	a	c	0	0
b	a	c	1	1
c	b	d	0	0
d	b	d	1	1





14.34 A sequential circuit has an input (X) and an output (Z). The output is the same as the input was two clock periods previously. For example,

$X = 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1$

$Z = 0\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0$

  
The first two values of Z are 0. Find a Mealy state graph and table for the circuit.



The direction of data is left to right
It could be right to left too.

A	B	
0	0	a
0	1	b
1	0	c
1	1	d

n	n+1		Z	
	X=0	X=1	X=0	X=1
a	a	c	0	0
b	a	c	1	1
c	b	d	0	0
d	b	d	1	1

 



THANK YOU