




Modern Digital System Design

ECE 2372 / Fall 2018 / Lecture 08

Texas Tech University
Dr. Tooraj Nikoubin

 Multiplexer, Decoder
Logic Implementation Using MUX & Decoder




Outline



Study of Components

 - Multiplexor, Decoder
- Logic Implementation Using MUX & Decoder




Multiple-Output Circuits




- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex: $F = ab + c'$, $G = ab + bc$


- Ex: $F = \underline{ab} + c'$, $G = \underline{ab} + bc$

 

Option 1: Separate circuits

 


Option 2: Shared gates

 


Decoder




 
- Decoder : knows what to do with this: Decode
- N input: 2^N output
- Memory Addressing
 - Address to a particular location
- **Decoder**: Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
 - So has four outputs, one for each possible input binary number



 


Decoder in Memory structures

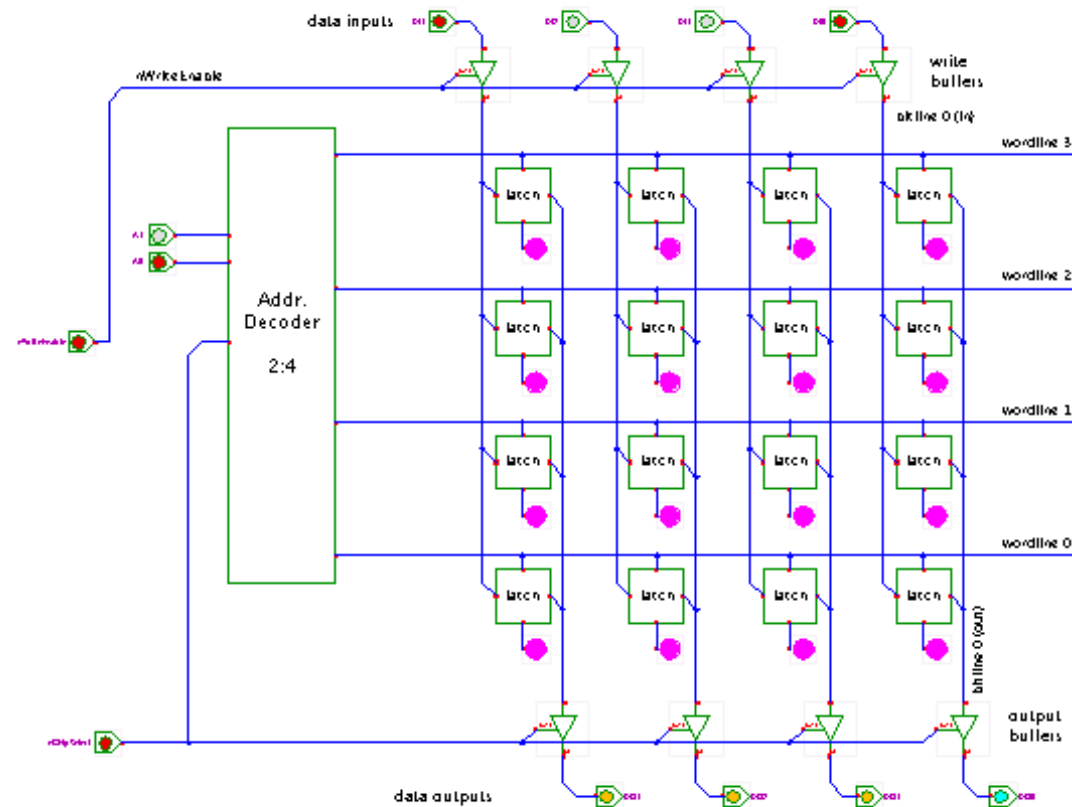


 



Decoders and Multiplexers (Muxes)

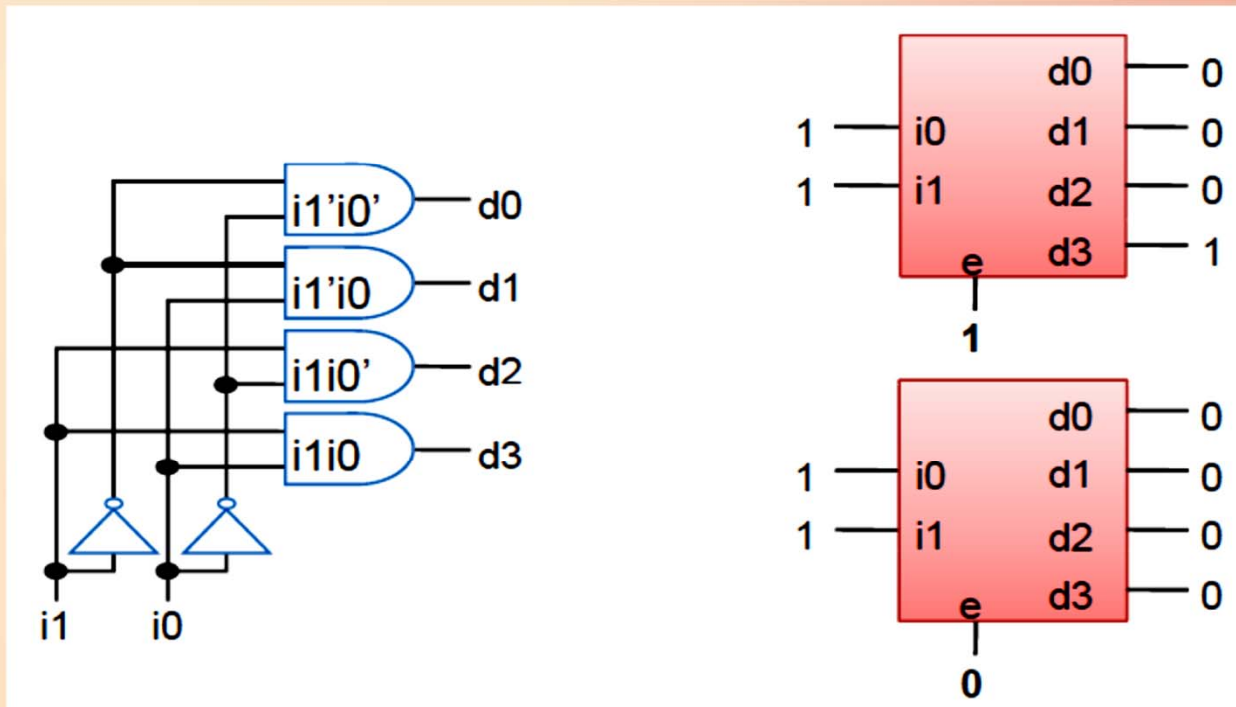- Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if $e=0$, Regular behavior if $e=1$
- n -input decoder: 2^n outputs




 


Decoder

 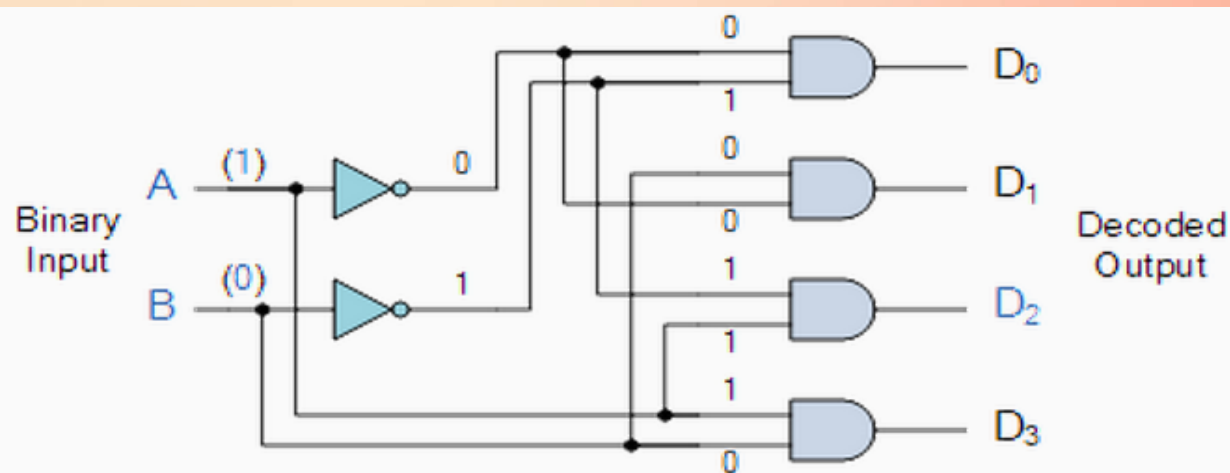


A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

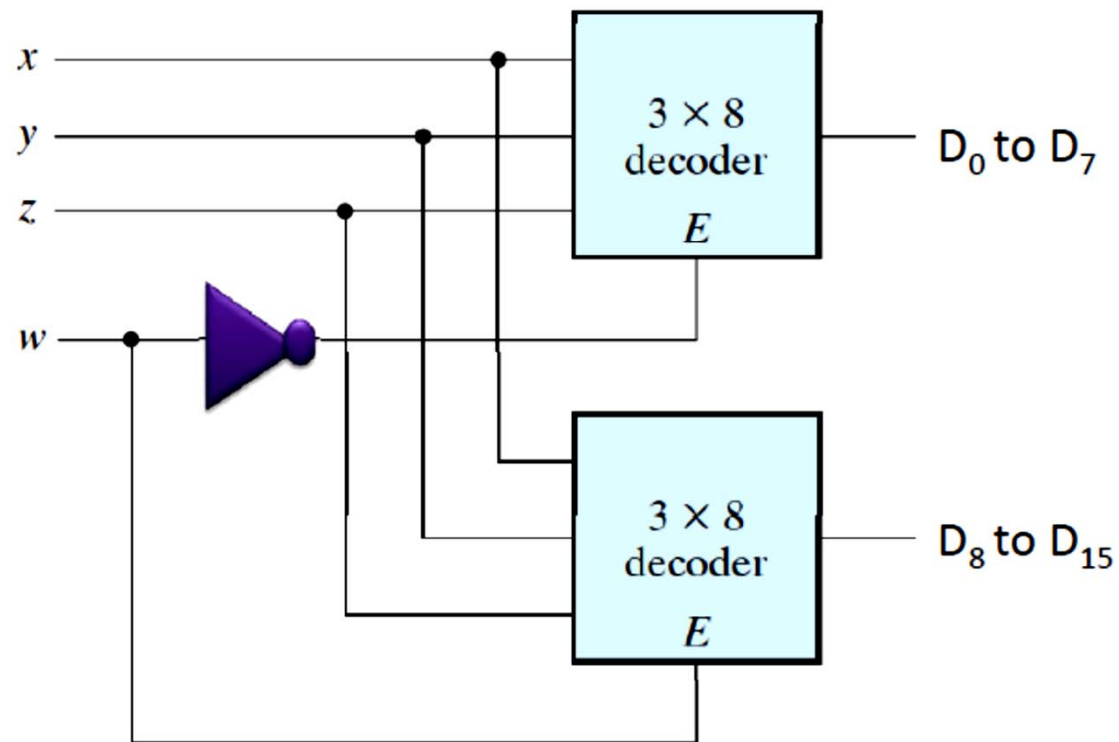4-to-16 Decoder using two 3-to-8 Decoders




 


Boolean Function Implementation using Decoders




 - Using a n -to- 2^n decoder and OR gates any functions of n variables can be implemented.
- Example:
 $S(x,y,z) = \Sigma(1,2,4,7)$, $C(x,y,z) = \Sigma(3,5,6,7)$
- Functions S and C can be implemented using a 3-to-8 decoder and two 4-input OR gates





Implementation of S and C

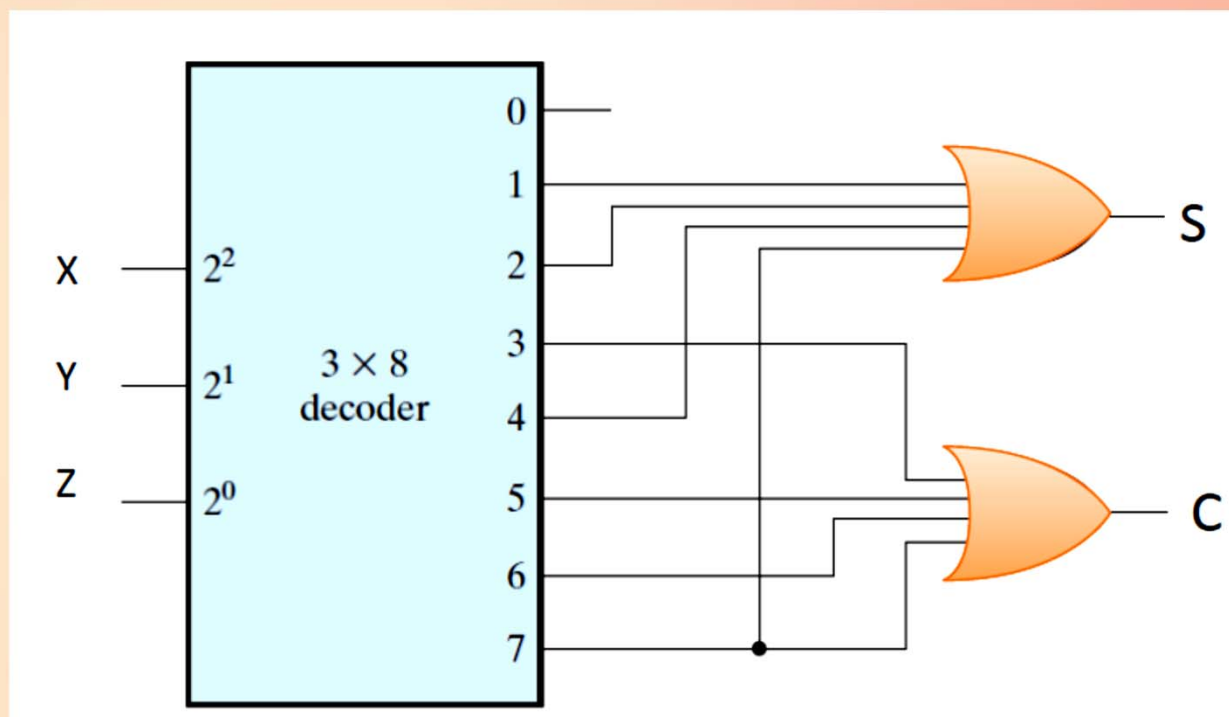

 


(Active Low Outputs)Decoder

 

 


 Configurable Function using Decoder & Memory





Any Function can be implemented

 Function depend on Memory
Elements, Direct correspondence to
Truth Table



Multiplexor (Mux)

  - Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
- **4** input mux → needs **2** select inputs to indicate which input to route through
- **8** input mux → **3** select inputs
- **N** inputs → $\log_2(N)$ selects
 - Like a rail yard switch




$$Mux \ 2 \times 1$$

$$Mux \ 4 \times 1$$


$$Mux \ 8 \times 1$$

$$Mux \ 2^k \times 1$$


$$k = 1, 2, 3, \dots$$

 


Mux Internal Design

 



2x1 mux

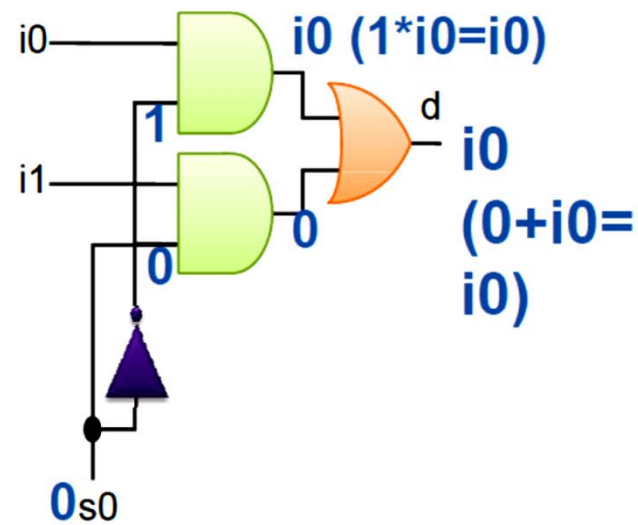

 


Mux Internal Design

 


 


Muxes Commonly Together -- N-bit Mux

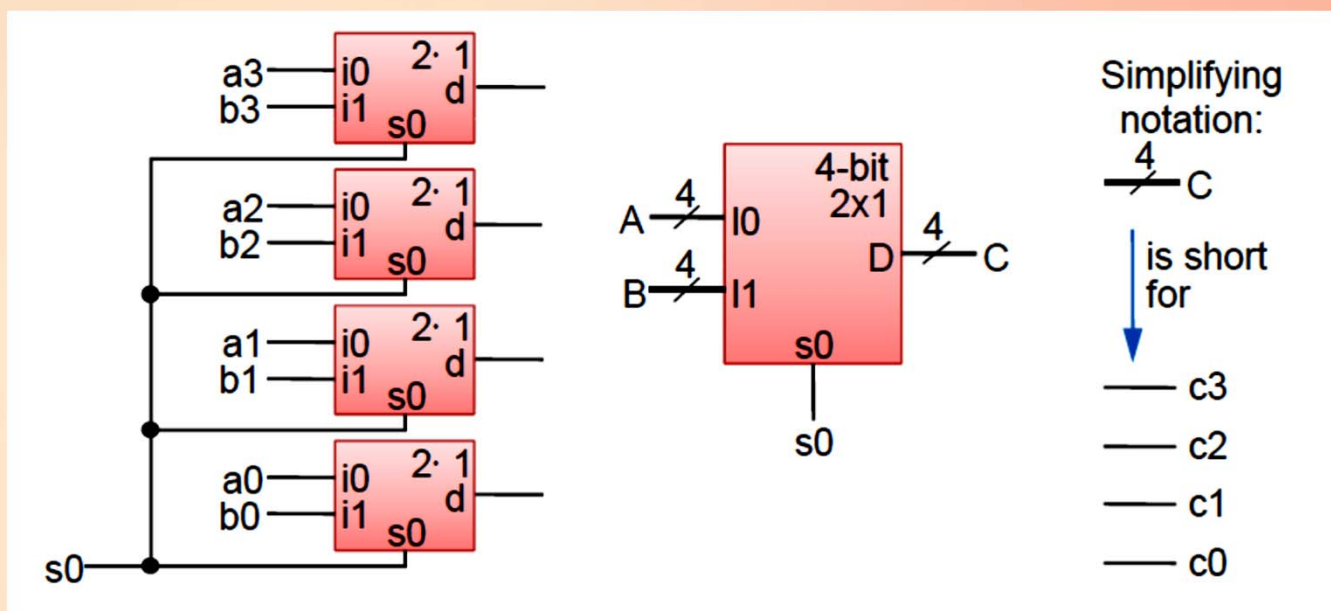


 - Ex: Two 4-bit inputs, A ($a_3 a_2 a_1 a_0$), and B ($b_3 b_2 b_1 b_0$)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B






Implementing logic Function using MUX

 


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 



Implementing logic Function using MUX

  


 


Implementing logic Function using MUX

  


 


(De Multiplexer) DEMUX

  


S	y ₀	y ₁
0	I	0
1	0	I

 


(De Multiplexer) DEMUX

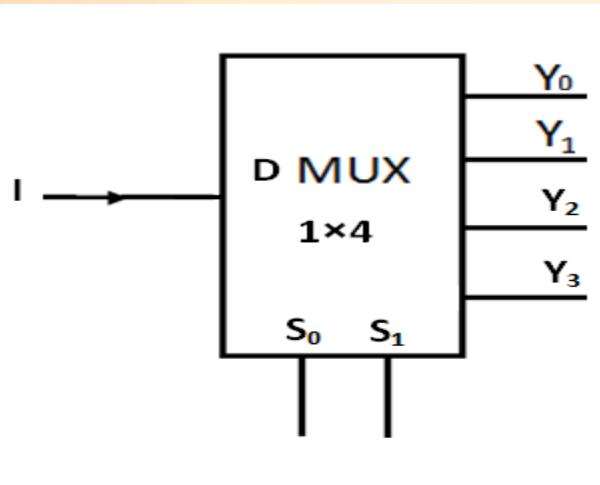


 



(De Multiplexer) DEMUX

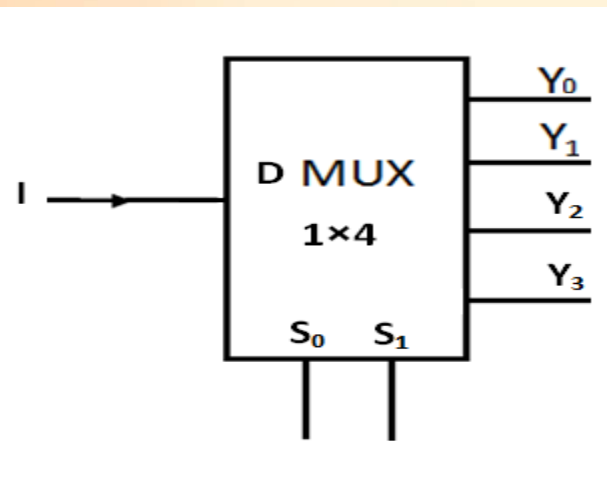


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

(De Multiplexer) DEMUX

  


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

Multiplexer



Multiplexer (MUX)

 

$$Mux \ 2 \times 1$$


$$Mux \ 4 \times 1$$

$$Mux \ 8 \times 1$$

·
·
·


$$Mux \ 2^k \times 1$$


$$k = 1, 2, 3,$$

 


Multiplexer

Four Input Multiplexer

 


 


Multiplexer

 


S	Y
0	I_0
1	I_1


Two-Input Multiplexer

  

$$Y = \bar{S}I_0 + SI_1$$

 


(De Multiplexer) DEMUX

 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 
$$F = S_0' S_1' . I_0 + S_0 S_1' . I_1 + S_0' S_1 . I_2 + S_0 S_1 . I_3$$




Four Input Multiplexer

 

 
$$F = S_0' S_1' . I_0 + S_0 S_1' . I_1 + S_0' S_1 . I_2 + S_0 S_1 . I_3$$





Four Input Multiplexer

 

 



Four Input Multiplexer

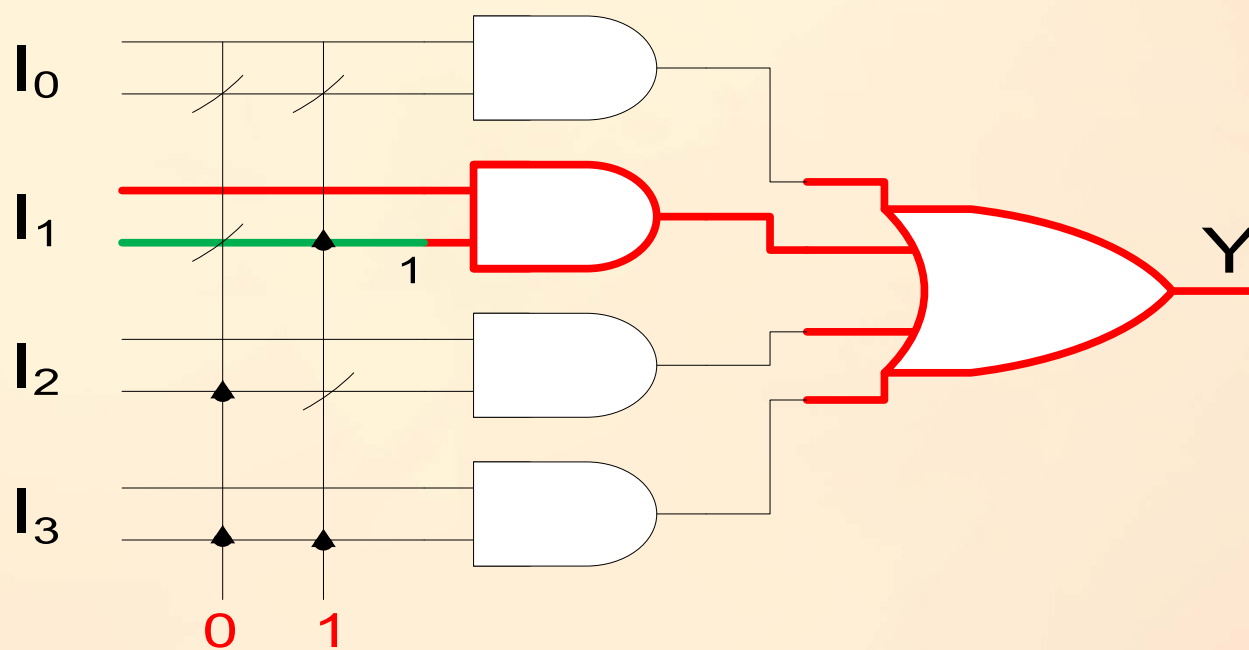

 



Four Input Multiplexer

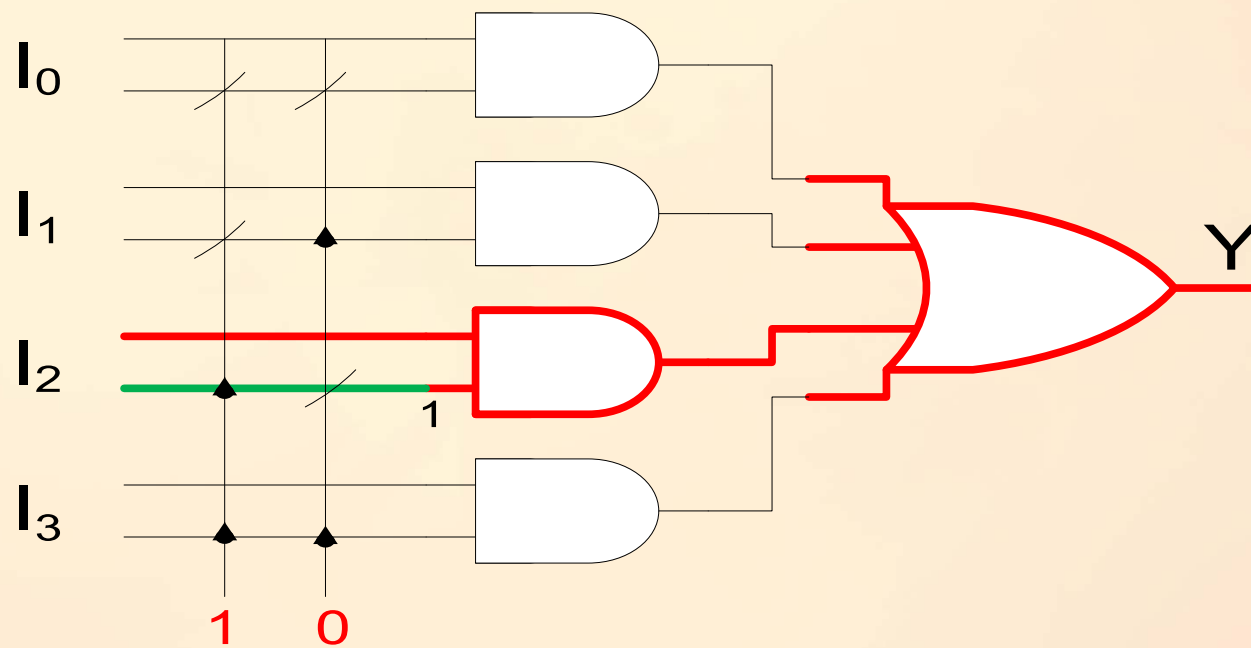

 


Four Input Multiplexer

 

 

(De Multiplexer) DEMUX

 

$D M u x 1 \times 2$

$D M u x 1 \times 4$

$D M u x 1 \times 8$


.

.


.

$D M u x 1 \times 2^k$

$k = 1, 2, 3,$

 


(De Multiplexer) DEMUX

 


S	Y ₀	Y ₁
0	0	I
1	I	0

$$Y_0 = S'I$$

$$Y_1 = SI$$

 

(De Multiplexer) DEMUX

 


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$Y_0 = S_0' S_1' . I$$


$$Y_1 = S_0 S_1' . I$$


$$Y_2 = S_0' S_1 . I$$

$$Y_3 = S_0 S_1 . I$$

 



(De Multiplexer) DEMUX

 

 



(De Multiplexer) DEMUX

 

 



(De Multiplexer) DEMUX

 

 



(De Multiplexer) DEMUX

 

 

(De Multiplexer) DEMUX

 


 


2 to 4 Decoder




The 2-to-4 Line Decoder/Demultiplexer

 

 

Decoder

 

$Dec\ 1 \times 2$

$Dec\ 2 \times 4$


$Dec\ 3 \times 8$

.

.

.

 
$Dec\ n \times 2^n \quad n = 1, 2, 3, \dots$




1-Input 2-Output Decoder




Dec 1*2

 

A	Y ₀	Y ₁
0	1	0
1	0	1

 

Decoder

 


B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
0	0	0	0	0	1

$$Y_0 = A' B'$$


$$Y_1 = A B'$$


$$Y_2 = A' B$$

$$Y_3 = A B$$

 



The 2 to 4 Line Decoder

 

 



The 2 to 4 Line Decoder

 

 



The 2 to 4 Line Decoder

 

 



The 2 to 4 Line Decoder

 

 



The 2 to 4 Line Decoder

 

 


(De Multiplexer) DEMUX

 


 


(De Multiplexer) DEMUX

 

A	Y_0	Y_1
0	1	0
1	0	1

 


(De Multiplexer) DEMUX

 


$$Y_1 = A$$

$$Y_0 = \overline{A}$$

A	Y ₀	Y ₁
0	1	0
1	0	1

 

The 2 to 4 Line Decoder

 


$$Y_1 = \bar{A}\bar{B}$$


$$Y_0 = A\bar{B}$$

$$Y_2 = \bar{A}B$$



$$Y_3 = AB$$


B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

 



The 2 to 4 Line Decoder

  

 


The 3 to 8 Line Decoder

 


 


The 3 to 8 Line Decoder

 


C	B	A	y ₀	y ₁	y ₂	y ₃	y ₄	y ₅	y ₆	y ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


The 3 to 8 Line Decoder

 


C	
0	1
1	2

 



8-to-1 MUX using 2-to-1 MUX

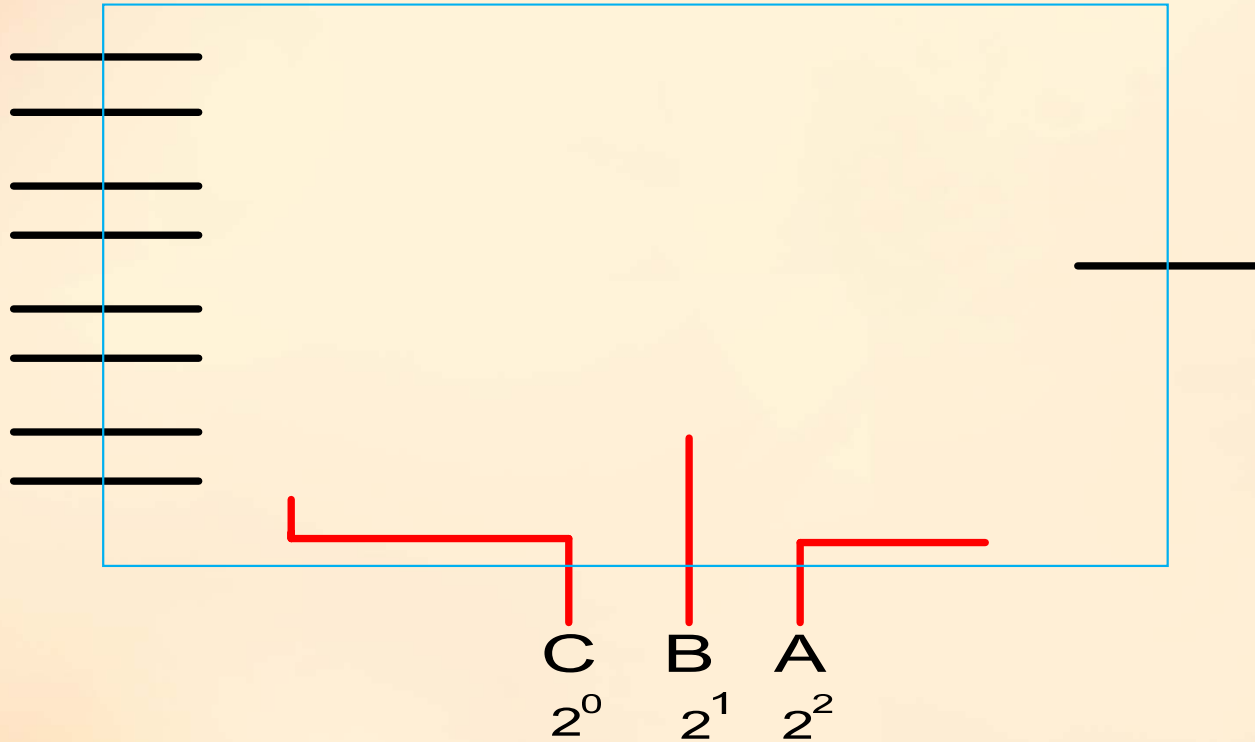

 



8-to-1 MUX using 2-to-1 MUX

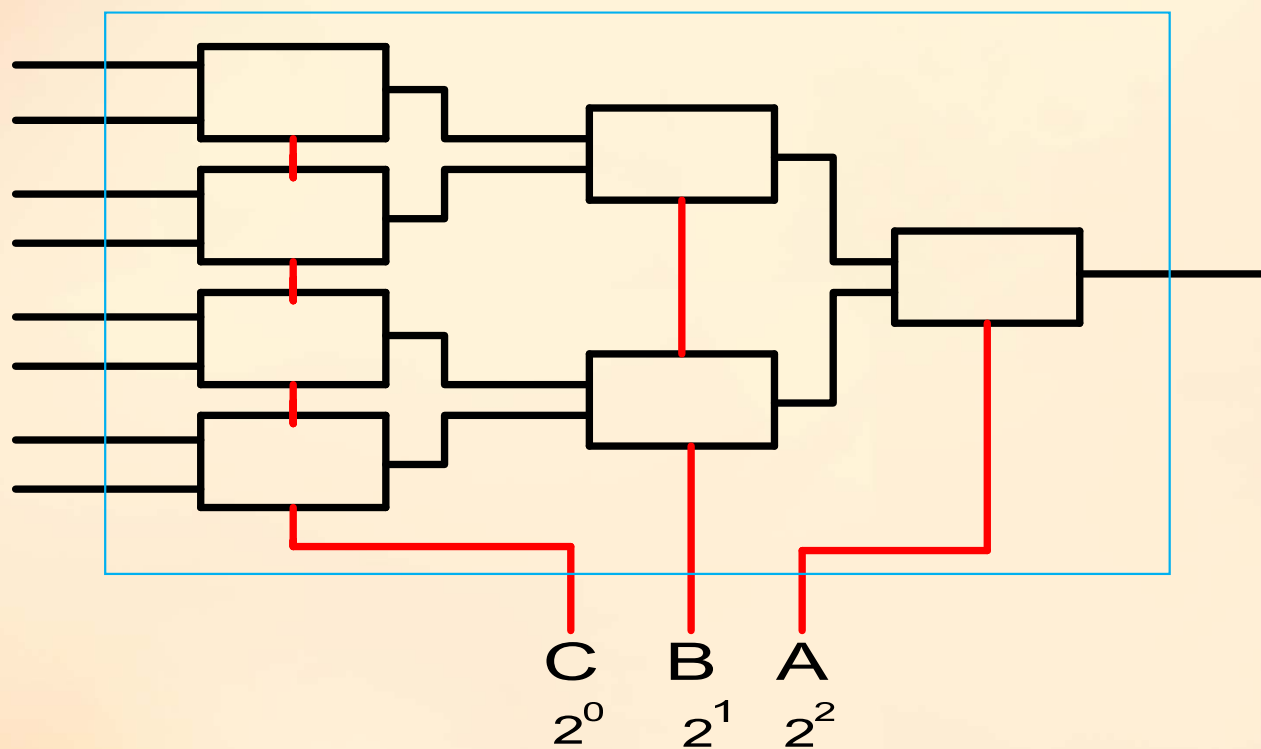

 


8-to-1 MUX using 2-to-1 MUX

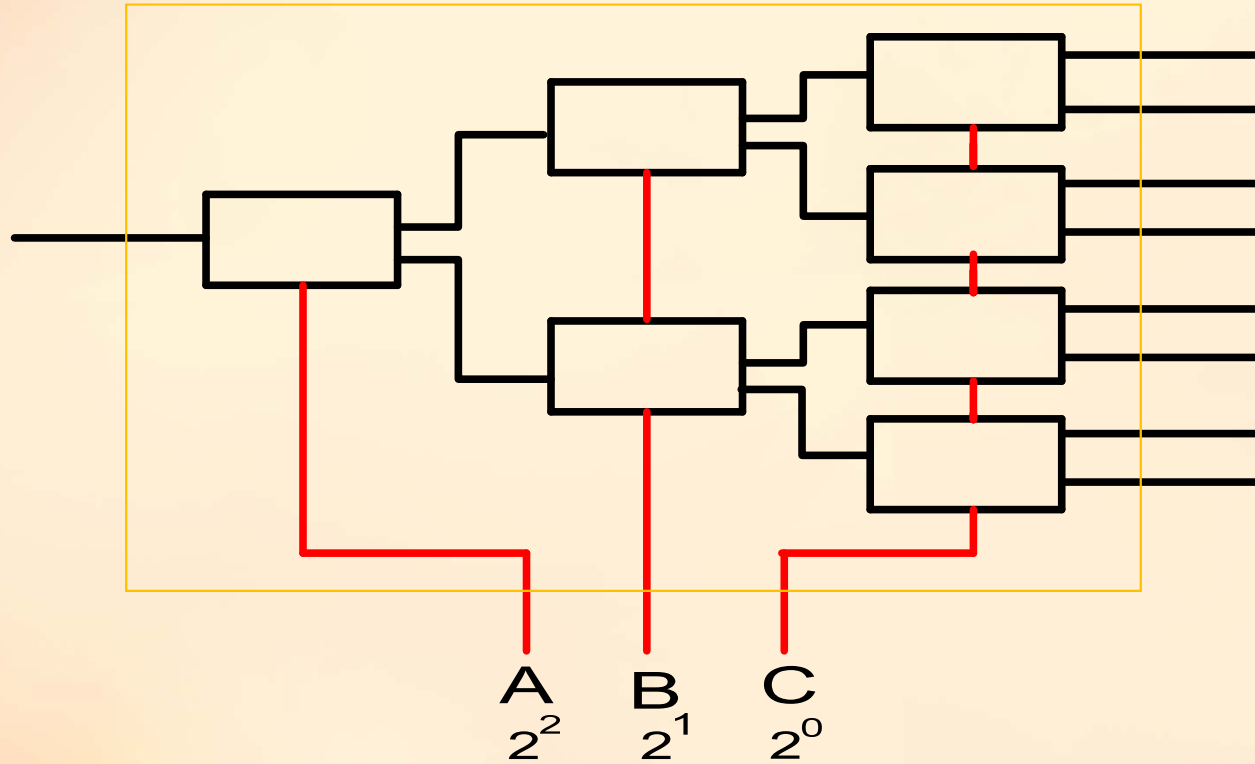

 


8-to-1 MUX using 2-to-1 MUX

 



$$\left. \begin{array}{c} \overline{B} \\ B \end{array} \right\} \overline{A}$$
 
$$\left. \begin{array}{c} \overline{B} \\ B \end{array} \right\} A$$



4-to-16 Decoder using 2-to-4 Decoders

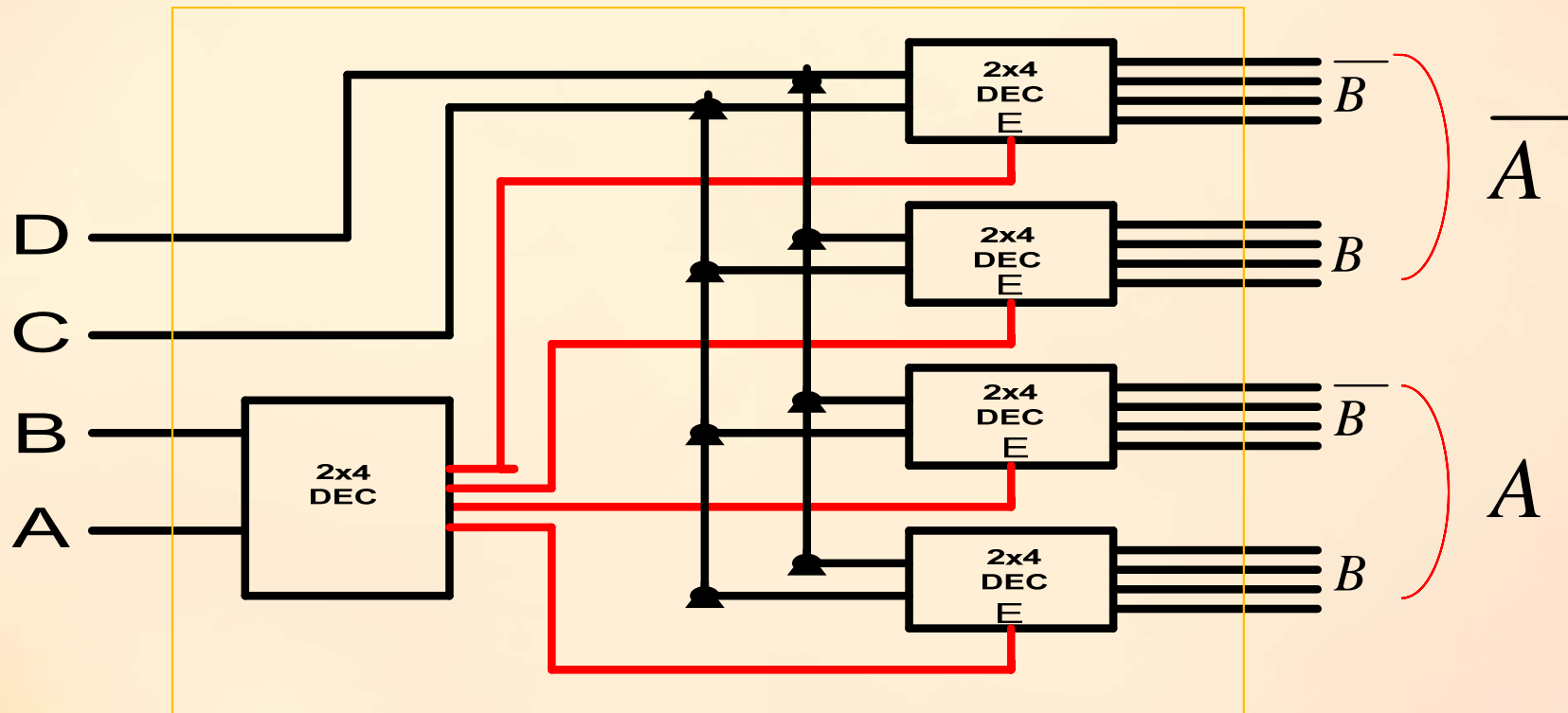

 

MUX and DEC Design

E#1: 4-to-1 Multiplexer using 2-to-1 Multiplexers

E#2: 8-to-1 Multiplexer using 2-to-1 Multiplexers

E#3: 16-to-1 Multiplexer using 2-to-1 Multiplexers


E#4: 64-to-1 Multiplexer using 2-to-1 Multiplexers

E#5: 16-to-1 Multiplexer using 4-to-1 Multiplexers


E#6: 32-to-1 Multiplexer using 4-to-1 Multiplexers


E#6: 3-to-8 Decoder using 2-to-4 Decoders with Enable

 E#7: 4-to-16 Decoder using 2-to-4 Decoders with Enable





MUX design

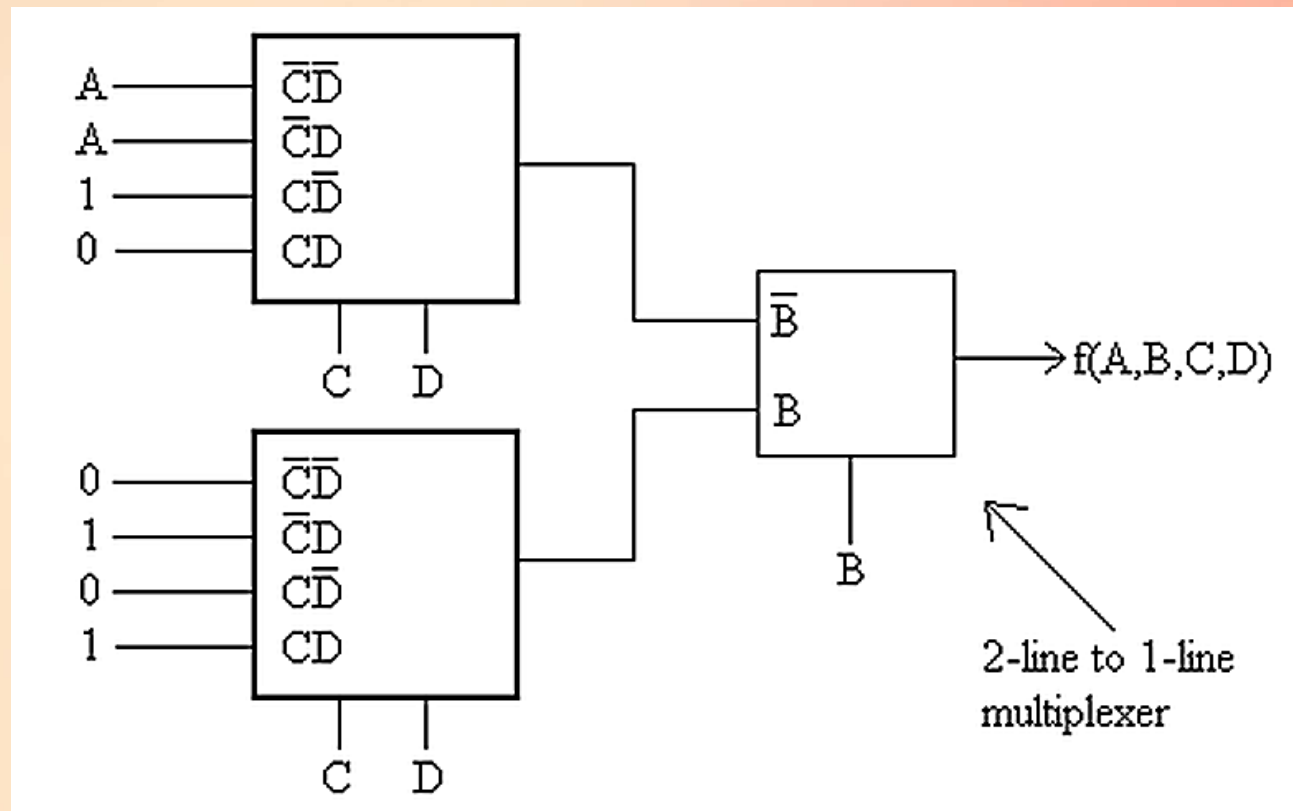

 



Implementing logic Function using MUX

 

 


Implementing logic Function using MUX

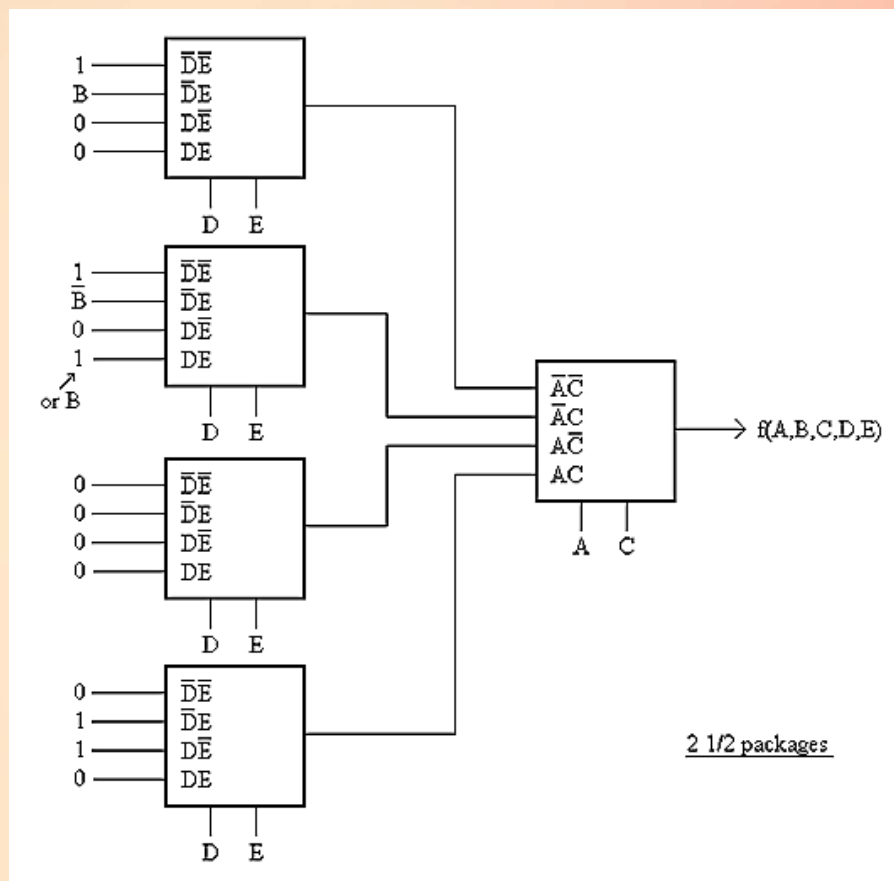


 

Implementing logic Function using MUX
 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$




 

Boolean Function Implementation using Multiplexers



 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$



D	0	1	0	1	0	1	0	1
C	0	0	1	1	0	0	1	1
B	0	0	0	0	1	1	1	1


	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
A'								
A								

 


Boolean Function Implementation using Multiplexers


 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$




B	0	1	0	1	0	1	0	1
D	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1
	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
C'	0	4	1	5	8	12	9	13
C	2	6	3	7	10	14	11	15

 

Boolean Function Implementation using Multiplexers


 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$




B	0	1	0	1	0	1	0	1
D	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1
	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
C'	0	4	1	5	8	12	9	13
C	2	6	3	7	10	14	11	15

Boolean Function Implementation using Multiplexers


 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$




B	0	1	0	1	0	1	0	1
D	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1
	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
C'	0	4	1	5	8	12	9	13
C	2	6	3	7	10	14	11	15


Boolean Function Implementation using Multiplexers


 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$




B	0	1	0	1	0	1	0	1
D	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1
	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
C'	0	4	1	5	8	12	9	13
C	2	6	3	7	10	14	11	15
	C'	C'	1	C'	1	C'	1	1

 


Boolean Function Implementation using Multiplexers



 
$$Y = \sum m(0, 1, 4, 5, 8, 9, 12, 13, 15) + d(3, 10, 11)$$



B	0	1	0	1	0	1	0	1
D	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1
	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
C'	0	4	1	5	8	12	9	13
C	2	6	3	7	10	14	11	15
	C'	C'	1	C'	1	C'	1	1

 

 Boolean Function Implementation using Multiplexers



	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15



Thank You