

Other Gates

Circuit Optimization


- **Goal: To obtain the simplest implementation for a given function**
- **Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm**
- **Optimization requires a cost criterion to measure the simplicity of a circuit**
- **Distinct cost criteria we will use:**
 - **Literal cost (L)**
 - **Gate input cost (G)**
 - **Gate input cost with NOTs (GN)**

Literal Cost

- **Literal** – a variable or its complement
- **Literal cost** – the number of literal appearances in a Boolean expression corresponding to the logic circuit diagram
- **Examples:**
 - $F = BD + A\bar{B}C + A\bar{C}\bar{D}$ $L = 8$
 - $F = BD + A\bar{B}C + A\bar{B}\bar{D} + AB\bar{C}$ $L = 11$
 - $F = (A + B)(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$ $L = 10$
 - Which solution is best? **The first solution**

Cost Criteria (continued)

 
- Example 1: $\nabla \nabla$ $GN = G + 2 = 9$
- $F = \overset{\bullet}{A} + \overset{\bullet}{B} \underset{\blacksquare}{C} + \overset{\bullet}{\bar{B}} \underset{\blacksquare}{\bar{C}}$ $L = 5$
- $G = \textcolor{teal}{L} + \textcolor{blue}{2} = 7$




- L (literal count) counts the AND inputs and the single literal OR input.
- G (gate input count) adds the remaining OR gate inputs
- GN(gate input count with NOTs) adds the inverter inputs

AND/OR Two-level Circuit optimization

 - The two implementations for F are shown below – it is quite apparent which is simpler!




$$F = \bar{Y} + \bar{X}Y\bar{Z} + XY$$

 

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

Multiple-Level Optimization

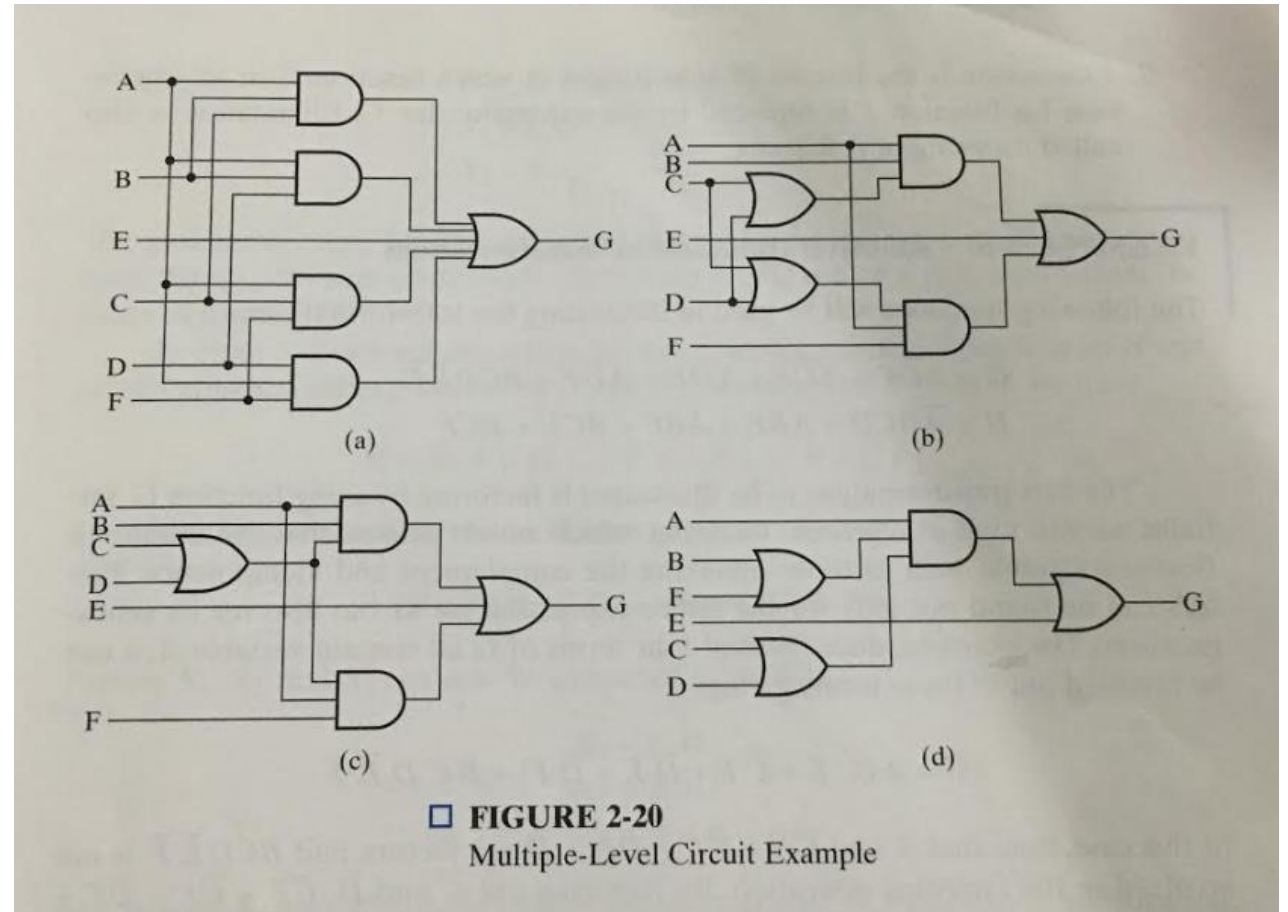- Multiple-level circuits - circuits that are not two-level (with or without input and/or output inverters)
- Multiple-level circuits can have reduced gate input cost compared to two-level (SOP and POS) circuits
- Multiple-level optimization is performed by applying transformations to circuits represented by equations while evaluating cost




Other Gate Types

- Why?
 - Implementation feasibility and low cost
 - Power in implementing Boolean functions
 - Convenient conceptual representation
- Gate classifications
 - Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).
 - Complex gate - a gate that requires more than one primitive operation type for its description
- Primitive gates will be covered first

Buffer

 - A buffer is a gate with the function $F = X$:




- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.

NAND Gate

- The basic NAND gate has the following symbol, illustrated for three inputs:

- AND-Invert (NAND)

 


X	Y	F
0	0	1
0	1	1
1	0	1
1	1	0

- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.

NAND Gates (continued)

 - Applying DeMorgan's Law gives Invert-OR (NAND)






X	Y	\overline{X}	\overline{Y}	$F = \overline{X} + \overline{Y}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

- This NAND symbol is called Invert-OR, since inputs are inverted and then ORed together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.

NAND Gates (universal gate)

   
- *Universal gate* - a gate type that can implement any Boolean function.
- The NAND gate is a universal gate as shown in Figure 2-24 of the text.



NOR Gate

- The basic NOR gate has the following symbol, illustrated for three inputs:

- OR-Invert (NOR)

 


X	Y	F
0	0	1
0	1	0
1	0	0
1	1	0

- NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert. The small circle (“bubble”) represents the invert function.

NOR Gate (continued)

 - Applying DeMorgan's Law gives Invert-AND (NOR)






X	Y	\bar{X}	\bar{Y}	$F = \bar{X}\bar{Y}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

- This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.

NOR Gate (universal gate)

   - ❑ **NAND, NOR universal gates: can accomplish any of the basic operations and produce inverter, OR gate or AND gate**
- ❑ **The non-inverting gates aren't: they can't produce an invert.**



Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The XOR function may be:
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

Exclusive OR/ Exclusive NOR

- Uses for the XOR and XNORs gate include:

- Adders/subtractors/multipliers
- Counters/incrementers/decrementers
- Parity generators/checkers

- Definitions

- The XOR function is:

$$X \oplus Y = X \bar{Y} + \bar{X} Y$$

- The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is:

$$\overline{X \oplus Y} = X Y + \bar{X} \bar{Y}$$

- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$\overline{(X \oplus Y)}$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:
X OR Y, but NOT BOTH
- the XNOR function is also known as the *equivalence* function, because

It is equals to 1 if and only if X is equivalent to Y

XOR/XNOR (Continued)

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$\mathbf{X \oplus Y \oplus Z = \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + X \overline{Y} \overline{Z} + X Y Z}$$

- The complement of the odd function is the even function.
- The XOR identities:

$$\mathbf{X \oplus 0 = X}$$

$$\mathbf{X \oplus 1 = \overline{X}}$$

$$\mathbf{X \oplus X = 0}$$


$$\mathbf{X \oplus \overline{X} = 1}$$

$$\mathbf{X \oplus Y = Y \oplus X}$$


$$\mathbf{(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z}$$

Symbols For XOR and XNOR

- XOR symbol:

 


- XNOR symbol:

 


- Shaped symbols exist only for two inputs

XOR Implementations

 - The simple SOP implementation uses the following structure:




- A NAND only implementation is:

 

 
Example: Odd Function Implementation

- Design a 3-input odd function $F = X \oplus Y \oplus Z$ with 2-input XOR gates
- Factoring, $F = (X \oplus Y) \oplus Z$
- The circuit:



 Example: Even Function Implementation

- Design a 4-input odd function $F = W \oplus X \oplus Y \oplus Z$ with 2-input XOR and XNOR gates
- Factoring, $F = (W \oplus X) \oplus (Y \oplus Z)$
- The circuit:



Hi-Impedance Outputs


- Logic gates introduced thus far
 - have 1 and 0 output values,
 - cannot have their outputs connected together, and
 - transmit signals on connections in only one direction.
- Three-state logic adds a third logic value, Hi-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.

Hi-Impedance Outputs (continued)

- What is a Hi-Z value?
 - The Hi-Z value behaves as an open circuit
 - This means that, looking back into the circuit, the output appears to be disconnected.
 - It is as if a switch between the internal circuitry and the output has been opened.
- Hi-Z may appear on the output of any gate, but we restrict gates to:
 - a 3-state buffer, or
 - Optional: a transmission gate (See Reading Supplement: More on CMOS Circuit-Level Design),each of which has one data input and one control input.

The 3-State Buffer

 - For the symbol and truth table, IN is the data input, and EN, the control input.
- For EN = 0, regardless of the value on IN (denoted by X), the output value is Hi-Z.
- For EN = 1, the output value follows the input value.
- Variations:
 - Data input, IN, can be inverted
 - Control input, EN, can be inverted by addition of “bubbles” to signals.



Truth Table

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1