



TEXAS TECH UNIVERSITY™

Department of Electrical and Computer Engineering




ECE 2372, Spring 2017
(Modern Digital System Design)

Instructor:

Dr. Tooraj Nikoubin

Review for SECOND TEST

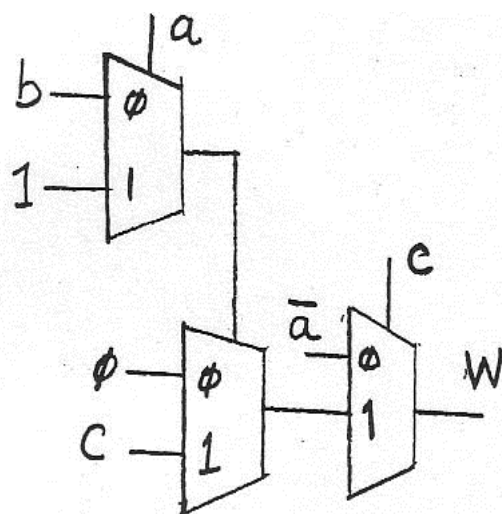


$$\bar{a}b + a \oplus b$$


$$\bar{a} \oplus c + bc$$


$$ab + \bar{a}c + a\bar{c}$$

$$\bar{a}\bar{c} + c(a+b+c)$$

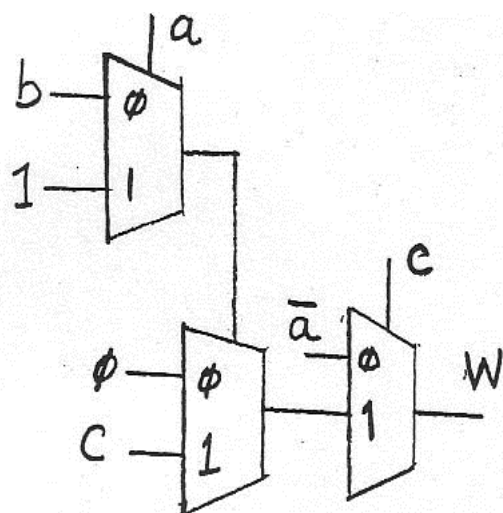

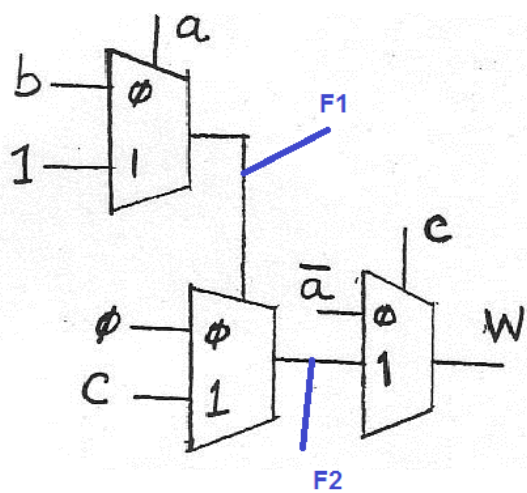
$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a + b + c) \end{aligned}$$




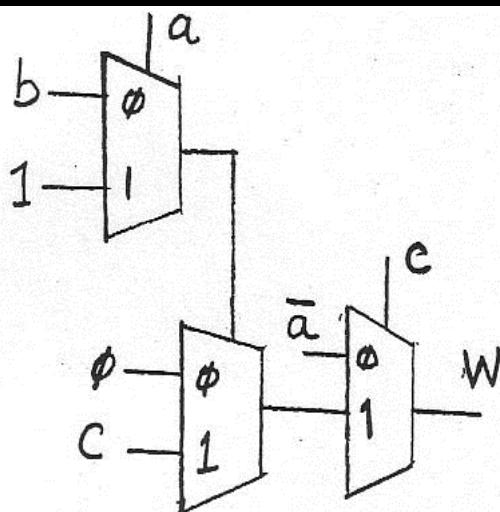

$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a+b+c) \end{aligned}$$

$$F1 = \bar{a}b + a = a + b$$

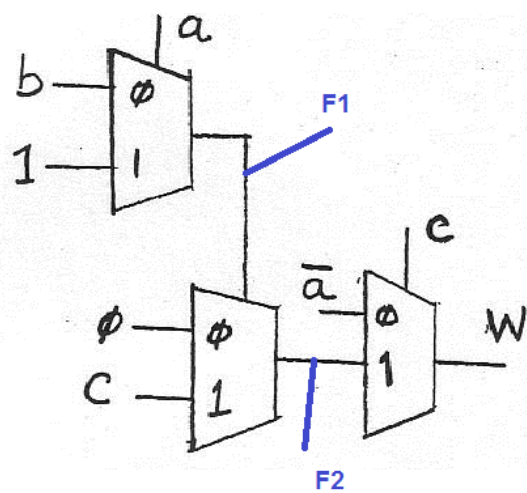


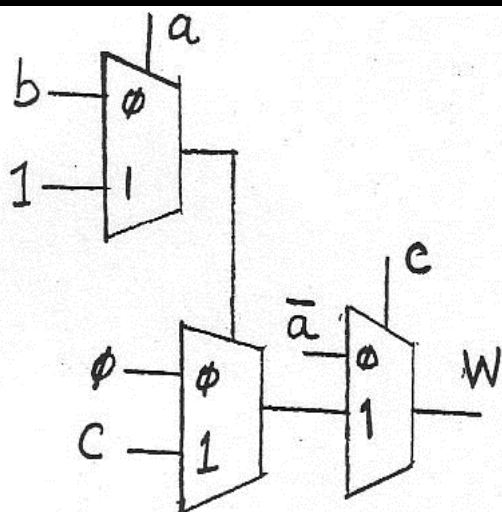


$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a+b+c) \end{aligned}$$

$$F1 = \bar{a}b + a = a + b$$

$$F2 = F1.c = c(a + b)$$

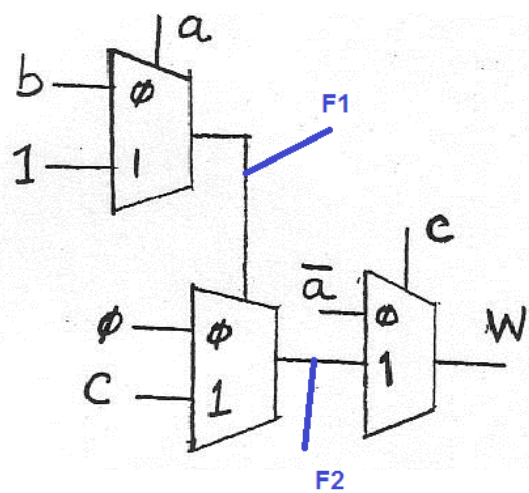

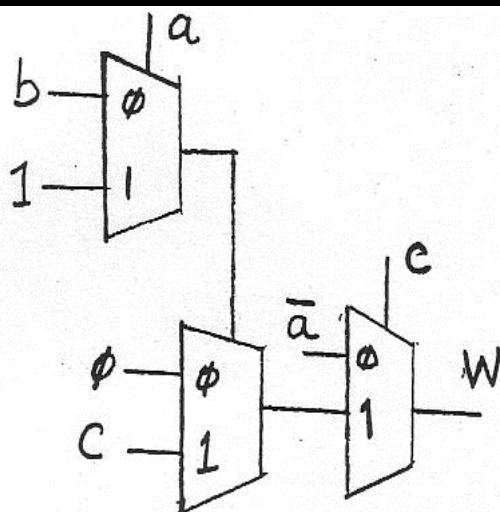



$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a+b+c) \end{aligned}$$

$$F1 = \bar{a}b + a = a + b$$

$$F2 = F1.c = c(a + b)$$
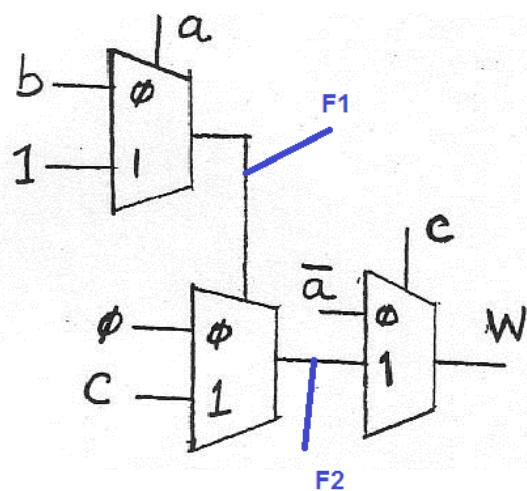
$$W = \bar{a}\bar{c} + cF2 = \bar{a}\bar{c} + c[c(a + b)]$$



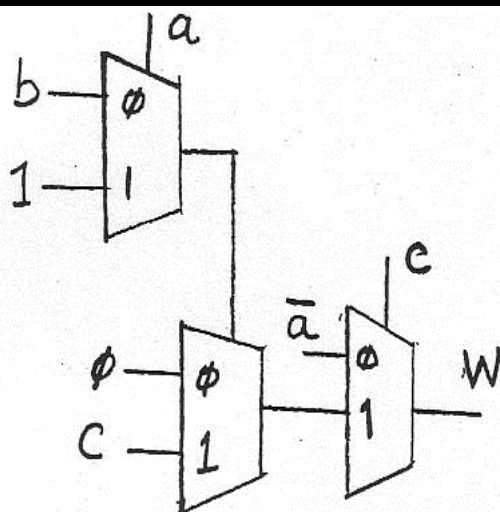


$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a + b + c) \end{aligned}$$


$$F1 = \bar{a}b + a = a + b$$

$$F2 = F1 \cdot c = c(a + b)$$

$$W = \bar{a}\bar{c} + cF2 = \bar{a}\bar{c} + c[c(a + b)]$$

$$W = \bar{a}\bar{c} + ac + bc$$

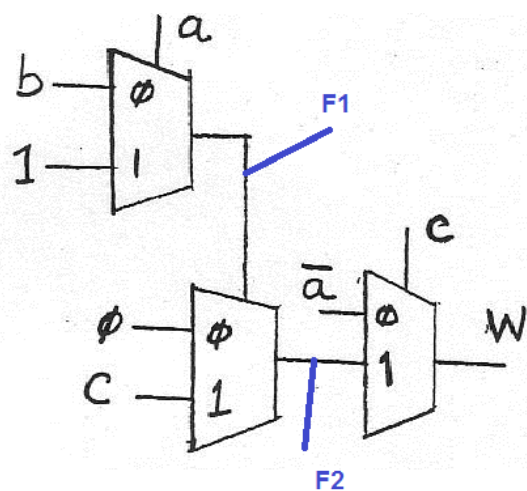

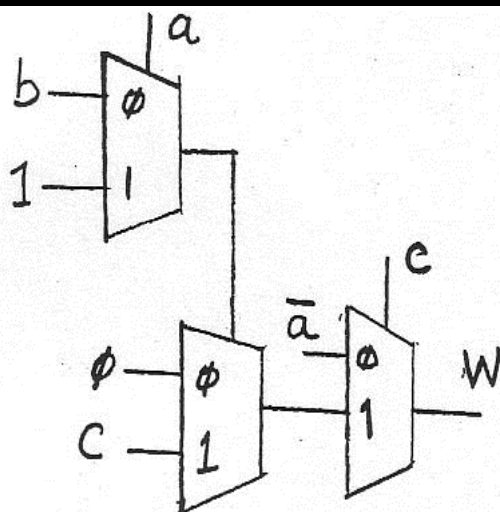

$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a + b + c) \end{aligned}$$


$$F1 = \bar{a}b + a = a + b$$


$$F2 = F1 \cdot c = c(a + b)$$

$$W = \bar{a}\bar{c} + cF2 = \bar{a}\bar{c} + c[c(a + b)]$$

$$W = \bar{a}\bar{c} + ac + bc$$

$$W = bc + (a \odot c)$$

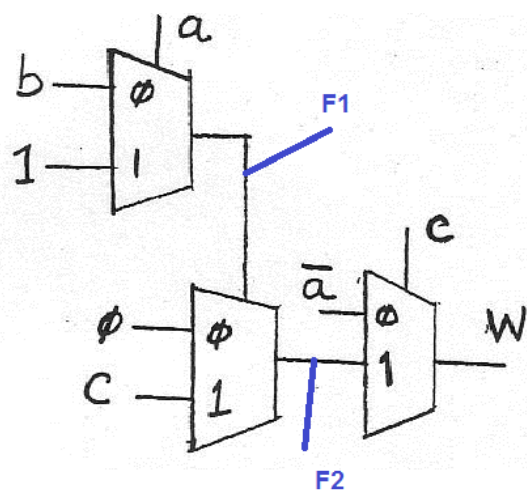

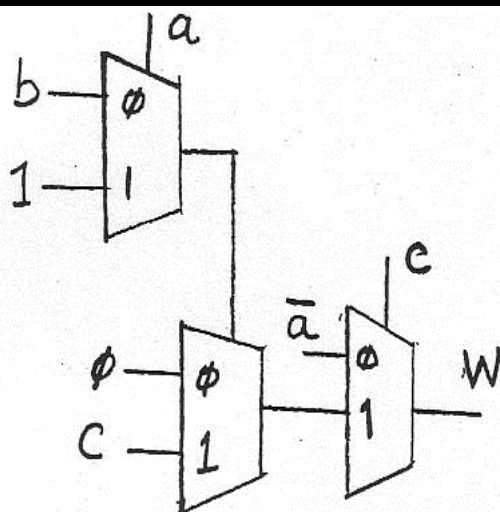

$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a + b + c) \end{aligned}$$

$$F1 = \bar{a}b + a = a + b$$


$$F2 = F1.c = c(a + b)$$


$$W = \bar{a}\bar{c} + cF2 = \bar{a}\bar{c} + c[c(a + b)]$$

$$W = \bar{a}\bar{c} + ac + bc$$

$$W = bc + (a \odot c)$$

$$W = bc + (\bar{a} \oplus c)$$

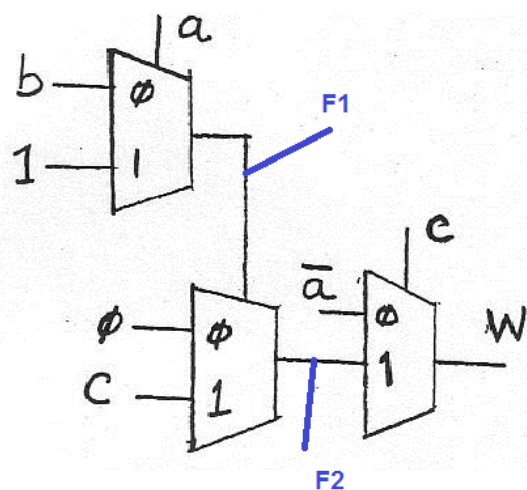

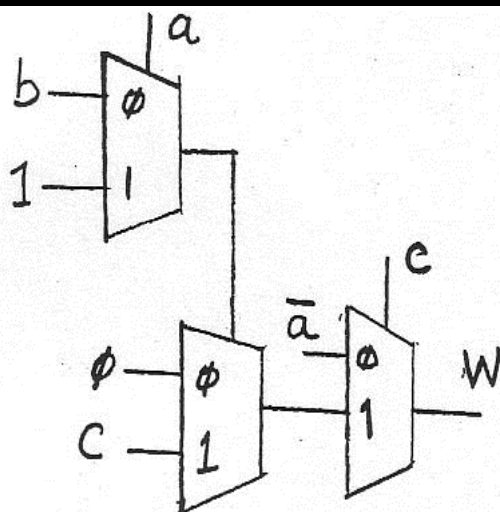

$$\begin{aligned} &\bar{a}b + a \oplus b \\ &\bar{a} \oplus c + bc \\ &ab + \bar{a}c + a\bar{c} \\ &\bar{a}\bar{c} + c(a+b+c) \end{aligned}$$

$$F1 = \bar{a}b + a = a + b$$


$$F2 = F1 \cdot c = c(a + b)$$

$$W = \bar{a}\bar{c} + cF2 = \bar{a}\bar{c} + c[c(a + b)]$$


$$W = \bar{a}\bar{c} + ac + bc$$

$$W = bc + (a \odot c)$$


$$W = bc + (\bar{a} \oplus c)$$

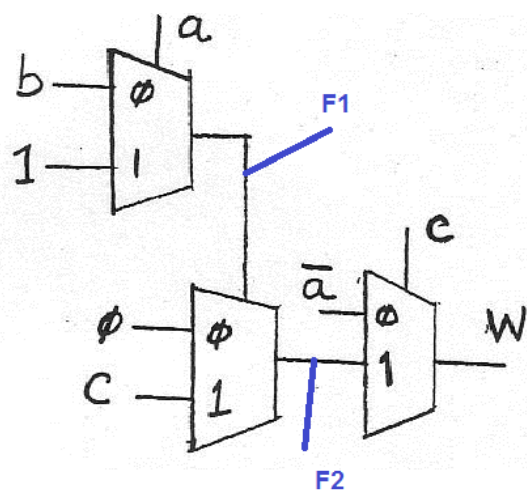

(2)

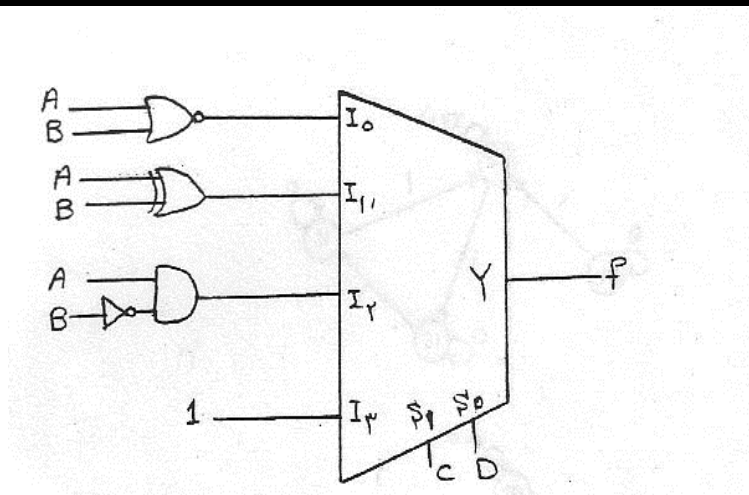

$$F = \sum_m$$

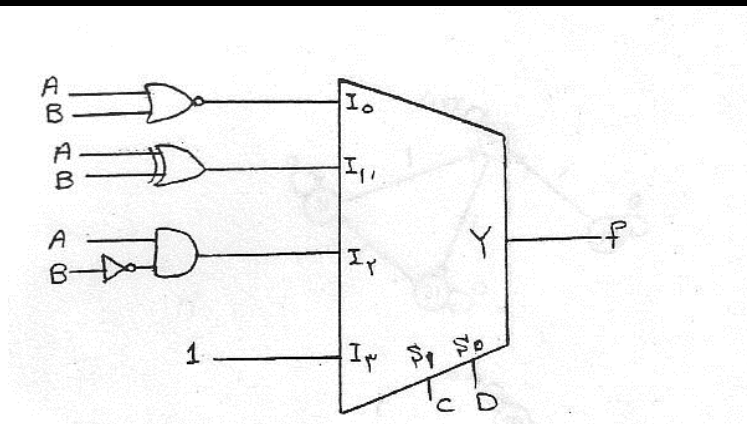


$$I_0 = \overline{A + B} = \overline{A}\overline{B}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = A\overline{B}$$

$$I_3 = 1$$

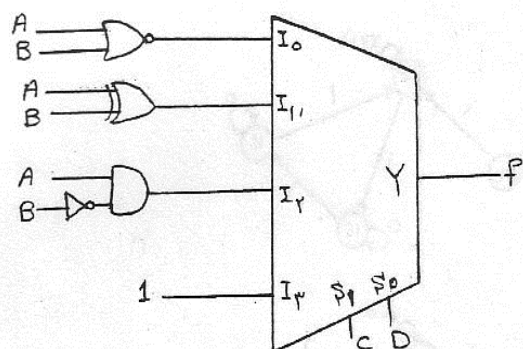


$$I_0 = \overline{A} + \overline{B} = \overline{A}\overline{B}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = A\overline{B}$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

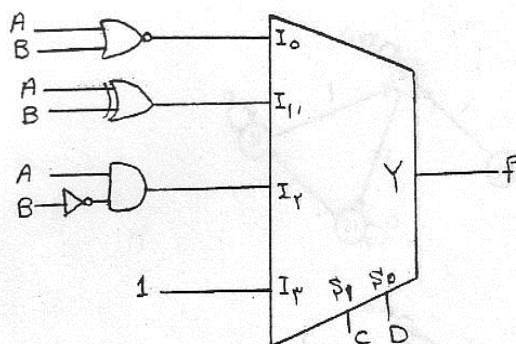


$$I_0 = \overline{A} + \overline{B} = \overline{AB}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = AB$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

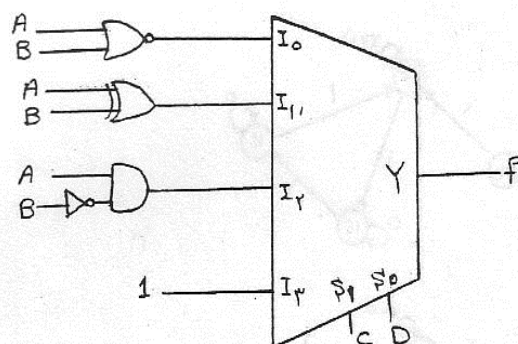


$$I_0 = \overline{A} + \overline{B} = \overline{AB}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = A\overline{B}$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

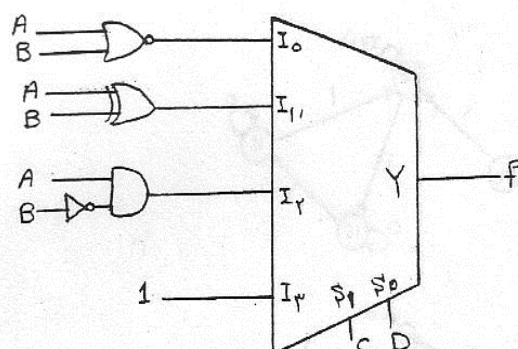


$$I_0 = \overline{A} + \overline{B} = \overline{AB}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = AB$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

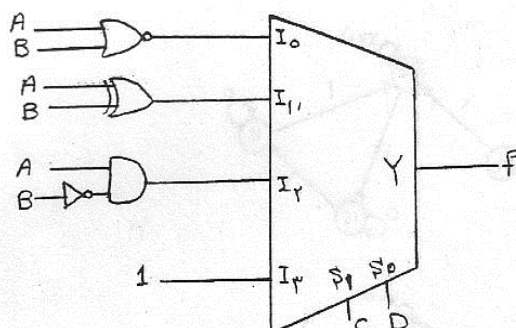


$$I_0 = \overline{A} + \overline{B} = \overline{A}\overline{B}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = A\overline{B}$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

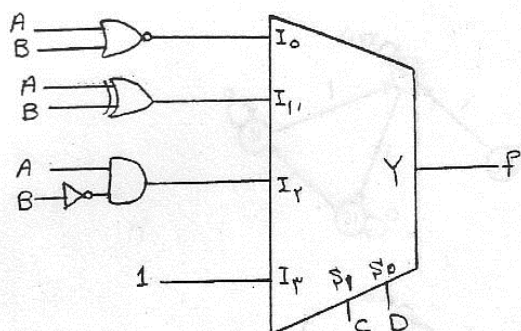

$$I_0 = \overline{A + B} = \overline{A}\overline{B}$$


$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = AB$$

$$I_3 = 1$$

D	0	1	0	1
C	0	0	1	1
AB				
00	0	1	2	3
01	4	5	6	7
11	12	13	14	15
10	8	9	10	11

$$Y = \sum m(0, 3, 5, 9, 10, 11, 15)$$

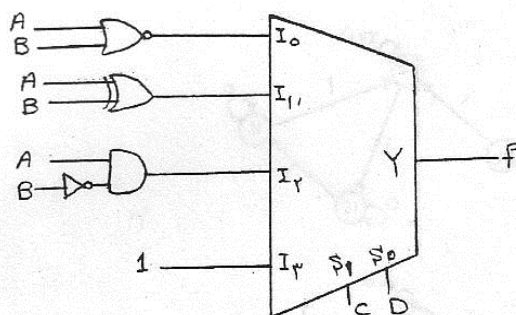

$$I_0 = \overline{A + B} = \overline{A}\overline{B}$$

$$I_1 = A \oplus B = A\overline{B} + \overline{A}B$$

$$I_2 = A\overline{B}$$

$$I_3 = 1$$

	D	0	1	0	1
	C	0	0	1	1
AB					
00		0	1	2	3
01		4	5	6	7
11		12	13	14	15
10		8	9	10	11

$$Y = \sum m(0, 3, 5, 9, 10, 11, 15)$$

(2)




$$I_0 = b + \bar{d}$$

$$I_1 = \bar{d}$$

$$I_2 = bd$$

$$I_3 = b$$

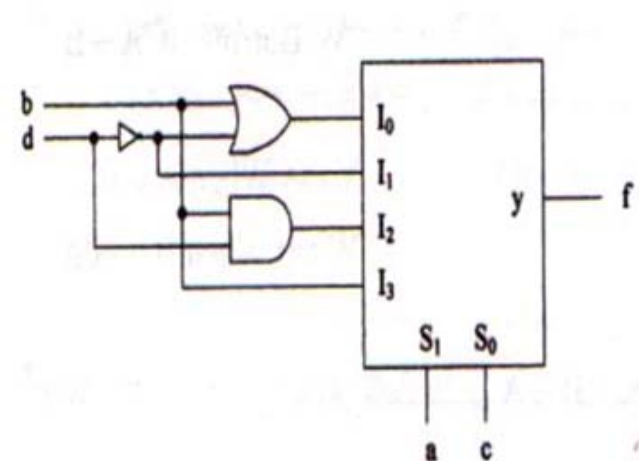




$$I_0 = b + \bar{d}$$

$$I_1 = \bar{d}$$

$$I_2 = bd$$

$$I_3 = b$$

		c	0	1	0	1
		a	0	0	1	1
bd	00	0	2	8	10	
	01	1	3	9	11	
	11	5	7	13	15	
	10	4	6	12	14	

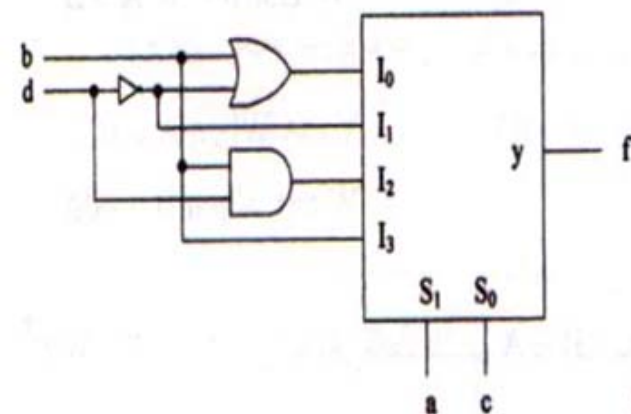




$$I_0 = b + \bar{d}$$


$$I_1 = \bar{d}$$

$$I_2 = bd$$

$$I_3 = b$$

		c	0	1	0	1
		a	0	0	1	1
bd	00	0	2	8	10	
	01	1	3	9	11	
	11	5	7	13	15	
	10	4	6	12	14	

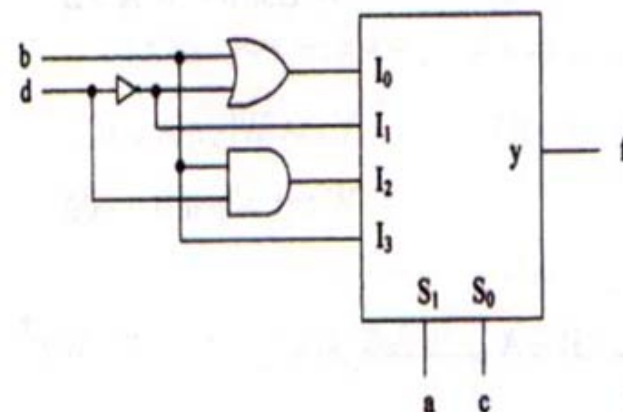

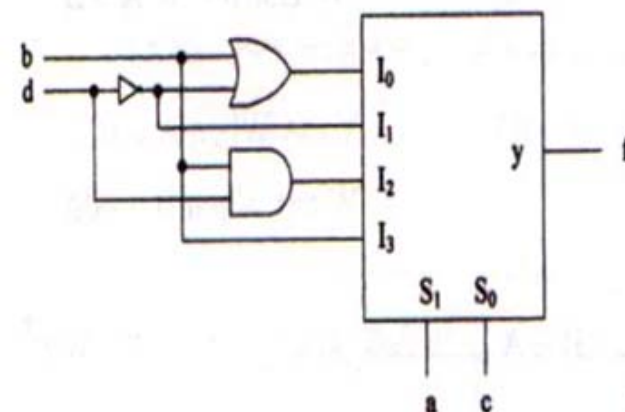

$$I_0 = b + \bar{d}$$

$$I_1 = \bar{d}$$


$$I_2 = bd$$

$$I_3 = b$$


		c			
		0	1	0	1
bd	a	0	0	1	1
	00	0	2	8	10
	01	1	3	9	11
	11	5	7	13	15
	10	4	6	12	14

$$Y = \sum m(0, 2, 4, 5, 6, 13, 14, 15)$$

(2)

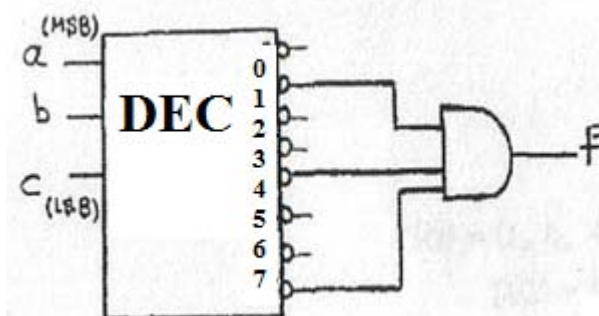

$$Y = \sum m(0, 2, 3, 5, 6)$$

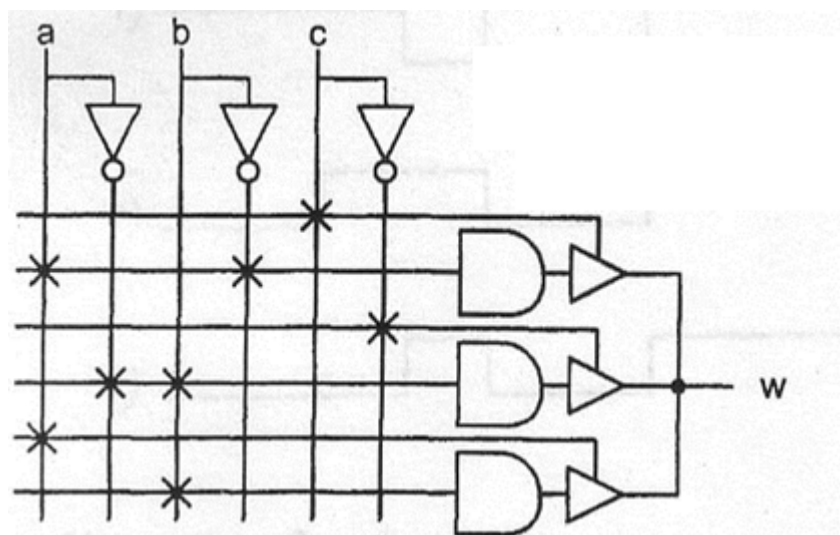


a	0	0	0	0	1	1	1	1	2)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x	

a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	1	0	1	1	1	1	1	1	

a	0	0	0	0	1	1	1	1	4)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0	

a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	1	x	1	

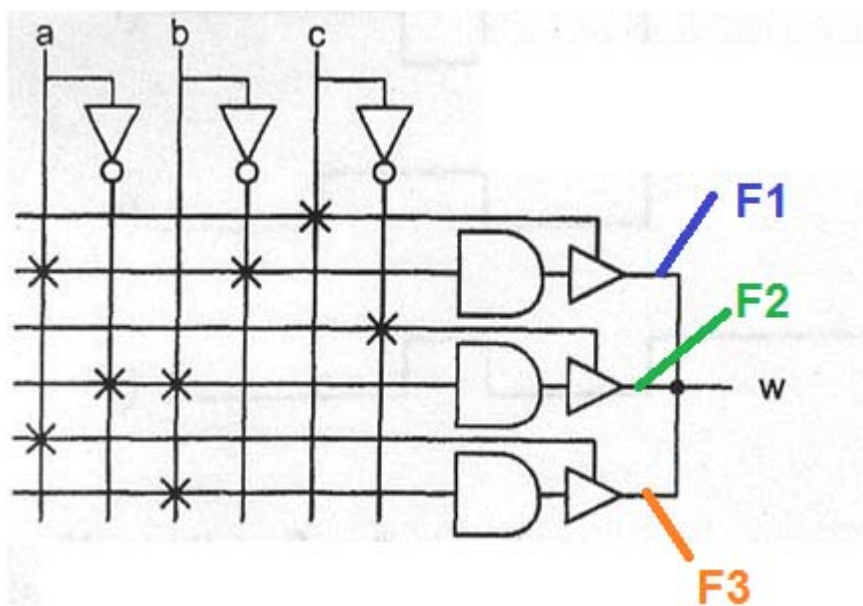

a	0	0	0	0	1	1	1	1	2)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x	


a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	1	0	1	1	1	1	1	1	

a	0	0	0	0	1	1	1	1	4)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0	

a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	1	x	1	



$$F1 = a\bar{b}c$$

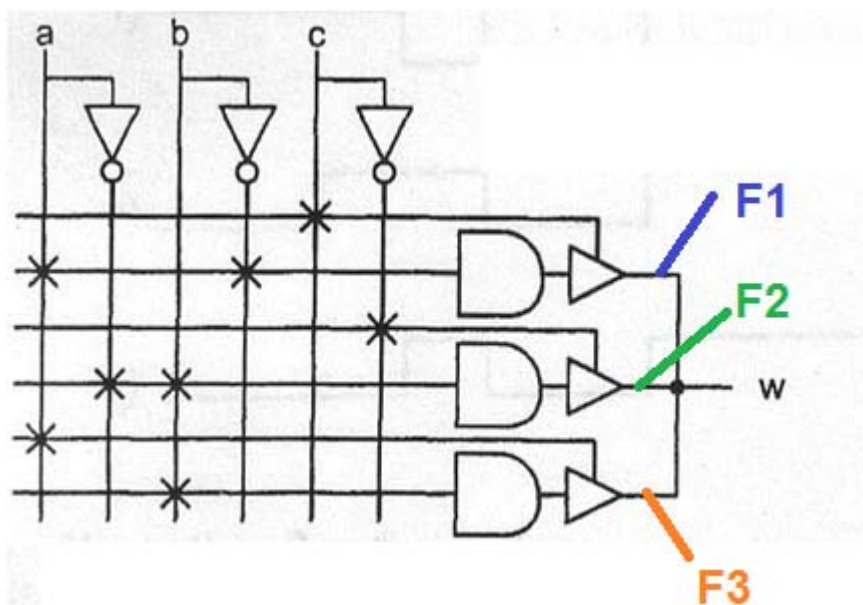


a	0	0	0	0	1	1	1	1	2)	a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x		w	1	0	1	1	1	1	1	1	

a	0	0	0	0	1	1	1	1	4)	a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0		w	0	0	1	0	0	1	x	1	



$$F1 = a\bar{b}c$$

$$F2 = \bar{a}b\bar{c}$$

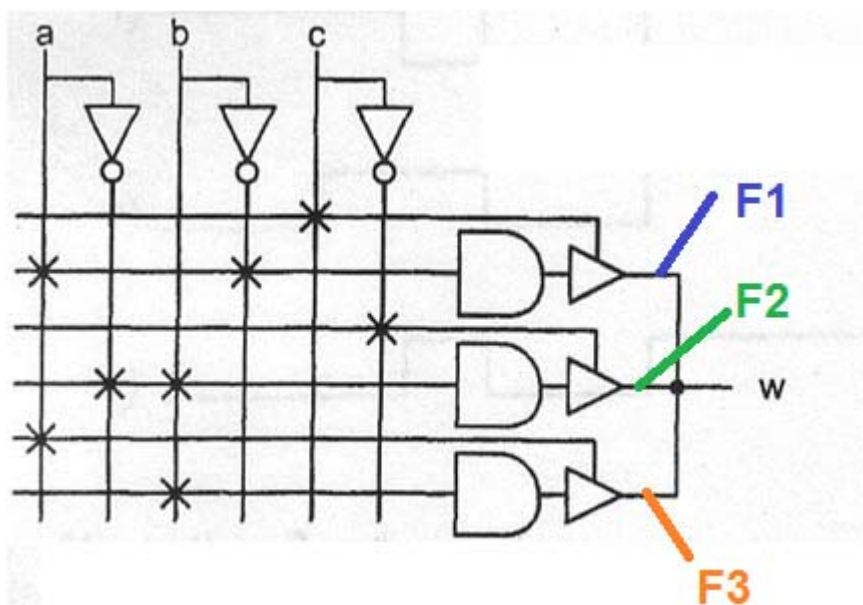

a	0	0	0	0	1	1	1	1	2)	a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x		w	1	0	1	1	1	1	1	1	


a	0	0	0	0	1	1	1	1	4)	a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0		w	0	0	1	0	0	1	x	1	



$$F1 = a\bar{b}c$$

$$F2 = \bar{a}b\bar{c}$$

$$F3 = ab$$

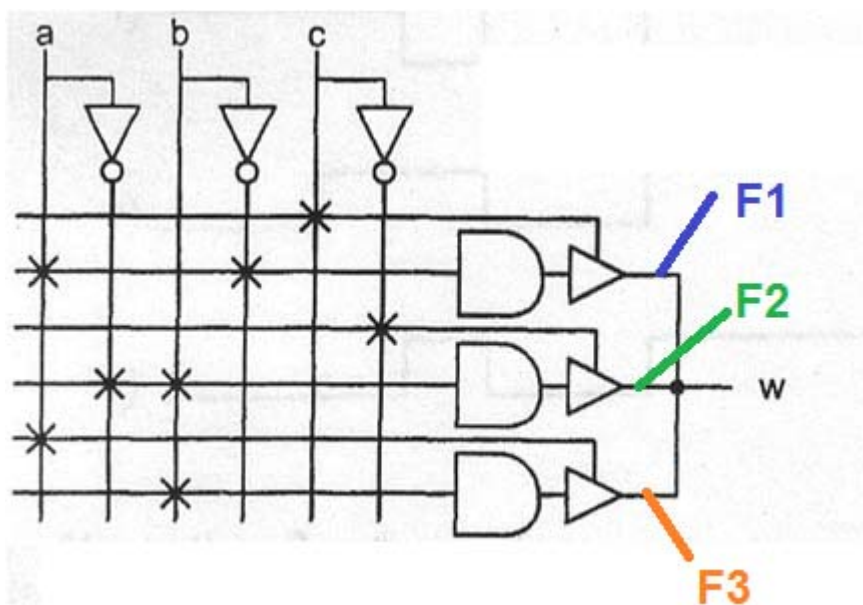

a	0	0	0	0	1	1	1	1	2)	a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x		w	1	0	1	1	1	1	1	1	

a	0	0	0	0	1	1	1	1	4)	a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0		w	0	0	1	0	0	1	x	1	




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

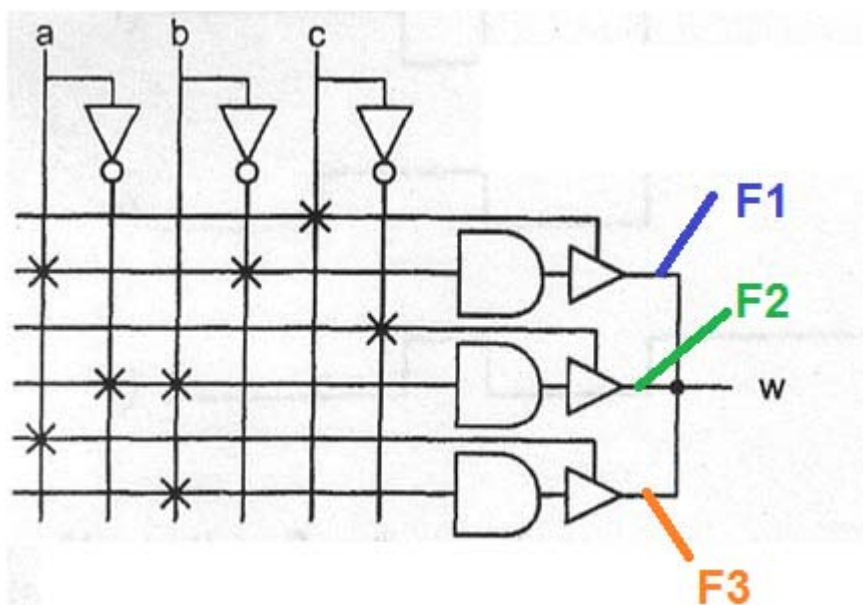

a	0	0	0	0	1	1	1	1	2)	a	0	0	0	0	1	1	1	1	1)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	x	x	x		w	1	0	1	1	1	1	1	1	

a	0	0	0	0	1	1	1	1	4)	a	0	0	0	0	1	1	1	1	3)
b	0	0	1	1	0	0	1	1		b	0	0	1	1	0	0	1	1	
c	0	1	0	1	0	1	0	1		c	0	1	0	1	0	1	0	1	
w	0	0	1	0	0	0	0	0		w	0	0	1	0	0	1	x	1	




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

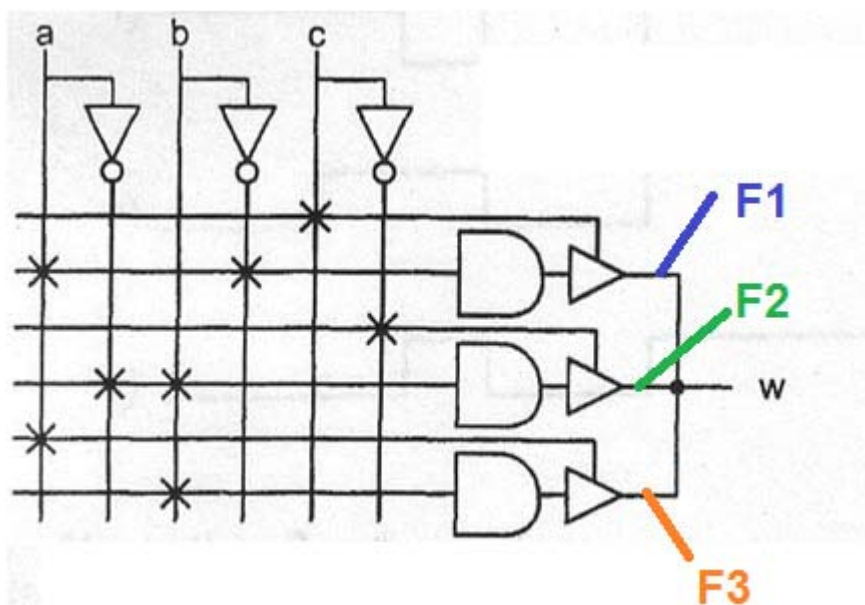

a	b	c	F1	F2	F3	w
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

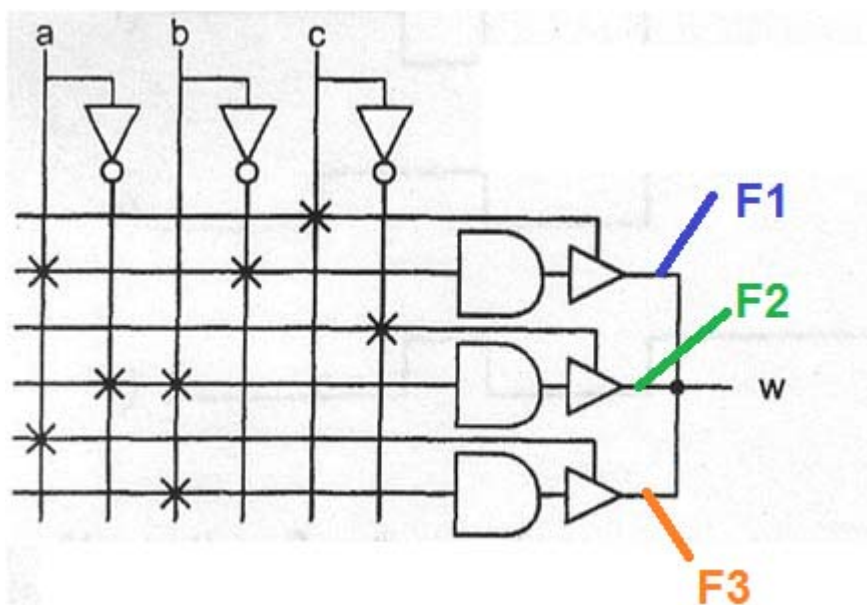

a	b	c	F1	F2	F3	w
0	0	0	-			
0	0	1	0			
0	1	0	-			
0	1	1	0			
1	0	0	-			
1	0	1	1			
1	1	0	-			
1	1	1	0			




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

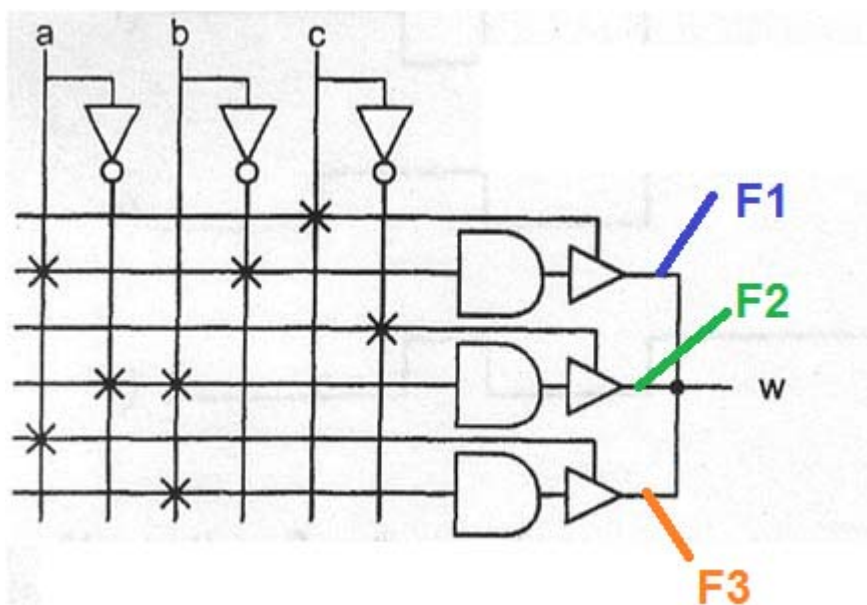

a	b	c	F1	F2	F3	w
0	0	0	-	0		
0	0	1	0	-		
0	1	0	-	1		
0	1	1	0	-		
1	0	0	-	0		
1	0	1	1	-		
1	1	0	-	0		
1	1	1	0	-		




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

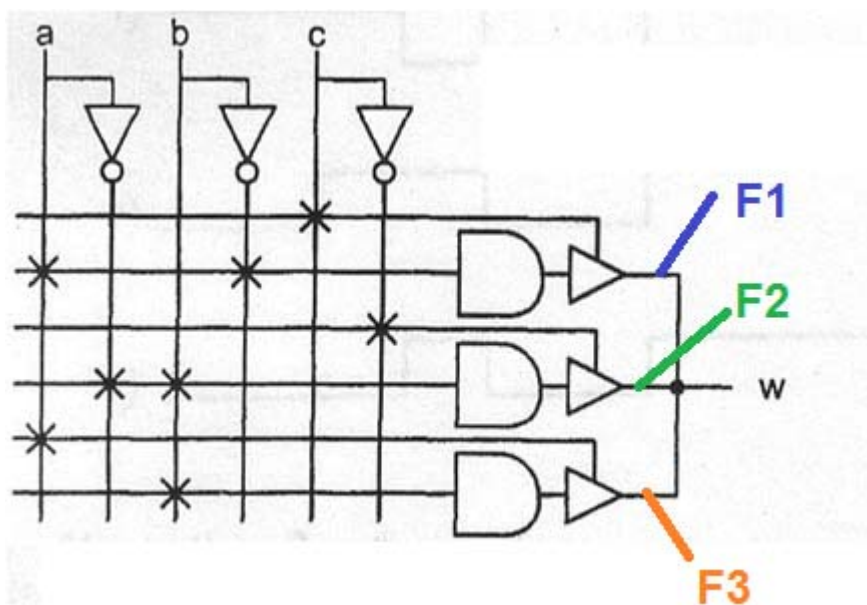

a	b	c	F1	F2	F3	w
0	0	0	-	0	-	
0	0	1	0	-	-	
0	1	0	-	1	-	
0	1	1	0	-	-	
1	0	0	-	0	0	
1	0	1	1	-	0	
1	1	0	-	0	1	
1	1	1	0	-	1	




$$F1 = a\bar{b}c$$

$$F3 = ab$$

$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

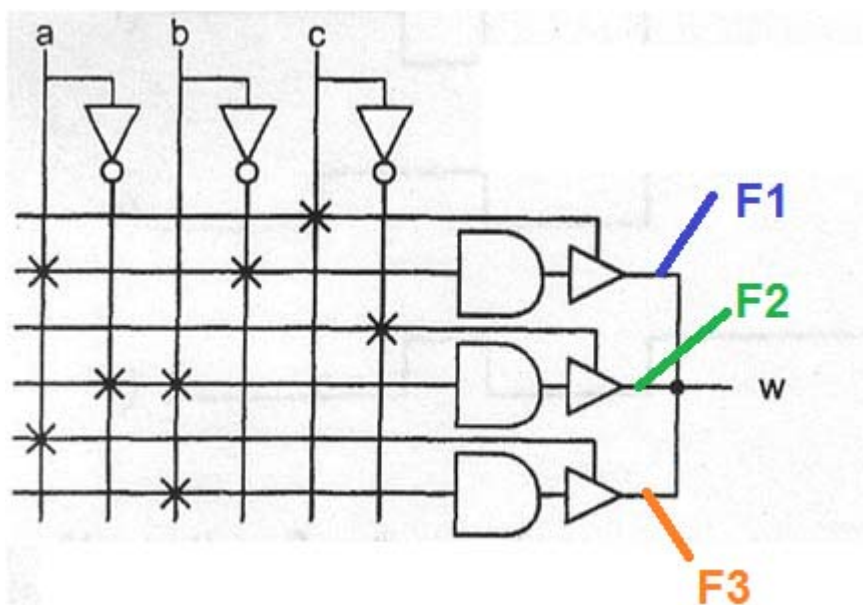

a	b	c	F1	F2	F3	w
0	0	0	-	0	-	0
0	0	1	0	-	-	0
0	1	0	-	1	-	1
0	1	1	0	-	-	0
1	0	0	-	0	0	0
1	0	1	1	-	0	X
1	1	0	-	0	1	X
1	1	1	0	-	1	X




$$F1 = a\bar{b}c$$

$$F3 = ab$$


$$F2 = \bar{a}b\bar{c}$$

$$W = F1 + F2 + F3$$

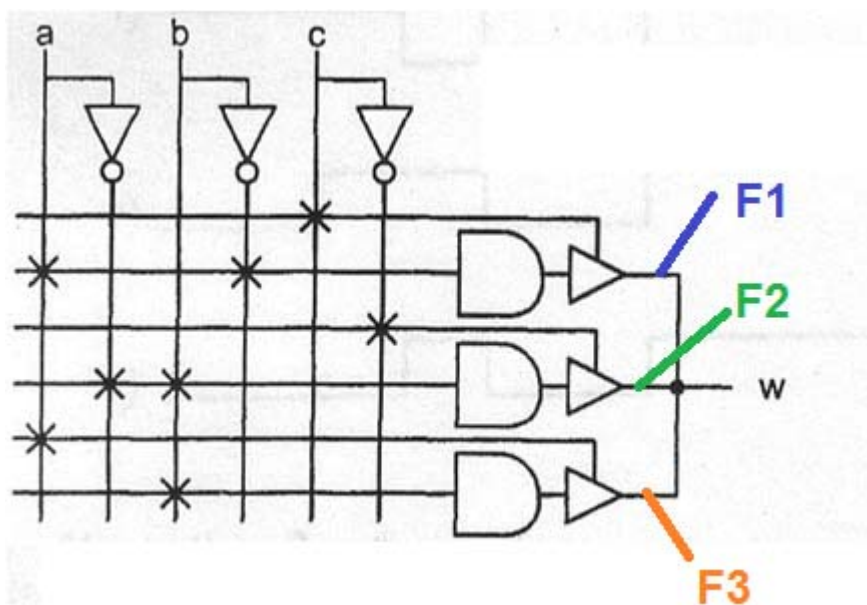


a	b	c	F1	F2	F3	w
0	0	0	-	0	-	0
0	0	1	0	-	-	0
0	1	0	-	1	-	1
0	1	1	0	-	-	0
1	0	0	-	0	0	0
1	0	1	1	-	0	X
1	1	0	-	0	1	X
1	1	1	0	-	1	X

(2)

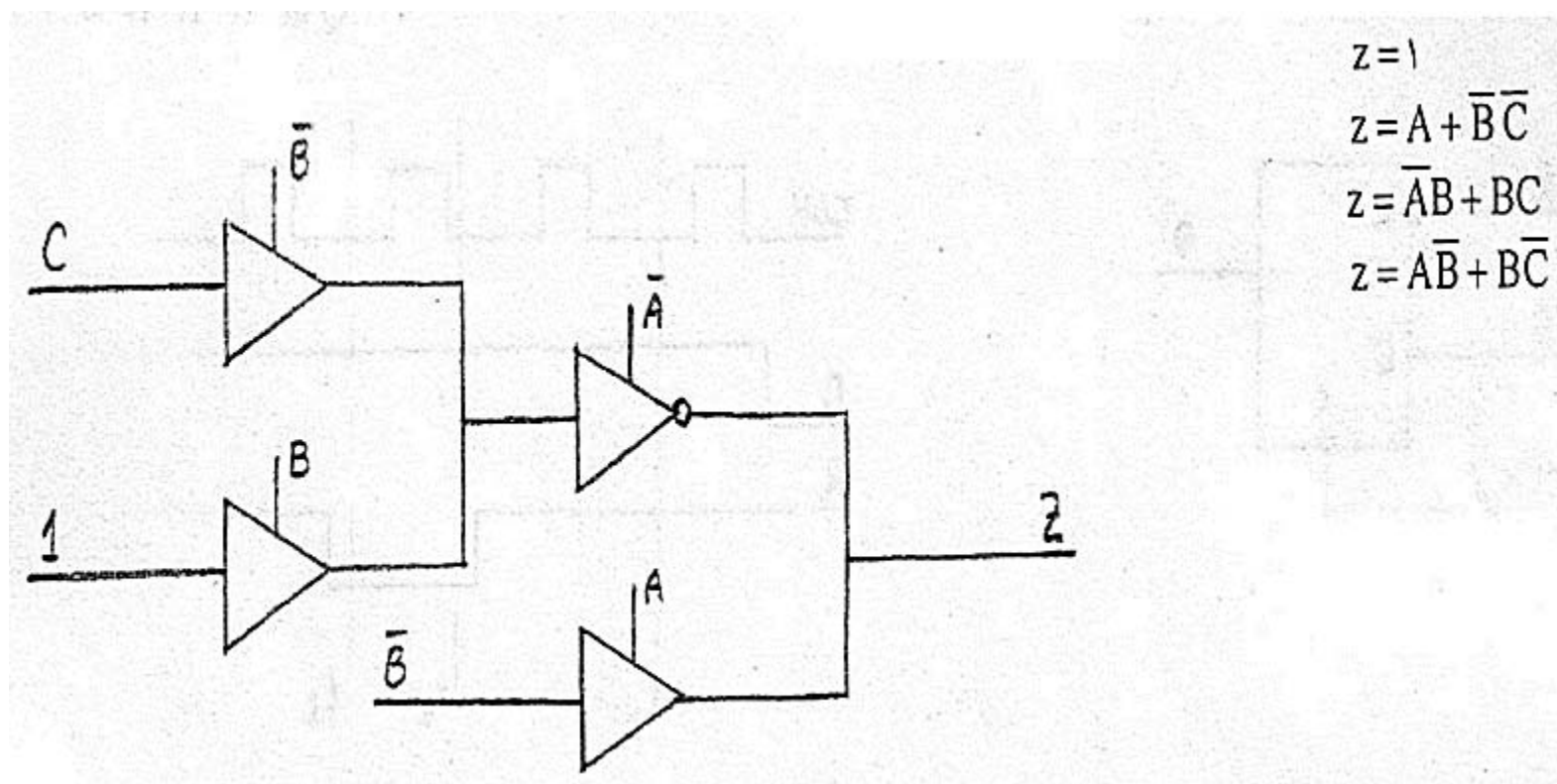

If $A = B$ then determine the output:

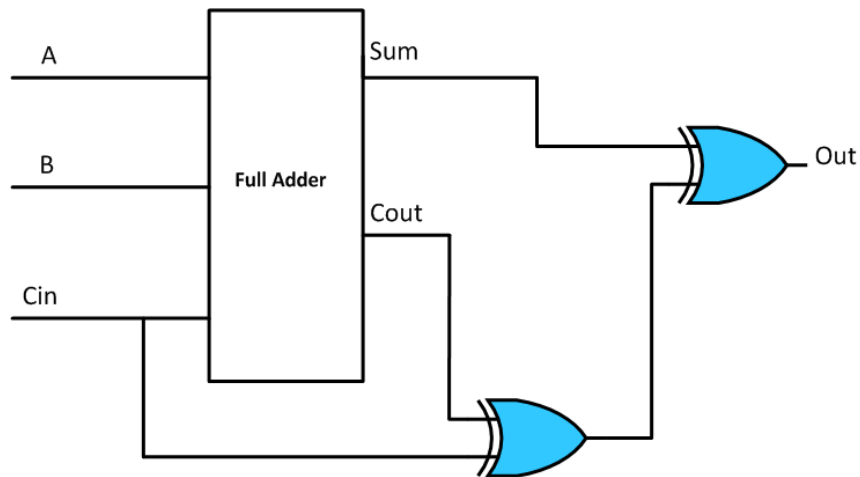

Out	
Cin	1
Sum	2
Cout	3
Sum' Xor Cout	4



Thank You